Signal (frequency) synthesis


Lecturer: Krébesz, Tamás



Oscillator-based freq. synth.


- Traditional way
- Uses a bank of oscillators
- Mixing, adding frequencies are performed my multiplier circuits (mixers)

Oscillator bank

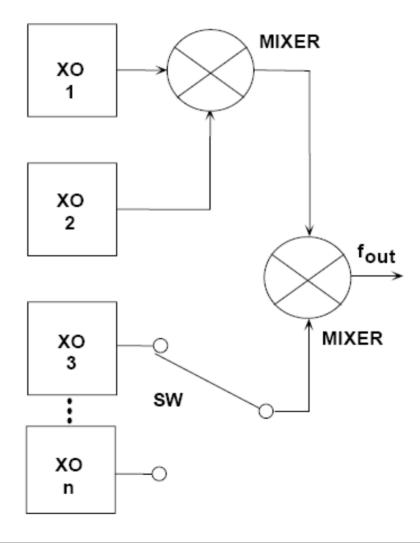


Phase-locked loop

More flexible solution

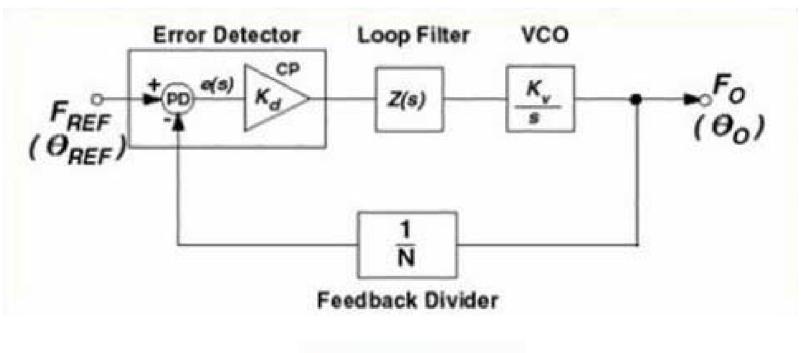


$$F_0 = N \times F_{REF}$$

Direct digital synthesizer (DDS)

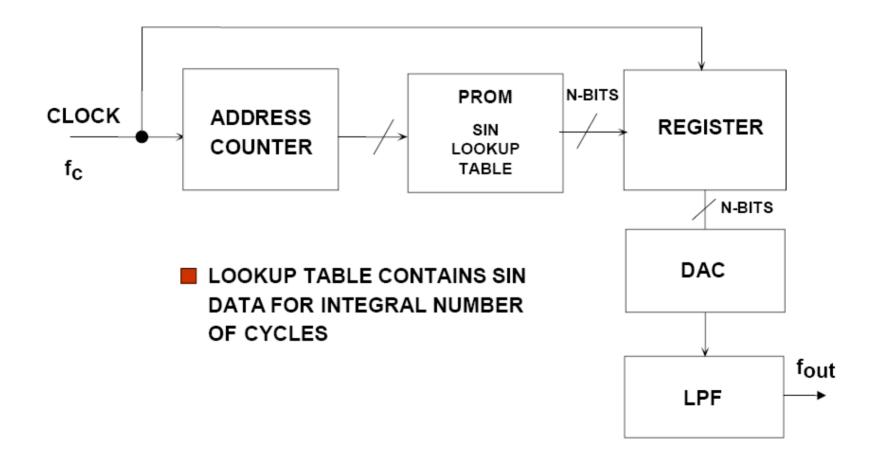

- In PROM arbitrary waveform can be stored (not necessarily sine)
- Frequency can be changed by
 - Changing fc
 - Reprogramming PROM (not typical)

Flexible, NCO-based DDS

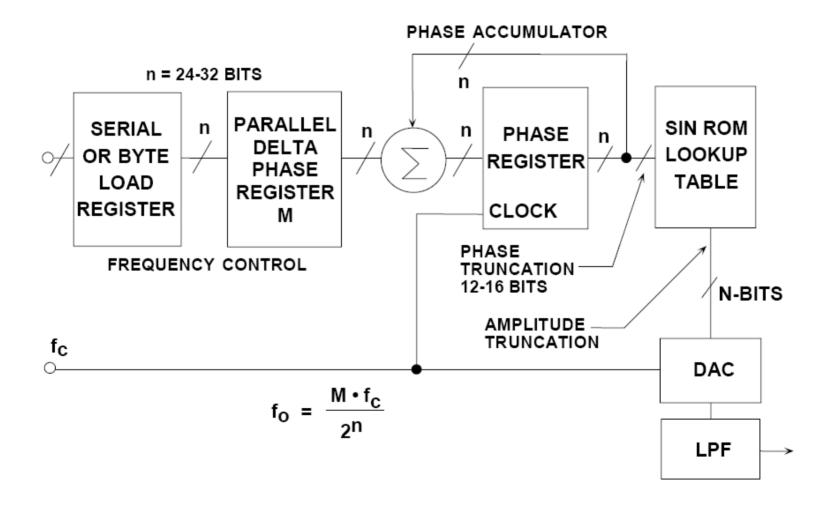

References

Analog devices: Mixed signal and DSP design techniques