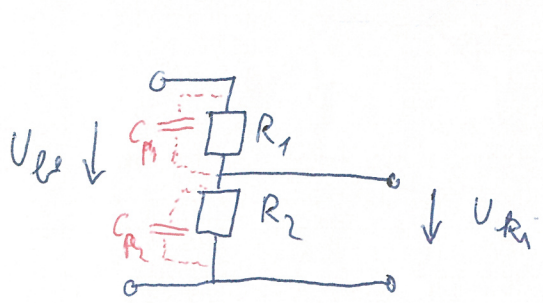



5.3. Kompensált osztó




$$C_1 \gg C_{p1}$$

$$C_2 \gg C_{p2}$$

$$\Rightarrow$$

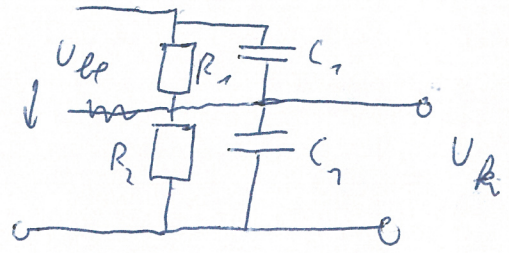

RC - tag

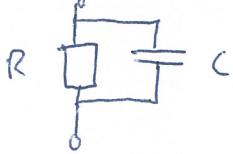

$$Z = \frac{R \cdot \frac{1}{sC}}{R + \frac{1}{sC}} = \frac{R}{1 + sRC}$$

osztó átvitele:

$$a = \frac{Z_2}{Z_1 + Z_2} = \frac{\frac{R_2}{1 + sR_2C_2}}{\frac{R_1}{1 + sR_1C_1} + \frac{R_2}{1 + sR_2C_2}}$$

$$R_1C_1 = R_2C_2$$

$$\Downarrow$$

$$\frac{R_2}{R_1 + R_2} \leftarrow \text{eredeti átvitel nagyfrekvencián is!}$$


$$a = \frac{1}{10} \quad R_2 = 100 \text{ k}\Omega \quad C_2 = 100 \text{ pF}$$

$$\downarrow \quad R_1 = ? \quad C_1 = ?$$

$$R_1 = 900 \text{ k}\Omega \quad C_1 = \frac{R_2 C_2}{R_1} = \frac{100}{9} \text{ pF} = 11,1 \text{ pF}$$

Bemeneti impedancia: Z1+Z2

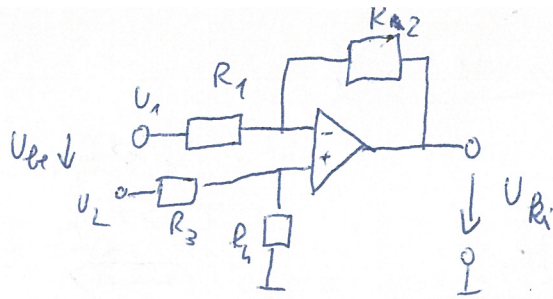5.20. $R_1 = 1,5 \text{ k}\Omega$
 $R_2 = 150 \text{ k}\Omega$
 $R_3 = 2,8 \text{ k}\Omega$
 $R_4 = 280 \text{ k}\Omega$
 $A_s = 100$



$$U_{ki} = -U_1 \cdot \frac{R_2}{R_1} + U_2 \cdot \frac{R_4}{R_3 + R_4} \cdot \left(1 + \frac{R_2}{R_1}\right)$$

$$U_{ki,c} = -U_c \cdot \frac{R_2}{R_1} + U_c \cdot \frac{R_4}{R_3 + R_4} \cdot \left(1 + \frac{R_2}{R_1}\right)$$

$$U_1 = U_c + \frac{U_s}{2} \quad U_2 = U_c - \frac{U_s}{2}$$

$$A_{u,c} = \frac{U_{ki,c}}{U_c} = -\frac{R_2}{R_1} + \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1}\right) = \frac{-R_2 R_3 - R_2 R_4 + R_1 R_4 + R_2 R_4}{R_1 (R_3 + R_4)}$$


$$= \frac{R_1 R_4 - R_2 R_3}{R_1 (R_3 + R_4)}$$

$$A_c \approx \frac{R_1 R_4 (1+h)^2 - R_2 R_3 (1-h)^2}{R_1 (R_3 + R_4)} \approx \frac{R_4}{R_3 + R_4} \cdot 4h$$

$R_1 R_4 \approx R_2 R_3$

$$U_{ki,s} = -\frac{U_s}{2} \cdot \frac{R_2}{R_1} - \frac{U_s}{2} \cdot \frac{R_4}{R_3 + R_4} \cdot \left(1 + \frac{R_2}{R_1}\right)$$

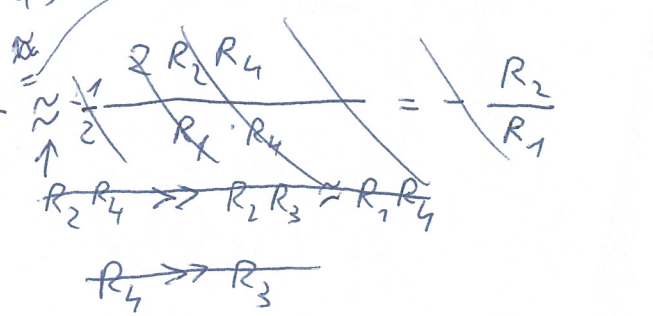
$$A_s = -\frac{1}{2} \cdot \frac{R_2 R_3 + R_2 R_4 + R_1 R_4 + R_2 R_4}{R_1 (R_3 + R_4)}$$



$$E_{w.c} = \frac{|A_c|}{|A_s|} = \frac{R_2}{R_1} \cdot \frac{R_3 + R_4}{R_4 \cdot 4h} = 12625 \approx 82 \text{ dB}$$

5.26.

u_{ke}

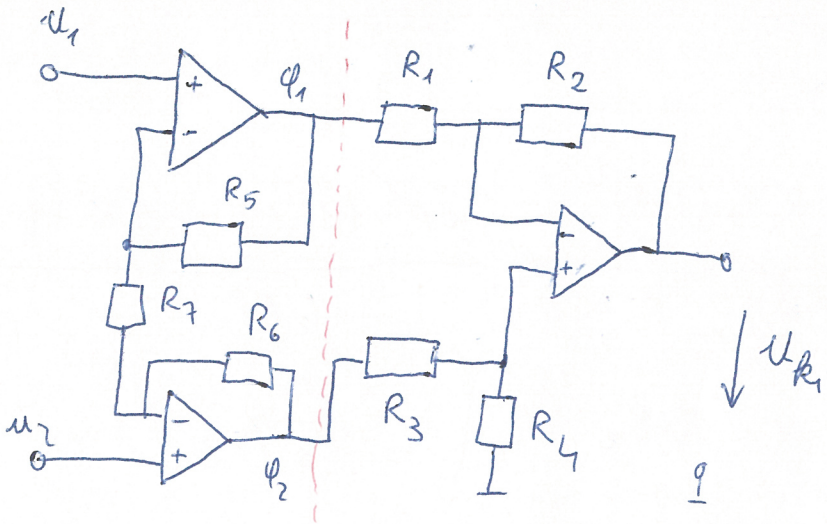

- 4db 25 kΩ
- 2db 5 kΩ
- 1db 5,55 kΩ

$A_S \stackrel{!}{=} 50$

①-es fokozat ②-es fokozat

② Differencialvisitas $\Rightarrow A_{S,2} = \frac{R_1 R_4 - R_2 R_3}{R_1 (R_3 + R_4)}$

$A_{S,2} = -\frac{R_2}{R_1}$

$R_1 R_4 \stackrel{!}{=} R_2 R_3$

① $\phi_1 = u_1 \cdot \left(1 + \frac{R_5}{R_7}\right) - u_2 \cdot \frac{R_5}{R_7}$

$\phi_2 = u_2 \left(1 + \frac{R_6}{R_7}\right) - u_1 \left(\frac{R_6}{R_7}\right)$

$\phi_{1,c} = u_c \left(1 + \frac{R_5}{R_7}\right) - u_c \frac{R_5}{R_7} = u_c \quad \left. \vphantom{\phi_{1,c}} \right\} A_{S,1} = 1$

$\phi_{2,c} = u_c$

$\phi_{1,s} = \frac{u_s}{2} \cdot \left(1 + \frac{R_5}{R_7}\right) + \frac{u_s}{2} \cdot \frac{R_5}{R_7} = \frac{u_s}{2} \left(1 + 2 \frac{R_5}{R_7}\right)$

$\phi_{2,s} = -\frac{u_s}{2} \left(1 + 2 \frac{R_6}{R_7}\right)$

$\frac{R_5}{R_7} = \frac{R_6}{R_7}$ legyen

\Downarrow
 $R_5 = R_6$

$R_1 = R_3 = 5 \text{ k}\Omega \quad R_2 = R_4 = R_5 = R_6 = 25 \text{ k}\Omega \quad R_7 = 5,55 \text{ k}\Omega$

$A_S = -\frac{R_2}{R_1} \left(1 + 2 \frac{R_5}{R_7}\right) = -50,045 \Rightarrow h_r = 0,09\%$

$$A_c = A_{c2} = \frac{R_1 R_4 - R_2 R_3}{R_1 (R_3 + R_4)}$$

$$R_1' = 1 \pm h$$

$$A_{c,wc} \approx \frac{R_1 R_4 (1+h)^2 - R_2 R_3 (1-h)^2}{R_1 (R_3 + R_4)} = \frac{5R^2 (1+h)^2 - 5R^2 (1-h)^2}{6R^2} \approx \frac{5R^2 4h}{6R^2}$$


$$R_1 = R_3 = R \quad R_2 = R_4 = 5R \quad \left| \quad = \frac{10}{3} h$$

$$E = \frac{|A_s|}{|A_c|} = \frac{|A_s|}{|A_c|} = \frac{-\frac{R_2}{R_1} \left(1 + 2 \frac{R_5}{R_7}\right)}{\frac{10}{3} h} = 75000 = 97,5 \text{ dB}$$

5.16. $A' = -5$

$R_1 = 1 \text{ k}\Omega$


$R_2 = 5,1 \text{ k}\Omega$

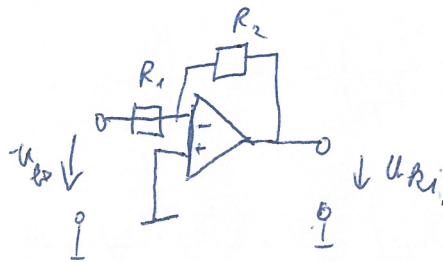


-0.1 +2%

$$A = -\frac{R_2}{R_1} = -5,1$$

$h_r = +2\%$

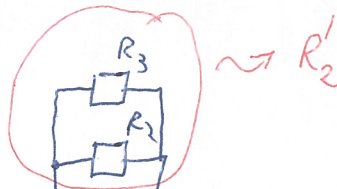

b) $R_3 = 270 \text{ k}\Omega$

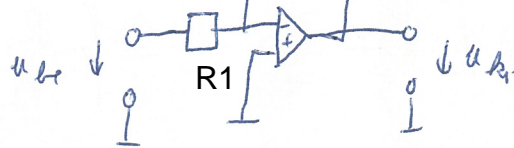

$$R_2' = R_2 \times R_3 = 5,0055 \text{ k}\Omega$$

$$R_1' = \begin{matrix} h_1 = 0,1\% \\ h_2 = 0,1\% \\ h_3 = 5\% \end{matrix}$$

$$A' = -5,0055 \quad h_r' = +0,11\%$$

$$A' = -R_2' / R_1 = -(R_2 \times R_3) / R_1$$

$$\frac{\Delta A'}{A'} \Big|_{w.c} = h_r' + \frac{\Delta R_1}{R_1} + \frac{R_3}{R_2 + R_3} \frac{\Delta R_2}{R_2} + \frac{R_2}{R_2 + R_3} \frac{\Delta R_3}{R_3} = 0,4\%$$

$$R_2' = \frac{R_2 R_3}{R_2 + R_3}$$


$$\frac{\partial R_2'}{\partial R_2} = \frac{R_3}{R_2 + R_3} - \frac{R_2 R_3}{(R_2 + R_3)^2}$$

$$= \frac{R_3^2}{(R_2 + R_3)^2}$$

$$\frac{\Delta R_2'}{R_2'} \Big|_{R_1} = \frac{\frac{R_3^2}{(R_2 + R_3)^2} \cdot R_2}{\frac{R_2 R_3}{R_2 + R_3}} \frac{\Delta R_2}{R_2}$$

$$= \frac{R_3}{R_2 + R_3} \cdot \frac{\Delta R_2}{R_2}$$

5.17

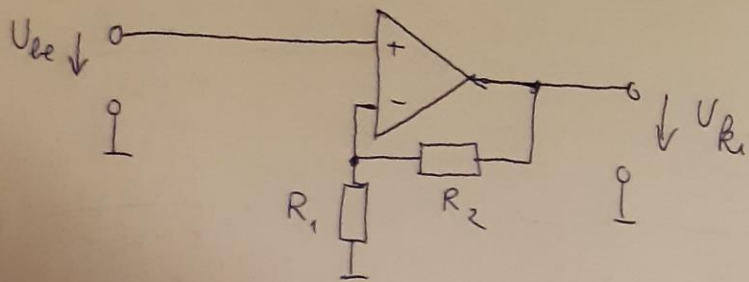

$$R_1 = 1 \text{ k}\Omega$$

$$R_2 = 9.1 \text{ k}\Omega$$

$$A_m = 1 + \frac{R_2}{R_1} = 10,1$$

$$A_v \stackrel{!}{=} 10 \rightarrow h_r = +1\%$$

$$\left. \frac{\Delta A}{A} \right|_{w.c} = \frac{R_3 + R_4}{R_1 + R_3 + R_4} \cdot h_r$$

$$+ \frac{R_3}{R_1 + R_3 + R_4} \cdot h_v + \frac{R_4}{R_1 + R_3 + R_4} \cdot h_v$$

$$= \frac{2(R_3 + R_4)}{R_1 + R_3 + R_4} \cdot h_v$$

$$\frac{2 \cdot 9 \text{ k}\Omega}{10 \text{ k}\Omega} \cdot 0,11\%$$

$$= 0,18\%$$


$$R_3 = 6,8 \text{ k}\Omega \quad R_4 = 2,2 \text{ k}\Omega$$

$$R_2' = R_3 + R_4$$

$$R_2' = 9 \text{ k}\Omega$$

$$A_m = 1 + \frac{R_2'}{R_1} = 10 \quad h_r = 0$$

h_rendszo = 0

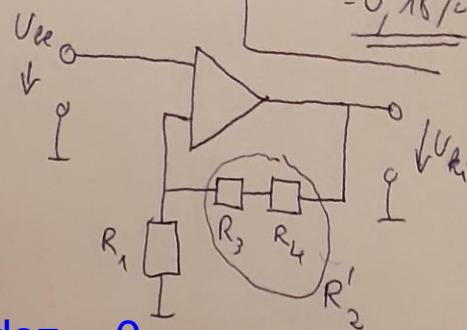

$$h_v = 0,1\%$$

$$\left. \frac{\Delta A}{A} \right|_{w.c} = \frac{\Delta R_1}{R_1} + \frac{\Delta R_2'}{R_2'}$$

$$A = 1 + \frac{R_2'}{R_1} = 1 + \frac{R_3 + R_4}{R_1} = \frac{R_1 + R_3 + R_4}{R_1}$$

$$\frac{\partial A}{\partial R_1} = - \frac{R_3 + R_4}{R_1^2}$$

$$\left. \frac{\Delta A}{A} \right|_{R_1} = \frac{- \frac{R_3 + R_4}{R_1^2} \cdot R_1}{\frac{R_1 + R_3 + R_4}{R_1}} \cdot \frac{\Delta R_1}{R_1} = - \frac{R_3 + R_4}{R_1 + R_3 + R_4} \cdot \frac{\Delta R_1}{R_1}$$

$$\frac{\partial A}{\partial R_3} = \frac{1}{R_1}$$

$$\left. \frac{\Delta A}{A} \right|_{R_3} = \frac{\frac{1}{R_1} \cdot R_3}{\frac{R_1 + R_3 + R_4}{R_1}} \cdot \frac{\Delta R_3}{R_3} = \frac{R_3}{R_1 + R_3 + R_4} \cdot \frac{\Delta R_3}{R_3}$$

$$\frac{\partial A}{\partial R_4} = \frac{1}{R_1}$$

$$\left. \frac{\Delta A}{A} \right|_{R_4} = \frac{\frac{1}{R_1} \cdot R_4}{\frac{R_1 + R_3 + R_4}{R_1}} \cdot \frac{\Delta R_4}{R_4} = \frac{R_4}{R_1 + R_3 + R_4} \cdot \frac{\Delta R_4}{R_4}$$

*