



BUDAPEST UNIVERSITY OF TECHNOLOGY AND ECONOMICS
FACULTY OF ELECTRICAL ENGINEERING AND INFORMATICS
DEPARTMENT OF MEASUREMENT AND INFORMATION SYSTEMS

Digital Design (VIMIAA01)

Introduction to the Verilog HDL

Tamás Raikovich
BUTE DMIS

BME-MIT

FPGA labor

Hardware Description Languages

- Hardware description languages have been developed for modeling and simulating hardware functions
- Only a part of the language elements can be used for design implementation
- Difference between standard programming languages and hardware description languages:
 - Standard programming languages: *sequential*
 - HDLs: describe *parallel* and *concurrent* behavior
- Two important HDLs:
 - *Verilog*
 - VHDL

BME-MIT


FPGA labor

Verilog HDL

- The Verilog HDL is similar to the C/C++ programming languages in many ways, for example:
 - Distinguishes the small and capital letters
 - Single-line comment: //
 - Block comment: /* */
 - Most of the operators are the same
- But the Verilog source code is not a software!
- Hereafter, only those language constructs will be introduced which can be used for implementing hardware designs
 - There are special language constructs for verification and simulation only

Verilog HDL - Modules

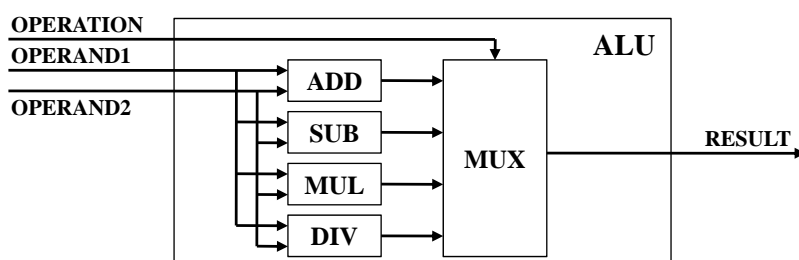- Verilog language uses a hierarchical, functional unit based design approach:
 - The whole design consists of several smaller *modules*
 - The complexity of the modules is decided by the designer
- Verilog module:
 - Definition of the input and output ports, through which the module is connected to the "outside world"
 - Definition of the logical relationship between the input and output ports



Verilog HDL – Modules

(Port declaration)

- The ports of the top-level module are connected to the I/O pins of the used hardware device
- Common syntax of the module declaration:

```
Module name
┌───────────┐
module SomeFunction(
    input  wire [7:0] op1,
    input  wire [7:0] op2,
    output wire [7:0] result
);
    assign result = op1 + op2;
endmodule
```

Port declaration in the port list of the module

Description of the functionality

Verilog HDL – Modules

(Port declaration)

- Port declaration syntax:
<direction> <data_type> <size> <port_name>;
- Direction:
 - Input port: *input*
 - Output port: *output*
 - Bi-directional: *inout*
- Data type: **wire is the default data type when omitted**
 - *wire*: behaves as its name says
 - *reg*: not always becomes a real register (data storage element)
 - Only output ports and internal signals can be *reg* type
- Signed type:
 - The *signed* keyword indicates that the signal represents a *two's complement* signed value
- Size: [j : i] → The size of the port is |j – i| + 1 bits
 - The rightmost bit is the j-th bit (j ≤ i is also allowed)
 - The leftmost bit is the i-th bit
 - Swapping the indices doesn't affect the bit order


Verilog HDL – Modules

(Port declaration)

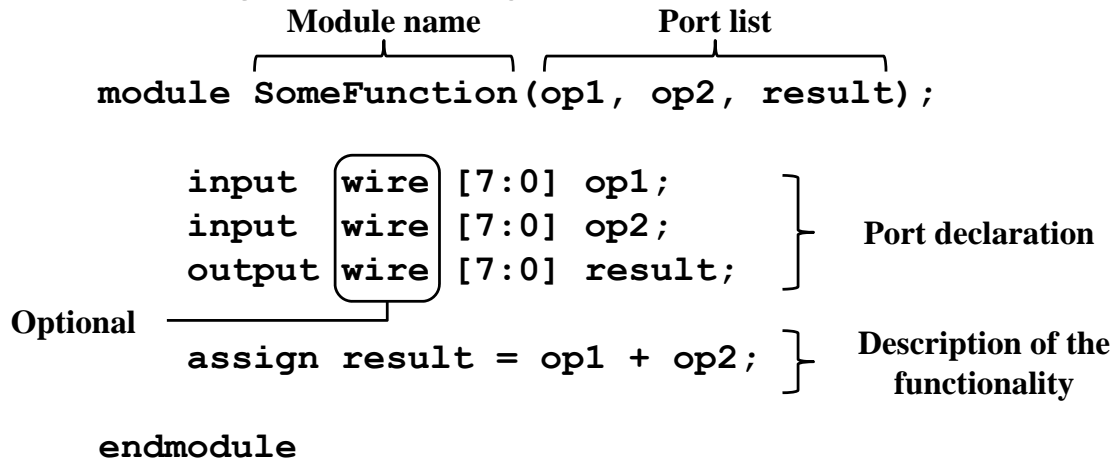- **Examples:**

- 1-bit input port: `input wire sel;`
- 16-bit output register: `output reg [15:0] result;`

- **Older syntax of the port declaration:**




Verilog HDL – Modules

(Module instantiation)

- **Module to be instantiated:**

```
module SomeFunction(input A, input B, output C);
  ...
endmodule
```

 - **This can be instantiated (i.e. can be used) in other modules by the following way:**



- **More instances can be created from a module, but every instance name must be different**

Verilog HDL – Modules

(Module instantiation – Example)

- **Problem: create a 4-bit binary adder by cascading 4 single-bit full adders (FADD)**
- **The header of the single-bit full adder (FADD) module**

```
module FADD(  
    input wire    a,    // "a" operand  
    input wire    b,    // "b" operand  
    input wire    ci,   // Input carry  
    output wire   s,    // Sum output  
    output wire   co    // Output carry  
);
```

- **4 FADD adders have to be instantiated in the module which implements the 4-bit adder**

Verilog HDL – Modules

(Module instantiation – Example)

```
module ADDER4(  
    input wire [3:0] a,    // 4-bit A operand input  
    input wire [3:0] b,    // 4-bit B operand input  
    input wire    ci,     // Input carry  
    output wire [3:0] s,   // 4-bit sum output  
    output wire    co     // Output carry  
);  
  
wire [4:0] c;    // The full internal carry chain  
  
assign c[0] = ci; // The 0th bit of the carry chain is the input carry  
  
// 4 FADD modules are built in, their names are ADD0, ADD1, ADD2, ADD3  
// Connecting the interfaces is obvious, carry is used for cascading  
FADD  ADD0(.a(a[0]), .b(b[0]), .ci(c[0]), .s(s[0]), .co(c[1]));  
FADD  ADD1(.a(a[1]), .b(b[1]), .ci(c[1]), .s(s[1]), .co(c[2]));  
FADD  ADD2(.a(a[2]), .b(b[2]), .ci(c[2]), .s(s[2]), .co(c[3]));  
FADD  ADD3(.a(a[3]), .b(b[3]), .ci(c[3]), .s(s[3]), .co(c[4]));  
  
assign co = c[4]; // The output carry is the 4th bit of the carry chain  
  
endmodule
```

Verilog HDL – Modules

(Internal signal declaration)

- **Internal signal declaration syntax:**
`<data_type> <size> <signal_name>;`
- Same as the port declaration, but there is no direction specification and the data type cannot be omitted
- **Examples:**
 - 1-bit wire: `wire counter_enable;`
 - 16-bit register: `reg [15:0] counter;`



Verilog HDL – Constants

(Possible signal values)

- **In the Verilog language, signals can have four values**
 - **0**: logic low level
 - **1**: logic high level
 - **z**: high-impedance state
 - **x**: unknown, cannot be determined, don't care
- **In case of the modern hardware system design, the z value (high-impedance state) is used only for implementing I/O interfaces**
- **In case of hardware implementation, the x value (don't care) can be used only to simplify the description (casex instruction)**



Verilog HDL – Constants

(Numeric constants)

- **Numeric constant definition syntax:**
`<-><bit_number>'<s><number_system><numeric_constant>`
- **The signed constants are two's complement codes**
- **Minus sign: generates the two's complement of the constant**
- **Bit number: size of the constant in bits**
 - The default size is 32 bits if omitted
- **Signed constant: indicated by the s character**
 - The constant is unsigned if omitted
 - The sign bit has to be interpreted according to the bit number
 - The sign extension is automatic in case of the signed constants
- **Number system: decimal is the default if omitted**
 - Binary: **b**, octal: **o**, decimal: **d**, hexadecimal: **h**
- **The '_' character can be used for separating the digits**
 - This produces a more readable and cleaner code



Verilog HDL – Constants

(Numeric constants – Examples)

Examples:

- **8'b0000_0100: 8-bit binary constant, its decimal value is 4**
- **6'h1f: 6-bit hexadecimal constant, its decimal value is 31**
 - In binary: **6'b01_1111**
- **128: 32-bit decimal constant**
 - In binary: **32'b00000000_00000000_00000000_10000000**
- **-4'sd15: 4-bit decimal constant, its value is 1**
 - The **4'sd15** itself in binary is **4'sb1111**, i.e. **-1** (signed!)
 - The minus sign generates the 2's complement → **4'sb0001**

Examples for the sign extension (repeating the original MSb bit):

```
wire [7:0] a = 4'd9; //a=6'b0000_1001 (9)
wire [7:0] b = 4'sd5; //b=6'b0000_0101 (5)
wire [7:0] c = 4'sd9; //c=6'b1111_1001 (-7)
wire [7:0] d = -4'd6; //d=6'b1111_1010 (-6)
```



Verilog HDL – Konstansok

(String constants)

- **String (text) constant declaration syntax:**
"characters_of_the_string"
- **Very useful for simulating controllers:** can be used to display the states as text
- **The characters of the strings are mapped to their 8-bit ASCII codes,** therefore the bit number of the string constant is 8 times the number of characters
- **The upper 8 bits have the value of the first character**
- **Example:**

```
wire [23:0] str = "HDL";  
//str[7:0]    = 8'b0100_1100 ('L')  
//str[15:8]  = 8'b0100_0100 ('D')  
//str[23:16] = 8'b0100_1000 ('H')
```



Verilog HDL – Parameters

(Parameter declaration)

- **Parameter definition syntax:**
parameter <name> = <constant>;
localparam <name> = <constant>;
- **The parameter name can be used as a constant in the module where the parameter is declared**
- **Normal parameters:** their default value can be changed when the module is instantiated
- **Local parameters:** their value cannot be changed
- **Example:**

```
parameter WIDTH = 8;  
  
wire [WIDTH-1:0] data;
```



Verilog HDL – Parameters

(Parameter declaration)

- **Alternative module definition syntax: normal parameters can be declared in the module header**

```

      Module name
    module SomeFunction #(
      parameter WIDTH = 8,
      parameter OTHER_PARAM = 2
    ) (
      input wire [WIDTH-1:0] op1,
      input wire [WIDTH-1:0] op2,
      output wire [WIDTH-1:0] result
    );

    assign result = op1 + op2;

endmodule
```

Parameter declaration in the module header

Port declaration in the port list

Description of the functionality

Verilog HDL – Parameters

(Instantiating module with parameters)

- **Module with parameters:**

```
module SomeFunction(input A, input B, output C);
parameter P1 = 8;
parameter P2 = 16;
  ⋮
endmodule
```

- **Instantiating this module:**

```
wire d, e, f;
SomeFunction #(
  .P1(3), .P2(20)
) Func2 (
  .A(f), .B(e), .C(d)
);
```

Giving new values to the parameters (optional)

Associating signals with ports

Verilog HDL - Operators

- The Verilog operators can have 1, 2 or 3 operands
- On the right side of the expressions, *wire* type, *reg* type and constant operands can appear
- If an operation requires same operand size, the smaller operand usually zero-extended to the size of the larger operand
- The expression evaluation is done by the normal precedence rules (the precedence can be controlled using brackets)

Operator	Precedence
Unary +, -, !, ~	1. (highest)
*, /, %	2.
Binary +, -	3.
<<, >>, <<<, >>>	4.
<, <=, >, >=	5.
==, !=, ===, !==	6.

Operator	Precedence
&, ~&	7.
^, ~^	8.
, ~	9.
&&	10.
	11.
?: (conditional op.)	12. (lowest)

Verilog HDL – Operators

(Arithmetic operators)

Arithmetic operators: + (addition), - (subtraction), * (multiplication), / (division), % (modulus)

- Number of operands: 2
- If the FPGA doesn't contain multipliers, the multiplication operator can be synthesized only if one of the operands is a power of 2 value
- The division and the modulus operators can be synthesized only if the right side operand is a power of 2 value
- **In case of addition, subtraction and multiplication, the smaller size signed operand is sign-extended to the size of the larger operand**
- Carry bit usability in case of addition and subtraction in the Xilinx FPGA devices:

	Adder	Subtractor	Adder/subtractor
Input carry bit (C _{in})	Available	Available	Not available
Output carry bit (C _{out})	Available	Not available	Not available

Verilog HDL – Operators

(Concatenation operator)

- **Concatenation operator: { }**
 - Appending multiple operands
`{5'b10110, 2'b10, 1'b0, 1'b1} = 9'b1_0110_1001`
 - The same operand can be concatenated multiple times
`{4{3'b101}}` = 12'b101_101_101_101
- **Important use cases:**
 - Sign extension: the sign bit must be copied to the upper bits
`wire [3:0] s_4bit; //4-bit signed`
`wire [7:0] s_8bit; //8-bit signed`
`assign s_8bit = {{4{s_4bit[3]}}, s_4bit};`
 - Masking a vector with a single bit: without concatenation, the smaller single-bit operand would be zero-extended to the size of the larger operand
`wire [3:0] data;`
`wire [3:0] mdata;`
`wire enable;`
`assign mdata = data & enable; //Wrong!!!`
`assign mdata = data & {4{enable}}; //Correct`

Verilog HDL – Operators

(Conditional and indexer operators)

- **Conditional operator: ? :**
`<conditional_expression> ? <expression1> : <expression2>`
 - This is the only operator with 3 operands
 - First, the **conditional_expression** is evaluated
 - If the result is not 0: **expression1** is evaluated
 - If the result is 0: **expression2** is evaluated
- **Selecting a part of a vector:**
`vector_name[i], vector_name[j:i]`
 - [i] selects the *i*-th bit of the vector
 - [j:i] selects the part of the vector between the *j*-th and the *i*-th bits (including the boundaries)

Verilog HDL – Operators

(Bitwise and logical operators)

- **Bitwise operators: ~ (NOT), & (AND), | (OR), ^ (XOR)**
 - Number of operands: NOT: 1 / AND, OR, XOR: 2
 - If the operands are vectors, the operation is executed bitwise
 - **If one operand is shorter than the other, the shorter operand is bit-extended with zeroes to match size**
 - If this is not desired, use the concatenation operator to match size
 - Examples:
 - $4'b0100 \mid 4'b1001 = 4'b1101$
 - $\sim 8'b0110_1100 = 8'b1001_0011$
- **Logical operators: ! (NOT), && (AND), || (OR)**
 - Number of operands: NOT: 1 / AND, OR: 2
 - Always yield a single-bit value: 0 or 1
 - Examples:
 - $4'b0000 \mid\mid 4'b0111 = 0 \mid\mid 1 = 1$
 - $4'b0000 \&\& 4'b0111 = 0 \&\& 1 = 0$
 - $!4'b0000 = !0 = 1$

Verilog HDL – Operators

(Bit reduction operators)

- **Bit reduction operators:
& (AND), ~& (NAND), | (OR), ~| (NOR), ^ (XOR), ~^ (NXOR)**
 - Number of operands: 1
 - Perform a bitwise operation on a single vector
 - Yield a 1-bit result: 0 or 1
 - Examples:
 - $\&4'b0101 = 0 \& 1 \& 0 \& 1 = 0$
 - $|4'b0101 = 0 \mid 1 \mid 0 \mid 1 = 1$
- **Important use cases:**
 - Testing for 0 value: NOR connection of the bits

```
wire [11:0] data;
wire all_zeros = ~|data;
```
 - Testing for 2^N-1 value (all 1s): AND connection of the bits

```
wire all_ones = &data;
```
 - Indicating the final state (terminal count) of the counter:

```
wire tc = (dir) ? (&cnt) : (~|cnt);
```

Verilog HDL – Operators

(Shift operators)

- **Logical shift operators: << (left), >> (right)**
 - Number of operands: 2
 - Examples:
 - `8'b0011_1100 >> 2 = 8'b0000_1111`
 - `8'b0011_1100 << 2 = 8'b1111_0000`
- **Arithmetic shift operators: <<< (left), >>> (right)**
 - Number of operands: 2
 - The arithmetic left shift is the same as the logical left shift
 - In case of unsigned operands, the arithmetic right shift is the same as the logical right shift
 - In case of signed operand, the arithmetic right shift replicates the sign bit to fill in the vacant positions (sign extension)
 - Examples:
 - `8'b1001_1100 >>> 2 = 8'b0010_0111`
 - `8'sb1001_1100 >>> 2 = 8'b1110_0111`

Verilog HDL – Operators

(Relational operators)

- **Relational operators:**
== (equality), != (inequality), < (less than), > (greater than), <= (less than or equal), >= (greater than or equal)
 - Number of operands: 2
 - The result is always a single-bit value: 0 or 1
 - The equality and inequality relations are mapped to gate based logic and usually, the less than and greater than relations are mapped to an arithmetic function
 - **The smaller signed operand is sign extended to the larger operand to match the size**
 - Example:
 - `(4'b1011 < 4'b0111) = 0`
 - `(4'b1011 != 4'b0111) = 1`

Verilog HDL - Assignments

- **Specifying the logic connection in case of *wire* signals:**
`assign <wire_signal> = <expression>;`
 - The value of the left *wire_signal* is determined in every moment by the right *expression* (combinational logic)
 - Example:

```
wire [15:0] a, b, c;  
assign c = a & b;
```
 - The logic connection can be specified at the declaration:

```
wire [15:0] a, b;  
wire [15:0] c = a & b;
```
- **Assigning a value to a *reg* type signal can be done in the *always* blocks using the blocking (=) or non-blocking (<=) assignment operators**

Verilog HDL – Assignments

(Interpretation of the always block by the simulator/verilog parser)

- ***Always* block:**
**`always @(sensitivity list)
assignments`**
 - The sensitivity list determines the events when the assignments are evaluated:
 - **`always @(a, b, c)`**: the assignments are evaluated when the value of the **a**, **b** or **c** input signals is changed
 - **`always @(*)`**: the assignments are evaluated when one of the always block input signals is changed
 - **`always @(posedge clk)`**: the assignments are evaluated at the rising edge of the **clk** signal and the output is changed only this time
 - **`always @(negedge clk, posedge rst)`**: the assignments are evaluated at the falling edge of **clk** or when the **rst** signal is set to 1

Verilog HDL – Assignments

(Interpretation of the always block by the synthesis tool)

- **Always block:**

```
always @(sensitivity list)
    assignments
```

– The sensitivity list determines what kind of logic element is used for implementing the behavioral description:

- **always @(a, b, c):** the combinational function of the *a*, *b* and *c* input signals is specified
- **always @(*):** like the previous one, the value of the output is changed when an input is changed (combinational logic)
- **always @(posedge clk):** we want to use a rising clock edge sensitive flip-flop or register elements, the inputs are sampled and the outputs are changed only this time
- **always @(negedge clk, posedge rst):** like the previous one, the operation is controlled by the falling edge of the *clk* but there is also a *rst* signal which becomes effective if it is set to 1

Verilog HDL – Assignments

(Using the always block for synthesis)

- **Always block:**

- In case of synthesis, value can be assigned to a *reg* type signal only one place in only one always block
- The *if...else*, the *case* and the *for* instructions can be used only in always blocks
- Multiple statements inside the always *block* must be grouped using *begin* and *end* keywords
- Example:

```
wire a;
reg b, c, d;

always @(a, b)
begin
    c <= a & b;
    d <= a | b;
end
//C is an AND gate

//Prohibited 2nd assignment
always @(*)
begin
    c <= b ^ d;
end
//Here, C is an XOR gate

//Peer descriptions. Which one takes effect?
```

Verilog HDL – Assignments

(Always block – Non-blocking assignment)

Interpreting the non-blocking assignment

- Until the next blocking assignment, the non-blocking assignments that belong to the same event evaluate their right side in parallel, then these values are assigned to the left side at the same time
- This is the operation model of the clock edge controlled storage elements, therefore a storage element is built into the sequential circuit for every non-blocking assignment
- If it is possible, always use non-blocking assignments because it is closer to the hardware view and it can cause less errors


```
module M(clk, a, b, c, y);
```

```
input wire clk, a, b, c;  
output reg y;
```

```
reg x;
```

```
always @(posedge clk)  
begin  
  x <= a | b;  
  y <= x & c;  
end
```

```
endmodule
```

 

BME-MIT

30

FPGA labor

Verilog HDL – Assignments

(Always block – Blocking assignment)

Interpreting the blocking assignment

- The blocking assignment operator (=) is the usual assignment, they are executed sequentially in order they are written and the new value of the left side variable is used for evaluating the next expressions
- Therefore, if the result of a blocking assignment is used in the same *always* block (in the same clock cycle) later, no storage element is built into the sequential circuit for the later assignment (see the signal x in the example)


```
module M(clk, a, b, c, y);
```

```
input wire clk, a, b, c;  
output reg y;
```

```
reg x;
```

```
always @(posedge clk)  
begin  
  x = a | b;  
  y = x & c;  
end
```

```
endmodule
```

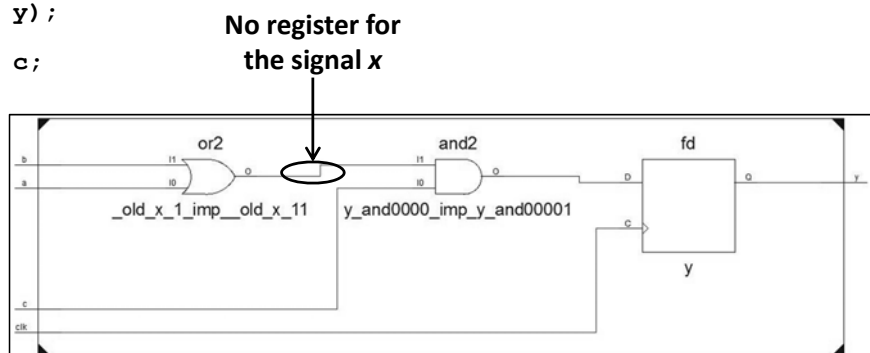

BME-MIT

31

FPGA labor


Verilog HDL – Assignments

(Example)

 
Example: 3-bit shift register

- Look at the difference between the two solution
- Only using the non-blocking assignments results in the correct circuit

```
module shr_3bit(clk, si, q0, q1, q2);  
input wire clk, si;  
output reg q0, q1, q2;  
  
always @(posedge clk)  
begin  
    q0 = si;    // q0 ← si  
    q1 = q0;    // q1 ← q0 ← si  
    q2 = q1;    // q2 ← q1 ← q0 ← si  
end  
  
endmodule
```


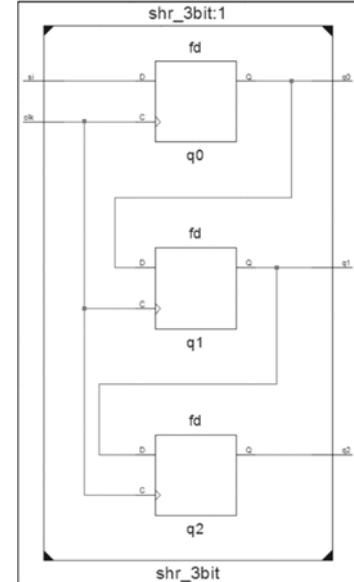
```
module shr_3bit(clk, si, q0, q1, q2);  
input wire clk, si;  
output reg q0, q1, q2;  
  
always @(posedge clk)  
begin  
    q0 <= si; // new q0 ← actual si  
    q1 <= q0; // new q1 ← actual q0  
    q2 <= q1; // new q2 ← actual q1  
end  
  
endmodule
```



Verilog HDL – IF instruction

- **Syntax of the *if* instruction:**

```
if (expression) instruction1; [else instruction2;]
```

– First, the given **expression** is evaluated:

- If its value is not 0: **instruction1** is executed
- If its value is 0: **instruction2** is executed

– The **else** path is optional, it can be omitted

– Multiple statements inside the **if** instruction must be grouped using **begin** and **end** keywords

– The nested **if** instructions result in hierarchical, sequential evaluation → PRIORITY!!!!

- This is the typical implementation of the control signals of the functional elements

Verilog HDL – CASE instruction

- **Syntax of the *case* instruction:**

```
case (expression)
  alternative1: instruction1;
  alternative2: instruction2;
  ⋮
  [default      : default_instruction;]
endcase
```

- The value of the ***expression*** is compared with the ***alternatives*** in order they are listed (their order may mean priority!)
- The instruction belonging to the first matching alternative is executed
- If there is no matching alternative, the ***default_instruction*** is executed written after the ***default*** keyword (optional)
- Multiple instructions must be grouped using ***begin*** and ***end*** keywords
- In case of the ***casex*** instruction, the alternatives can contain ***x*** (don't care) value also, this may result in simpler description

Verilog HDL – FOR instruction

- **Syntax of the *for* instruction:**

```
for ([initialization]; [condition]; [operation])
  instruction;
```

- **The operation of the for loop:**

1. The ***initialization part*** sets the initial value of the loop variable
2. The ***condition*** is evaluated: if it is false, the loop is terminated
3. The given ***instruction*** is executed
4. The given ***operation*** is executed, then go to step 2

- **Multiple instructions must be grouped using *begin* and *end* keywords and the *begin* keyword must be labelled with a unique label (*begin: label*)**

- **In vace of hardware implementation, the *for* structure inside the *always* block can be used in a static way only, for simplifying the description (for example: indexing or value checking)**

- The general ***for*** loop used in the programming languages can be replaced with controller and datapath in the hardware

- **The loop variable should be declared as *integer* type**



Verilog HDL – FOR instruction

- **First example: reversing the bit order**
 - The *for* loop is used for indexing
 - Without the loop, 32 assignments would be required
- **Second example: 4 x 8 bit register file**
 - The *for* loop is used for indexing and checking equality
 - Without the loop, 4 conditional assignments would be required

```
module BitReverse(din, dout);  
    input wire [31:0] din;  
    output reg [31:0] dout;  
  
    integer i; //Loop variable  
  
    always @(*)  
        for (i=0; i<32; i=i+1)  
            begin: reverse loop  
                dout[i] <= din[31-i];  
            end  
  
endmodule  
  
module RegFile(clk, addr, we, din, r0, r1, r2, r3);  
    input wire clk, we;  
    input wire [1:0] addr;  
    input wire [7:0] din;  
    output wire [7:0] r0, r1, r2, r3;  
  
    reg [7:0] r [3:0]; //4 x 8 bit reg. file  
    integer i; //Loop variable  
  
    always @(posedge clk)  
        for (i=0; i<4; i=i+1)  
            if (we && (addr == i))  
                r[i] <= din;  
  
    assign {r3,r2,r1,r0} = {r[3],r[2],r[1],r[0]};  
  
endmodule
```

Verilog HDL - Examples

  - **Example: 1-bit 2-to-1 multiplexer**
 - Selects one from several inputs and its value is routed to the output
 - Ports:
 - Data inputs: IN0, IN1
 - Input select signal: SEL
 - Data output: OUT
 - Operation:
 - If SEL=0: IN0 is routed to the output
 - If SEL=1: IN1 is routed to the output
 - The multiplexer is a combinational logic



```
wire in0, in1, sel, out;  
assign out = (in0 & ~sel) | (in1 & sel);
```

Verilog HDL - Examples

- **Example: 8-bit 2-to-1 multiplexer**

- 1st solution: using the bitwise logic operators
- *In this case, using the bitwise logic operators is not the best solution, because the described function cannot be determined easily from the source code!*

```
module Mux_2to1_8bit(  
    input wire [7:0] in0,  
    input wire [7:0] in1,  
    input wire      sel,  
    output wire [7:0] out  
);  
  
    assign out = (in0 & {8{~sel}}) | (in1 & {8{sel}});  
  
endmodule
```

Verilog HDL - Examples

- **Example: 8-bit 2-to-1 multiplexer**

- 2nd solution: using the conditional operator

```
module Mux_2to1_8bit(  
    input wire [7:0] in0,  
    input wire [7:0] in1,  
    input wire      sel,  
    output wire [7:0] out  
);  
  
    assign out = (sel) ? in1 : in0;  
  
endmodule
```

Verilog HDL - Examples

- **Example: 8-bit 2-to-1 multiplexer**
 - 3rd solution: using the IF instruction

```
module Mux_2to1_8bit(  
    input  wire [7:0] in0,  
    input  wire [7:0] in1,  
    input  wire      sel,  
    output reg [7:0] out  
);  
  
always @(*)          //or always @(in0, in1, sel)  
    if (sel == 0)  
        out <= in0;  
    else  
        out <= in1;  
  
endmodule
```

Verilog HDL - Examples

- **Example: 8-bit 2-to-1 multiplexer**
 - 4th solution: using the CASE instruction

```
module Mux_2to1_8bit(  
    input  wire [7:0] in0,  
    input  wire [7:0] in1,  
    input  wire      sel,  
    output reg [7:0] out  
);  
  
always @(*)          //or always @(in0, in1, sel)  
    case (sel)  
        1'b0: out <= in0;  
        1'b1: out <= in1;  
    endcase  
  
endmodule
```

Verilog HDL - Examples

- **Example: 8-bit 4-to-1 multiplexer**

```
module Mux_4to1_8bit(in0, in1, in2, in3, sel, out);  
  
    input  wire [7:0] in0, in1, in2, in3;  
    input  wire [1:0] sel;  
    output reg  [7:0] out;  
  
    always @(*) //or always @(in0, in1, in2, in3, sel)  
        case (sel)  
            2'b00: out <= in0;  
            2'b01: out <= in1;  
            2'b10: out <= in2;  
            2'b11: out <= in3;  
        endcase  
  
endmodule
```


Implementing combinational logic

- **Wire** type signals can implement combinational logic only
- **Reg** type signals can implement both combinational and sequential logic
- When *combinational logic* is implemented using *reg* type signals:
 - The assignment(s) must be evaluated when at least one input signal is changed:
 - The sensitivity list of the always block has to contain all input signals of the combinational logic or a * character
 - *negedge* or *posedge* must not be in the sensitivity list

Implementing combinational logic

- When *combinational logic* is implemented using *reg* type signals:
 - The *always* blocks must contain only **fully specified if** and **case** instructions
 - If the *if* and *case* instructions are not fully specified, **latches** will be inserted (asynchronous flip-flop)
 - The state of the *reg* type signal is preserved by the *latch* when no assignment is made for the given condition(s)
 
```
reg reg_signal;  
  
always @(*)  
  if (sel)  
    reg_signal <= in0;
```




BME-MIT

FPGA labor

Implementing combinational logic

- Latches are undesired, they implement asynchronous sequential logic and not combinational logic
- When the *if* and *case* instructions are fully specified (*if*: all *else* paths are present, *case*: all possible alternatives are listed or the *default* keyword is used):
 - The result will be combinational logic (example: MUX)
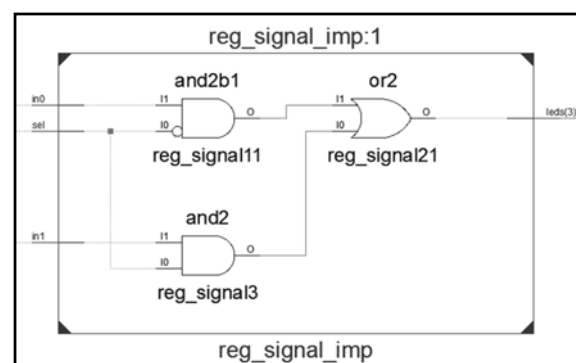
```
reg reg_signal;  
  
always @(*)  
  if (sel)  
    reg_signal <= in1;  
  else  
    reg_signal <= in0;
```




BME-MIT

FPGA labor

Implementing sequential logic

- Only *reg* type signals can implement sequential logic:
 - Asynchronous: latches (**must be avoided!**)
 - Synchronous: flip-flops, registers
- Registers change their state at the rising or falling edge of the clock signal
 - The sensitivity list of the *always* block must contain the clock signal preceded by the *posedge* (rising edge) or the *negedge* (falling edge) keyword
 - The clock cannot be used explicitly in the assignment expressions inside the *always* block
- The *if* and *case* instructions can be not fully specified
 - If so, the clock enable input of the flip-flops is used to prevent the state change when there is no assignment

Implementing sequential logic

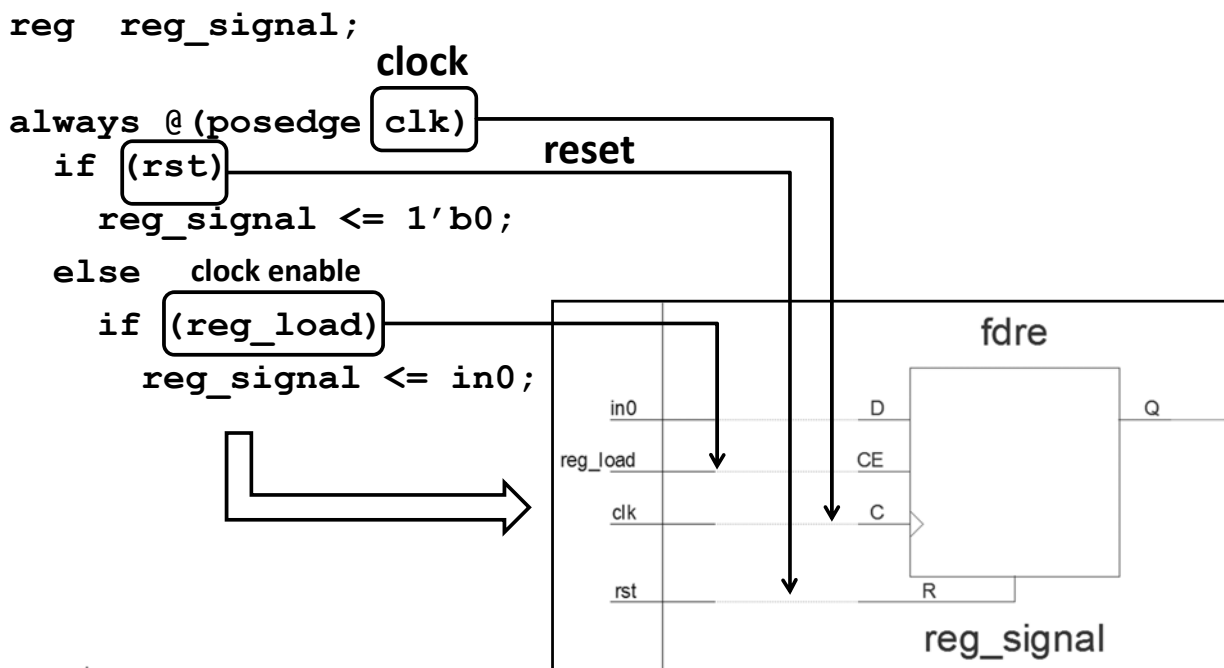

Synchronous/asynchronous control signals

- **Synchronous control signals:**

- Have effect only at the rising or falling clock edge
- The sensitivity list doesn't contain the synchronous control signals

```
//Active-high synchronous reset
always @(posedge clk)
  if (rst)
    some_reg <= 1'b0;
  else
    some_reg <= data_in;
```

```
//Active-low synchronous reset
always @(posedge clk)
  if (rst == 0)
    some_reg <= 1'b0;
  else
    some_reg <= data_in
```

- **Asynchronous control signals**



- Have immediate effect
- The sensitivity list **must** contain the asynchronous control signals preceded with the **posedge** or the **negedge** keyword

```
//Active-high asynchronous reset
always @(posedge clk, posedge rst)
  if (rst)
    some_reg <= 1'b0;
  else
    some_reg <= data_in;
```

```
//Active-low asynchronous reset
always @(posedge clk, negedge rst)
  if (rst == 0)
    some_reg <= 1'b0;
  else
    some_reg <= data_in
```

Finite state machines (FSMs)

- **Local parameters can be used to define the states**
- **A register is required to store the current state**
- **The *case* instruction can be used to select the current state**
 - In each alternative, the **if** or **case** instructions can be used to check the value of the inputs and execute the proper state transition
- **Example: traffic light controller**
 - 4 states: red, red-yellow, green, yellow
 - An external timer generates the 1 clock cycle long enable signal

 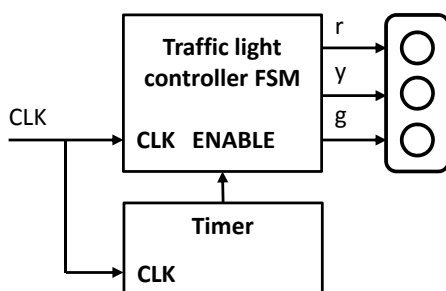

Finite state machines (FSMs)

First implementation:

- The state register and the next state logic are in different always blocks
- User state encoding (the synthesis tool can optimize it)

```
localparam STATE_R = 2'd0;
localparam STATE_RY = 2'd1;
localparam STATE_G = 2'd2;
localparam STATE_Y = 2'd3;

reg [1:0] state;
reg [1:0] next_state;

//State register (sequential logic)
always @(posedge clk)
  if (rst)
    state <= STATE_R;
  else
    if (enable)
      state <= next_state;

//Next state logic (combinational logic)
always @(*)
  case (state)
    STATE_R : next_state <= STATE_RY;
    STATE_RY : next_state <= STATE_G;
    STATE_G : next_state <= STATE_Y;
    STATE_Y : next_state <= STATE_R;
  endcase

//Driving the outputs (combinational logic)
assign r = (state == STATE_R) |
           (state == STATE_RY);
assign y = (state == STATE_Y) |
           (state == STATE_RY);
assign g = (state == STATE_G);
```

Finite state machines (FSMs)

Second implementation:

- The state register and the next state logic are in the same always block
- User state encoding (the synthesis tool can optimize it)

```
localparam STATE_R = 2'd0;
localparam STATE_RY = 2'd1;
localparam STATE_G = 2'd2;
localparam STATE_Y = 2'd3;

reg [1:0] state;

//State register and the next state logic
always @(posedge clk)
begin
  if (rst)
    state <= STATE_R;
  else
    case (state)
      STATE_R : if (enable)
                  state <= STATE_RY;
                else
                  state <= STATE_R;
      STATE_RY : if (enable)
                  state <= STATE_G;
                else
                  state <= STATE_RY;
      STATE_G : if (enable)
                  state <= STATE_Y;
                else
                  state <= STATE_G;
      STATE_Y : if (enable)
                  state <= STATE_R;
                else
                  state <= STATE_Y;
    endcase
end

//Driving the outputs (combinational logic)
assign r = (state==STATE_R) | (state==STATE_RY);
assign y = (state==STATE_Y) | (state==STATE_RY);
assign g = (state==STATE_G);
```

Finite state machines (FSMs)

Third implementation:

- The state register and the next state logic are in different always blocks
- Output encoding: the *(* fsm_encoding = "user" *)* Xilinx-specific Verilog directive disables the state encoding optimization for the state register

```
localparam STATE_R = 3'b100;
localparam STATE_RY = 3'b110;
localparam STATE_G = 3'b001;
localparam STATE_Y = 3'b010;

(* fsm_encoding = "user" *)
reg [2:0] state;
reg [2:0] next_state;

//State register (sequential logic)
always @(posedge clk)
  if (rst)
    state <= STATE_R;
  else
    if (enable)
      state <= next_state;

//Next state logic (combinational logic)
always @(*)
  case (state)
    STATE_R : next_state <= STATE_RY;
    STATE_RY: next_state <= STATE_G;
    STATE_G : next_state <= STATE_Y;
    STATE_Y : next_state <= STATE_R;
  endcase

//Driving the outputs
assign r = state[2];
assign y = state[1];
assign g = state[0];
```

Datapath components

• Adder:

- Use the + (addition) operator
- The result can be 1 bit wider: the MSb is the output carry

```
wire [15:0] a, b, sum0, sum1, sum2;
wire      cin, cout;
assign sum0 = a + b;           //No cin and cout
assign sum1 = a + b + cin;     //Cin is used, no cout
assign {cout, sum2} = a + b + cin; //Cin and cout are used
```

• Subtractor:

- Use the – (subtraction) operator
- No borrow output: use 1 bit wider subtractor instead

```
wire [15:0] a, b, diff0, diff1;
wire      cin;
assign diff0 = a - b;           //No cin and cout
assign diff1 = a - b - cin;     //Cin is used, no cout
```

• Adder/subtractor:

- No input carry and output carry signals are available

```
wire [15:0] a, b;
wire [15:0] result;
wire      sel;
assign result = (sel) ? (a - b) : (a + b);
```

Datapath components

- **Shifter:**

- Use the {} (concatenation) operator instead of the shift operators
- The size of the constants must be specified

```
wire [7:0] din;  
wire [7:0] lshift = {din[6:0], 1'b0}; //Left shift  
wire [7:0] rshift = {1'b0, din[7:1]}; //Right shift
```

- **Comparator:**

- Use the relational operators

```
wire [15:0] a, b;  
wire      a_lt_b = (a < b); //Less than comparator  
wire      a_eq_b = (a == b); //Equality comparator  
wire      a_gt_b = (a > b); //Greater than comp.
```

- **Multiplier:**

- Use the * (multiply) operator
- The product size is the sum of the operand sizes
- Can be synthesized only, if the FPGA contains multipliers

```
wire [15:0] a, b;  
wire [31:0] prod = a * b;
```

Datapath components

- **Shift register (example):**

- Synchronous reset and load
- Bi-directional: can shift left and right

```
reg [7:0] shr;  
wire [7:0] din;  
wire      rst, load, dir, serin;  
  
always @(posedge clk)  
  if (rst)  
    shr <= 8'd0; //Reset  
  else  
    if (load)  
      shr <= din; //Load  
    else  
      if (dir)  
        shr <= {serin, shr[7:1]}; //Right shift  
      else  
        shr <= {shr[6:0], serin}; //Left shift
```

Datapath components

- Counter (example):
 - Synchronous reset and load
 - Bi-directional: can count up and down

```

reg [8:0] cnt;
wire [8:0] din;
wire      rst, load, dir;
wire      tc = (dir) ? (cnt==9'd0) : (cnt==9'd511);

always @(posedge clk)
    if (rst)
        cnt <= 9'd0; //Reset
    else
        if (load)
            cnt <= din; //Load
        else
            if (dir)
                cnt <= cnt - 9'd1; //Down count
            else
                cnt <= cnt + 9'd1; //Up count
    
```

Datapath components

(Priority of the control signals)

The value of the control inputs are examined in the order they are listed inside the *always* blocks (nested if instructions)

```

always @(posedge clk)
    if (rst)
        cnt <= 9'd0;
    else
        if (load)
            cnt <= data_in;
        else
            if (en)
                cnt <= cnt + 9'd1;

always @(posedge clk)
    if (rst)
        cnt <= 9'd0;
    else
        if (en)
            if (load)
                cnt <= data_in;
            else
                cnt <= cnt + 9'd1;

always @(posedge clk)
    if (en)
        if (clr)
            cnt <= 9'd0;
        else
            if (load)
                cnt <= data_in;
            else
                cnt <= cnt + 9'd1;
    
```

rst	load	en	Operation
1	x	x	Reset
0	1	x	Load
0	0	1	Up count
0	0	0	No change

rst	en	load	Operation
1	x	x	Reset
0	1	1	Load
0	1	0	Up count
0	0	x	No change

en	clr	load	Operation
0	x	x	No change
1	1	x	Clear
1	0	1	Load
1	0	0	Up count