

# Analog to Digital Converters


Lecturer: Krébesz, Tamás

# ADCs in general

- Mode of conversion
  - Direct: measured voltage is directly converted into a digital signal (feedbacked or not)
  - Indirect: measured voltage is converted into time, frequency, etc., first then into digital signal
- Mode of measurement
  - Instantaneous value: at difened time instants
  - Average value: at amplitude dependent time instant


# Successive approximating ADC

- An example for ADC with feedback

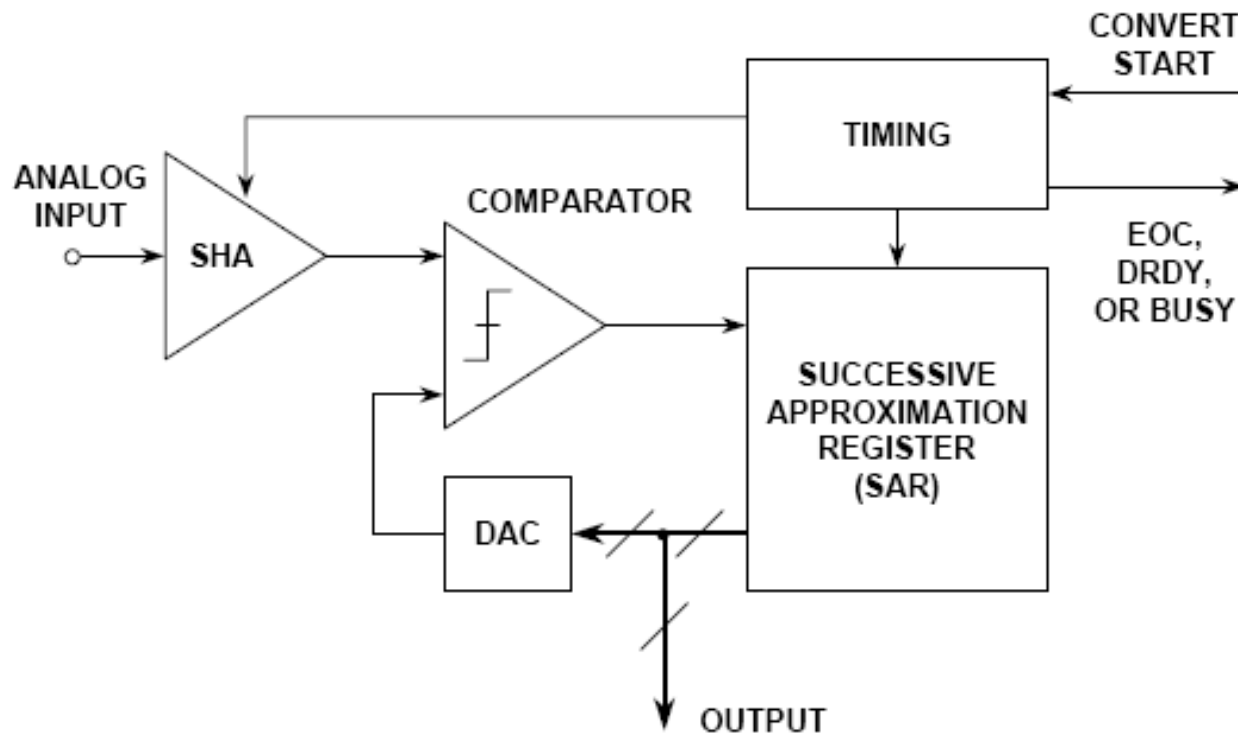


- Accuracy and linearity of the ADC is determined by the DAC unit
  - DAC remark:
    - in the past laser trimmed thin-film resistors were used->expensive and vulnerable
    - Today switched capacitors are used->great temperature tracking  $<1\text{ppm}/\text{Celsius}$

 
- Control solutions:
  - ADC with counter: very slow  
when level reached,  
it is grabbed



 
- Tracking counter: slow  
when level reached,  
it is tracked



- Block diagram:

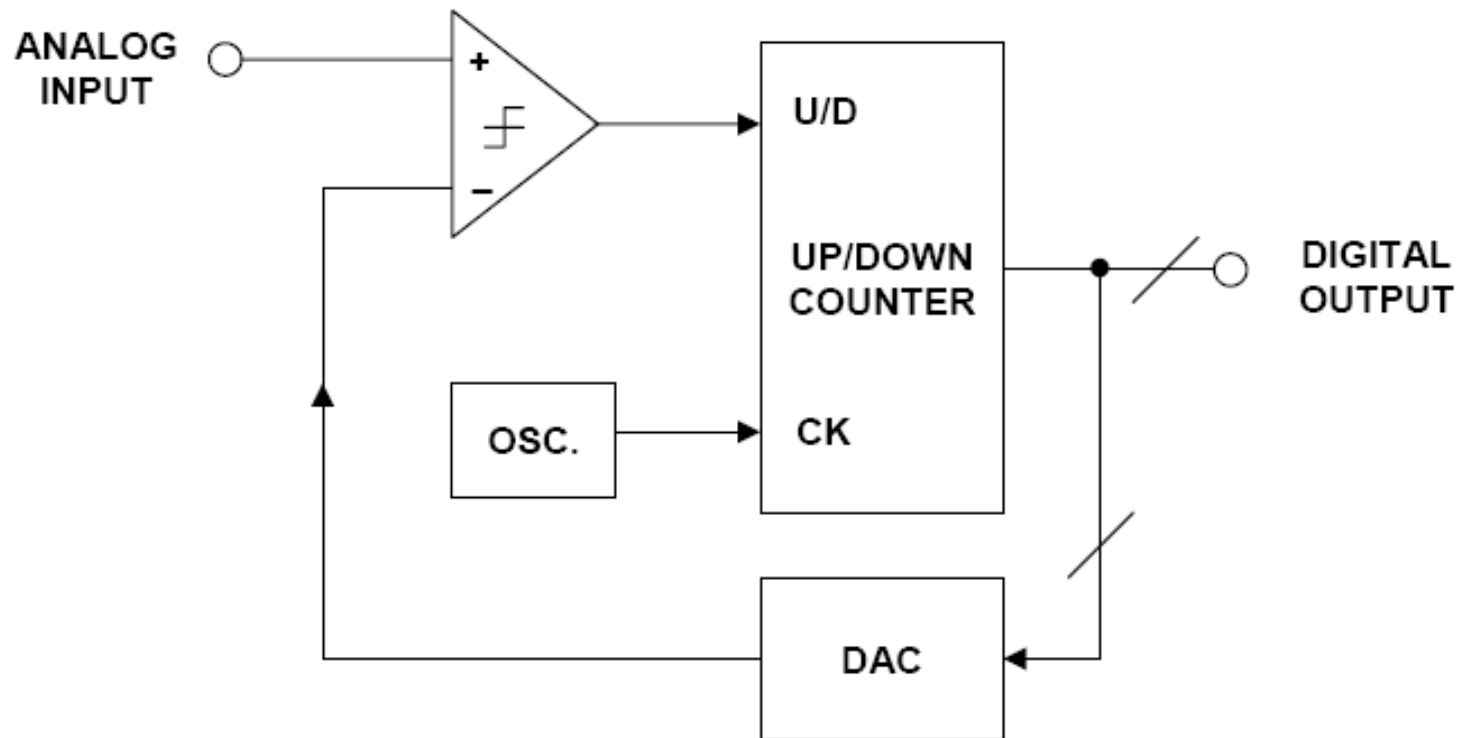


 - Successive approximating: most popular  
12-16 bits






# Switched capacitor DAC

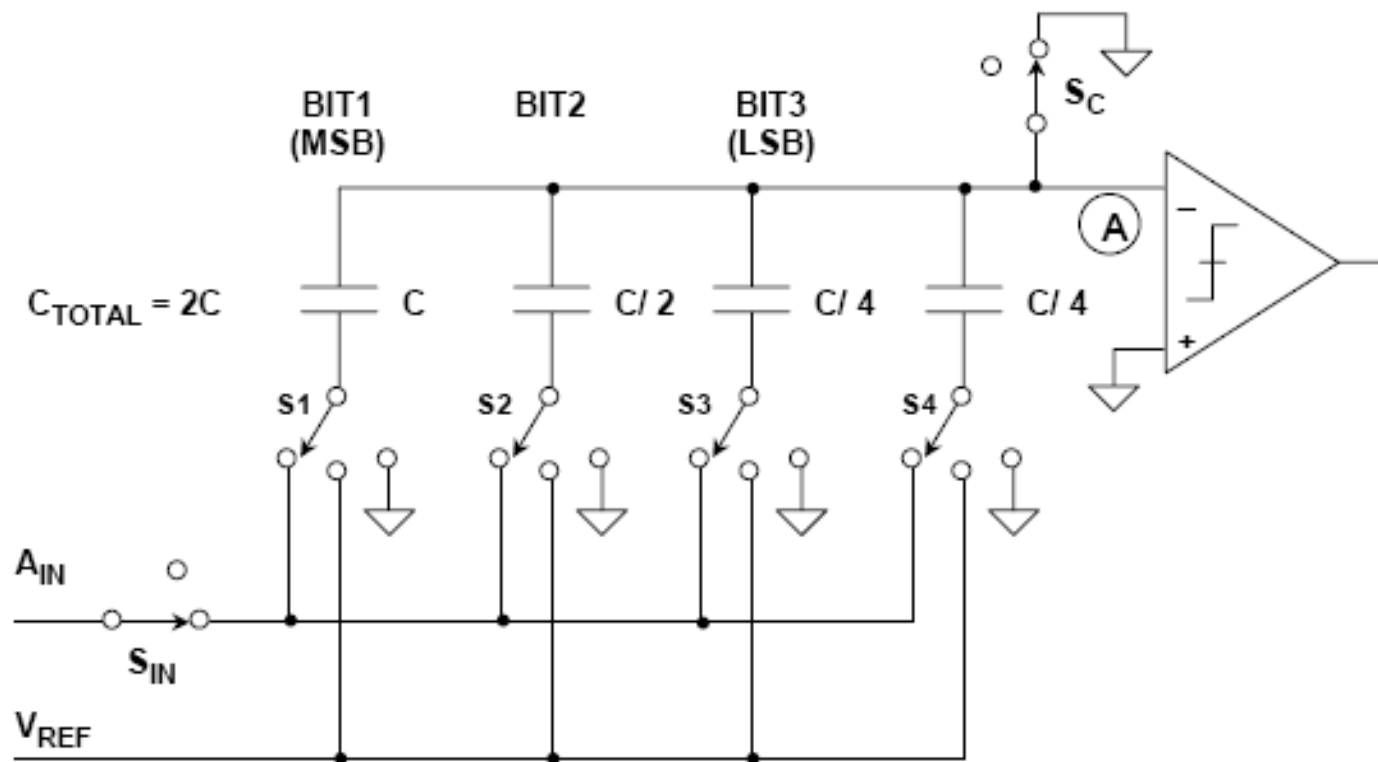

- $S_{in}$ ,  $S_C$  on: track or sample
- $S_{in}$  off: hold
- $S_C$  off: node A moves as the bit switches are manipulated
  
- $S_1 S_2 S_3 S_4$  grounded:  $V_A = -A_{in}$
- $S_1$  switched to  $V_{REF}$ :  $U_A = V_{REF}/2 - A_{in}$
  
- Note: sum of  $C=2C$  all the time ( $C=Q/V$ )


# Falsh converter (parallel ADC)

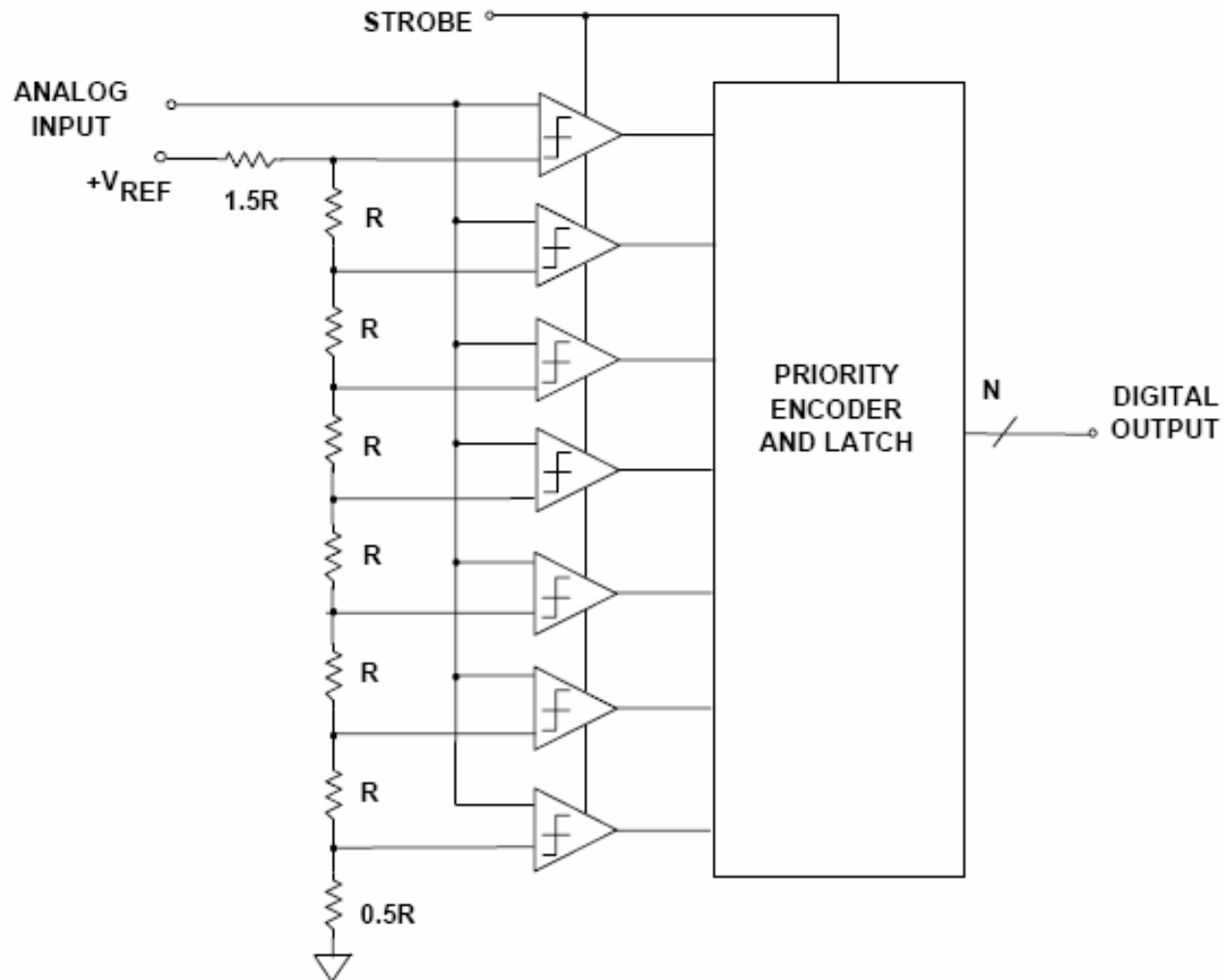

- For N bit resolution:
  - $2^N$  resistors and
  - $2^N-1$  capacitors are needed
- Features:
  - Too many resistors
  - Big Si area
  - Expensive
  - Laser trimming
  - High input capacitance
  - Poor linearity
  - Fast: 100MHz- $\rightarrow$ 10-12bit; 1-20GHz- $\rightarrow$ 8bit


# Subranging ADCs

- Flash advantages without disadvantages

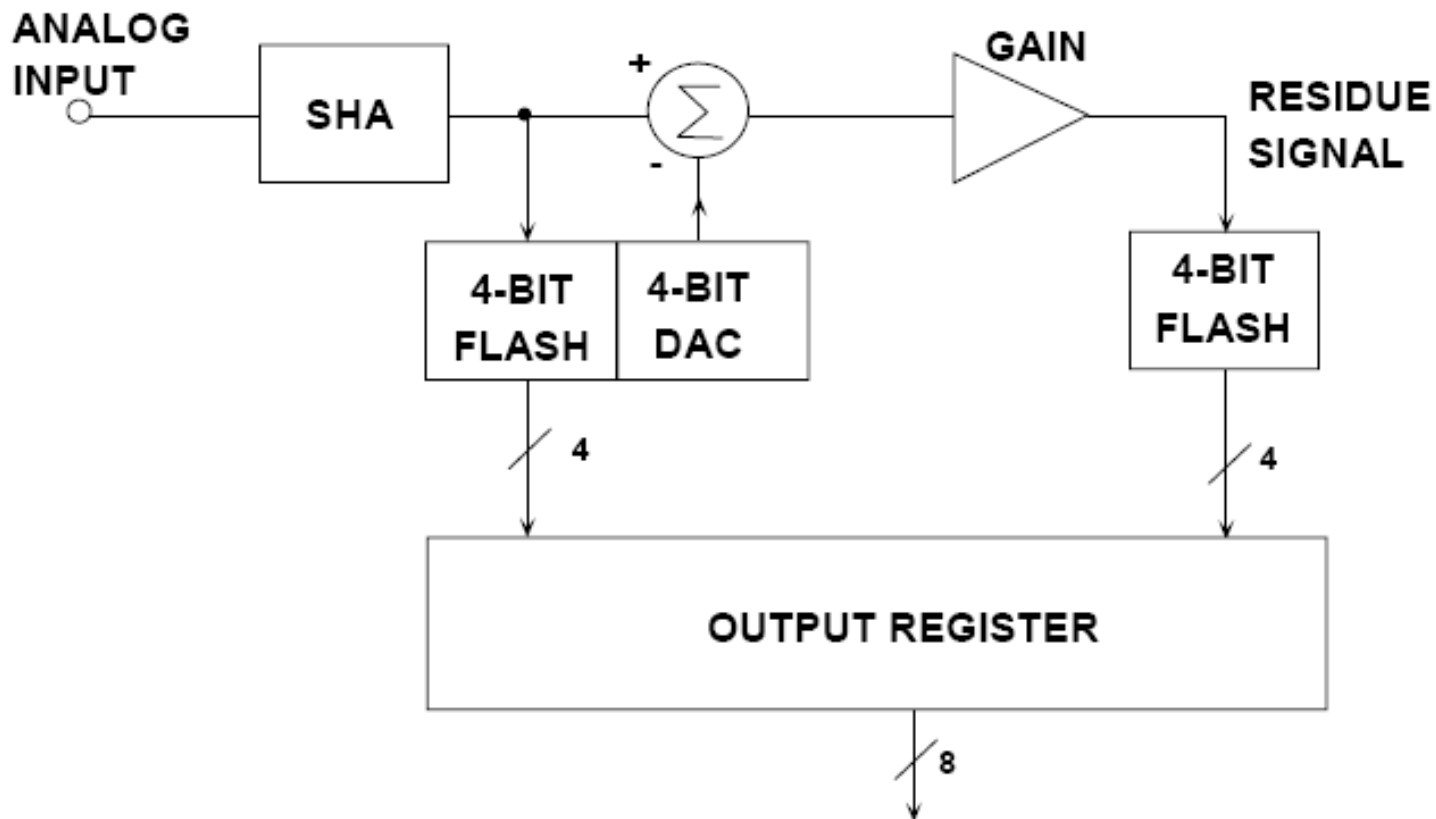


- Lower power consumption compared to Flash AD
- Smaller Si area
- Less resistors of one order is needed than in case of Flash AD
- $\frac{1}{2}$  speed reduction compared to Flash AD
- How to speed up: use pipeline technique

# Pipelined subranging ADC

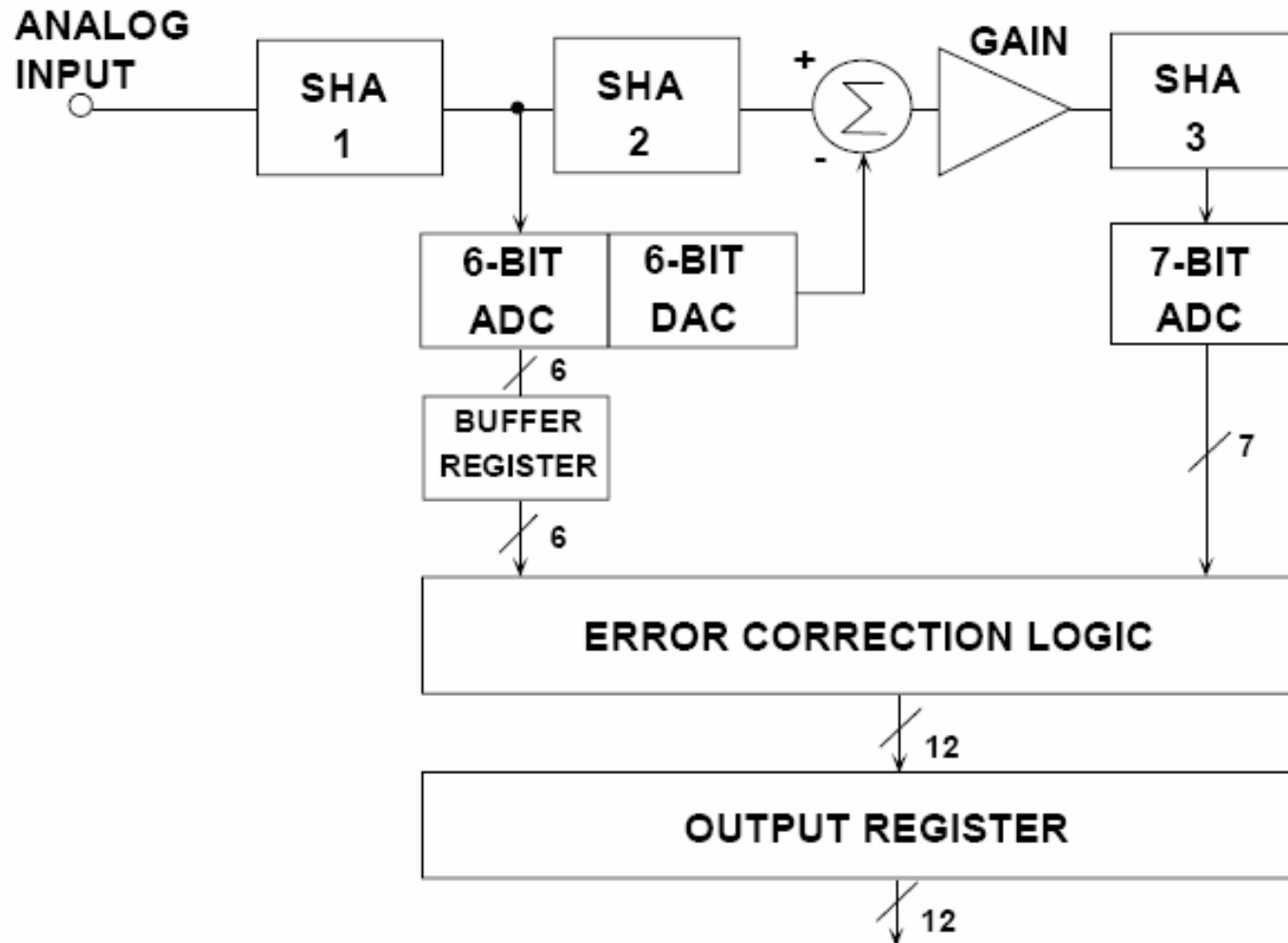


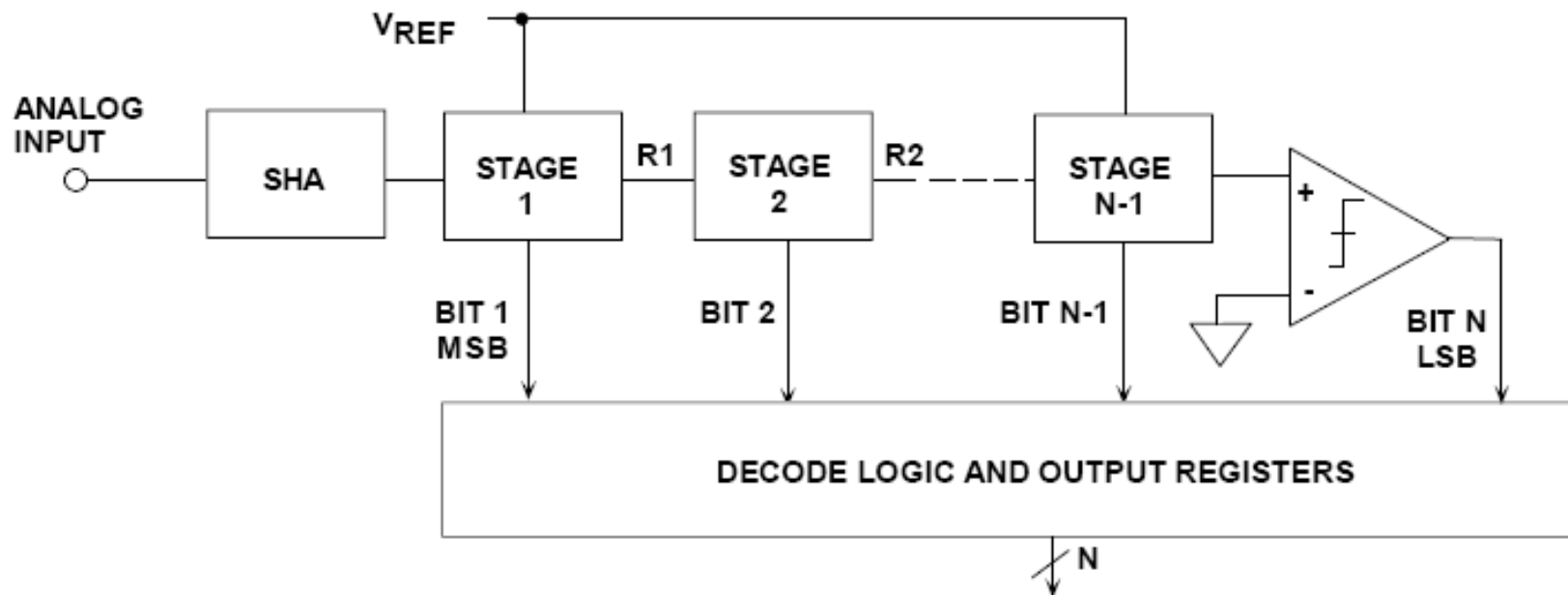
# Bit-per-stage ADC (serial, ripple)

- One form of multistage subranging ADC with one bit per stage and no error correction






- Simple stage of binary DAC

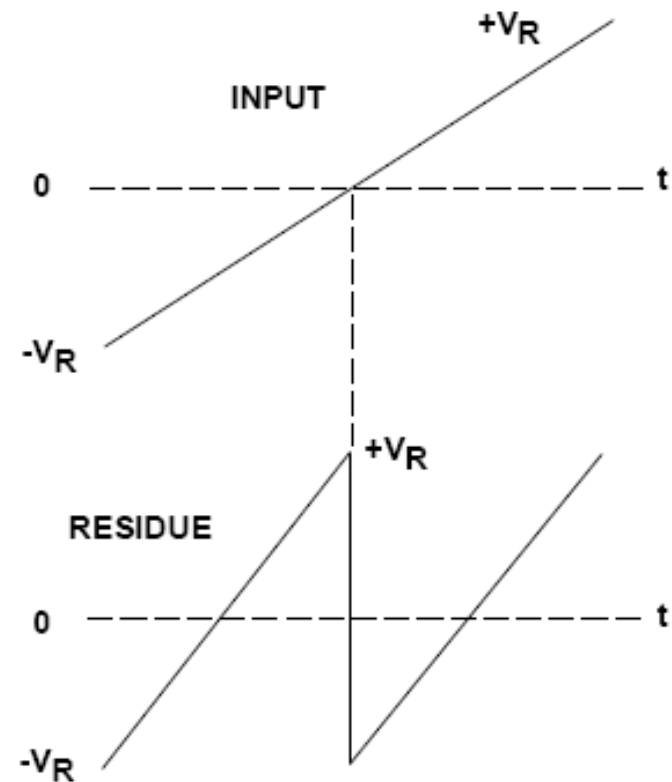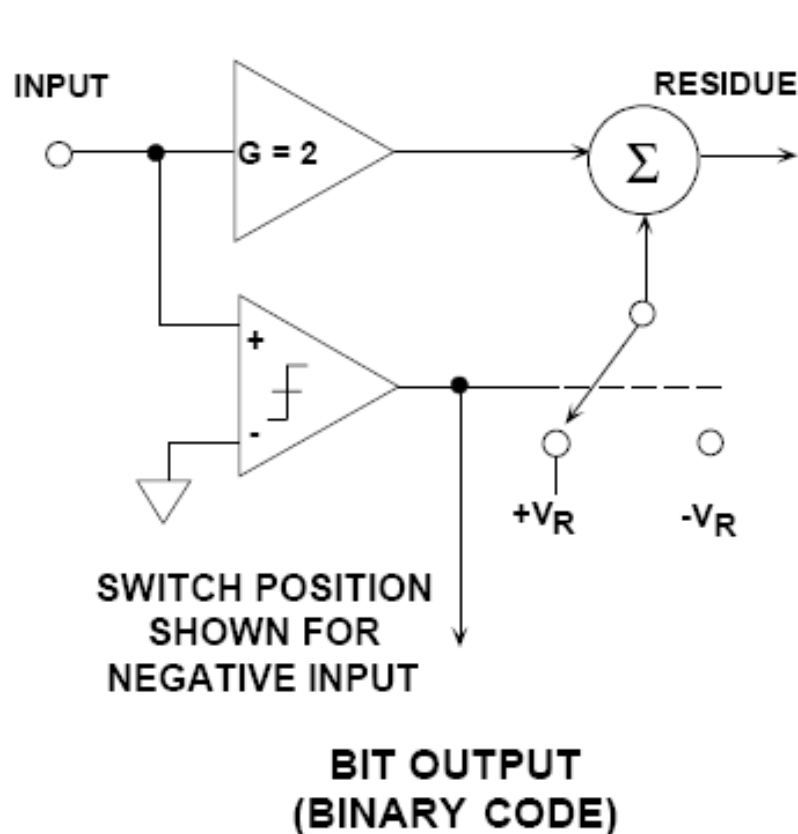


- 3-bit case:


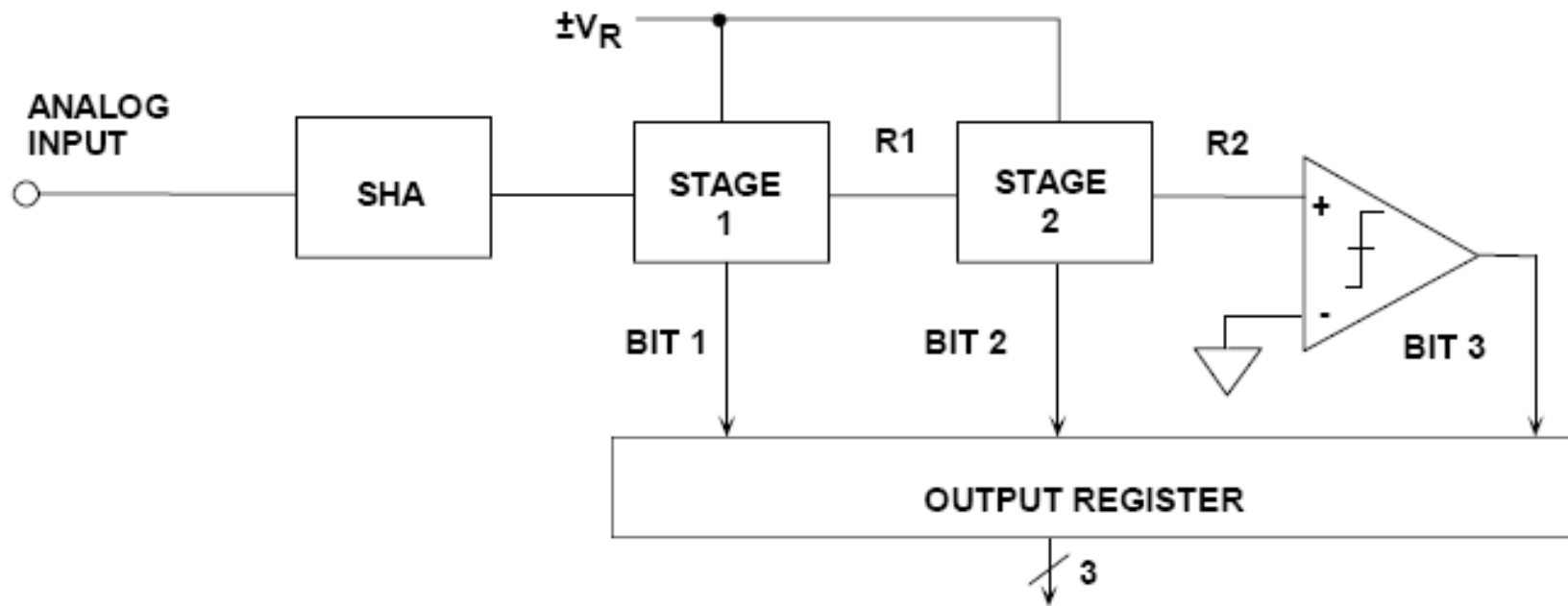

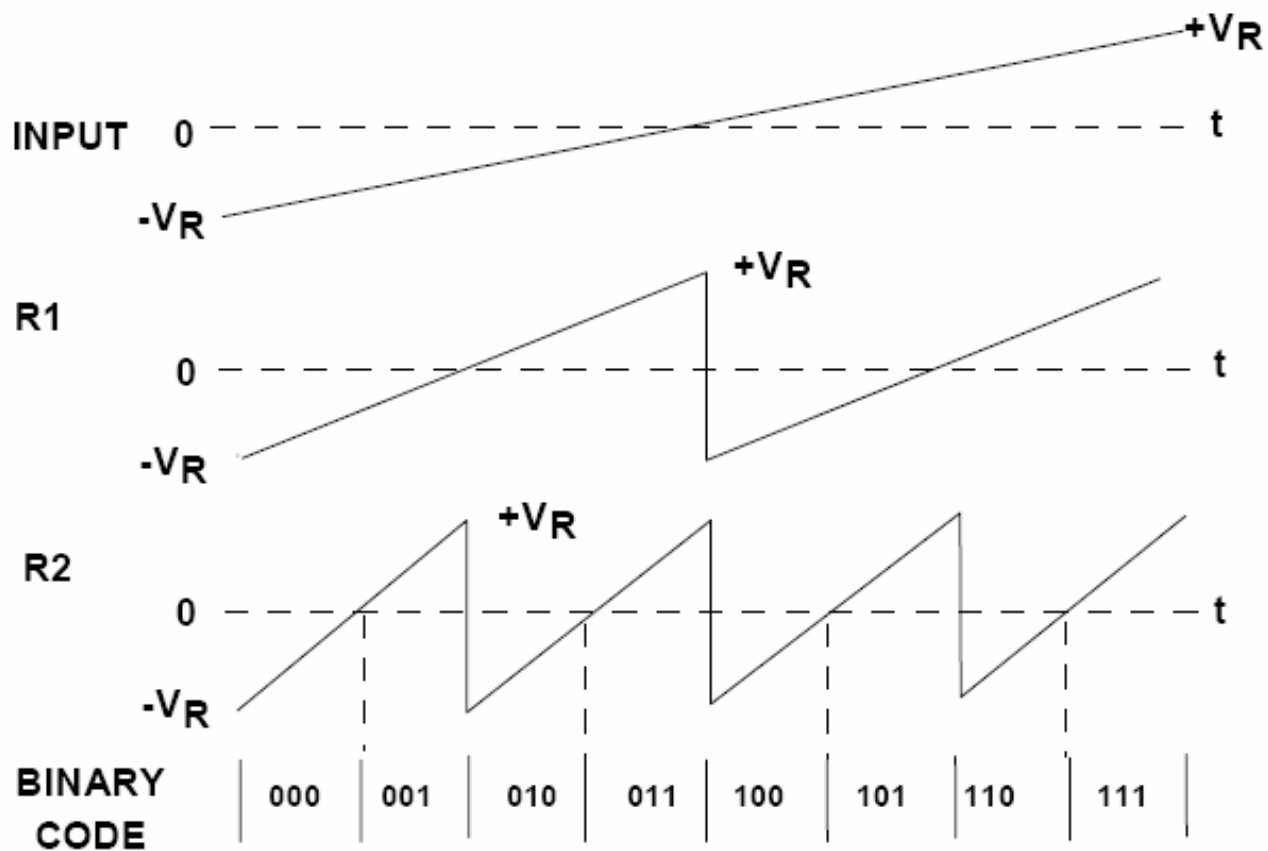
## – Input and residue waveforms


- See and understand using the simulation SW



 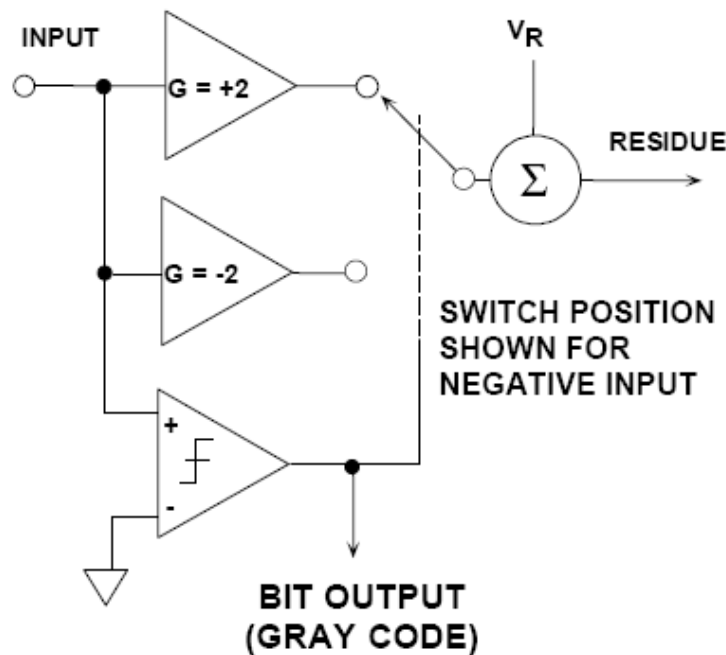
- Input is a ramp signal
- Long settling time because of discontinuities
- Note: R2 has 2x frequency compared to R1
- Magnitude amplifier is a better architecture



## – MagAmp block diagram

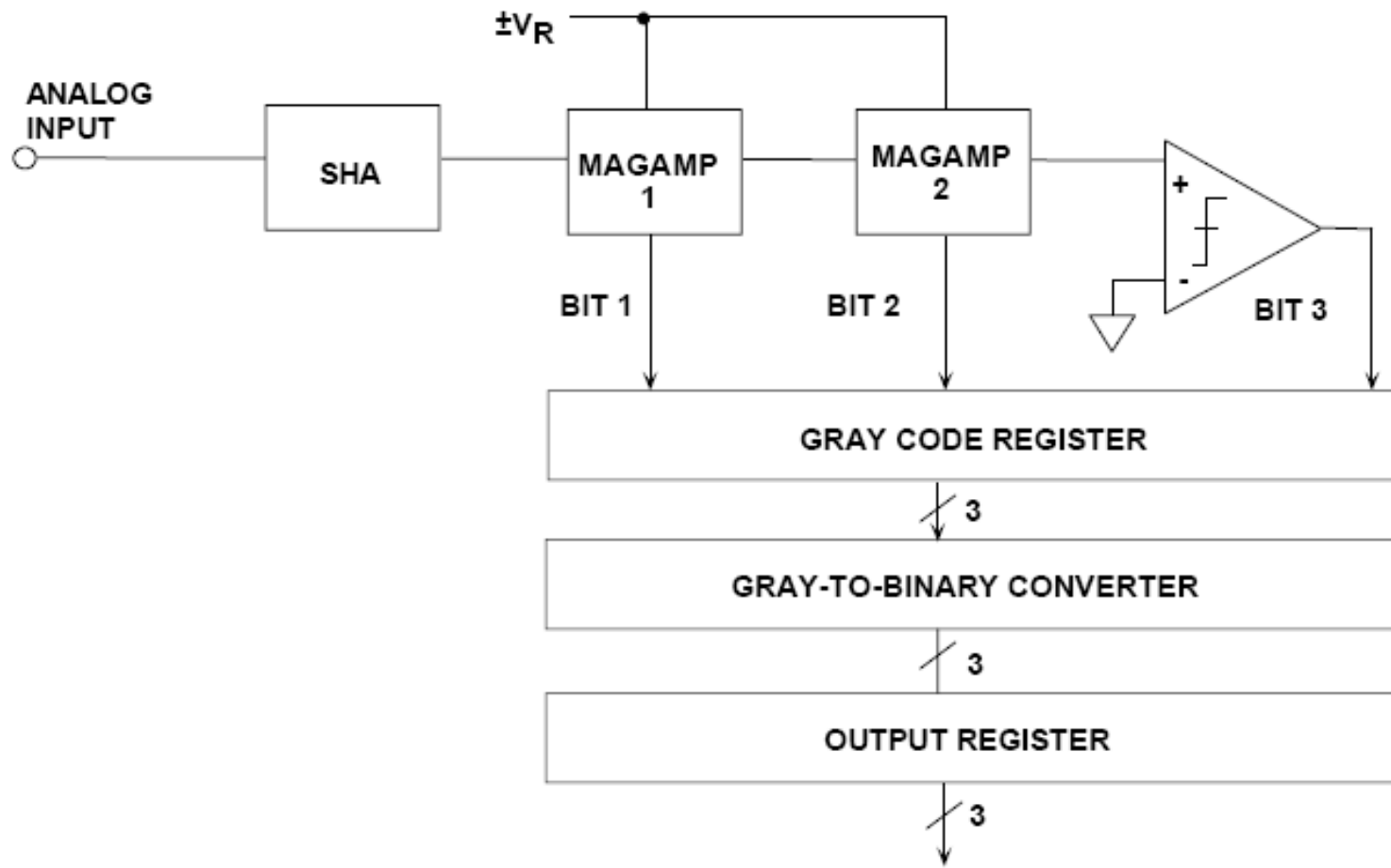


– Input and residue waveforms

 

- No discontinuity
  - Fast settling
  - High speed->competitor to Flash AD
- No need for laser trimmed resistances
- Note: outputs Gray-code that has to be converted into standard binary

# Dual architecture

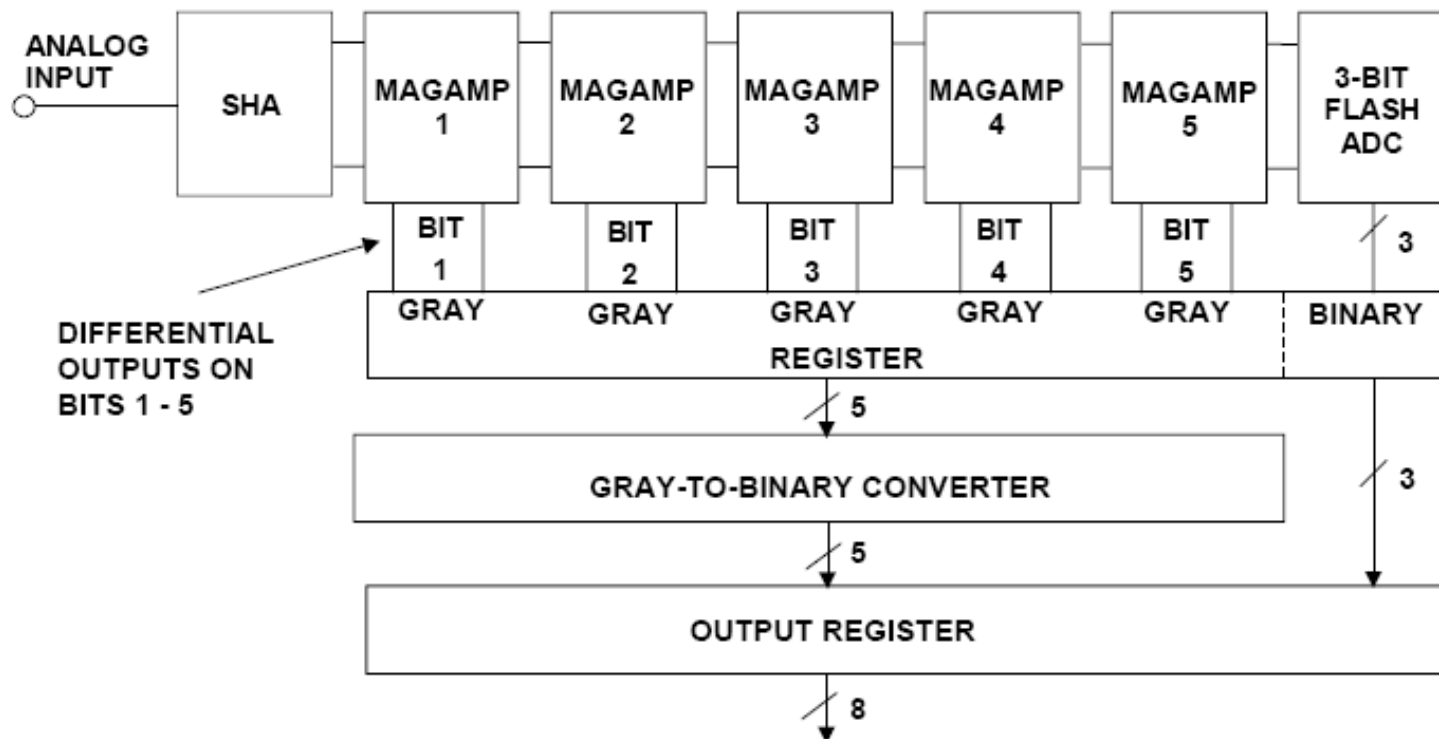
- Example: first 5 bits MagAmp last 3 bits Flash






- Resolution: 8-bit
- Speed: 100 MSPS

# Ramp Run-Up ADC

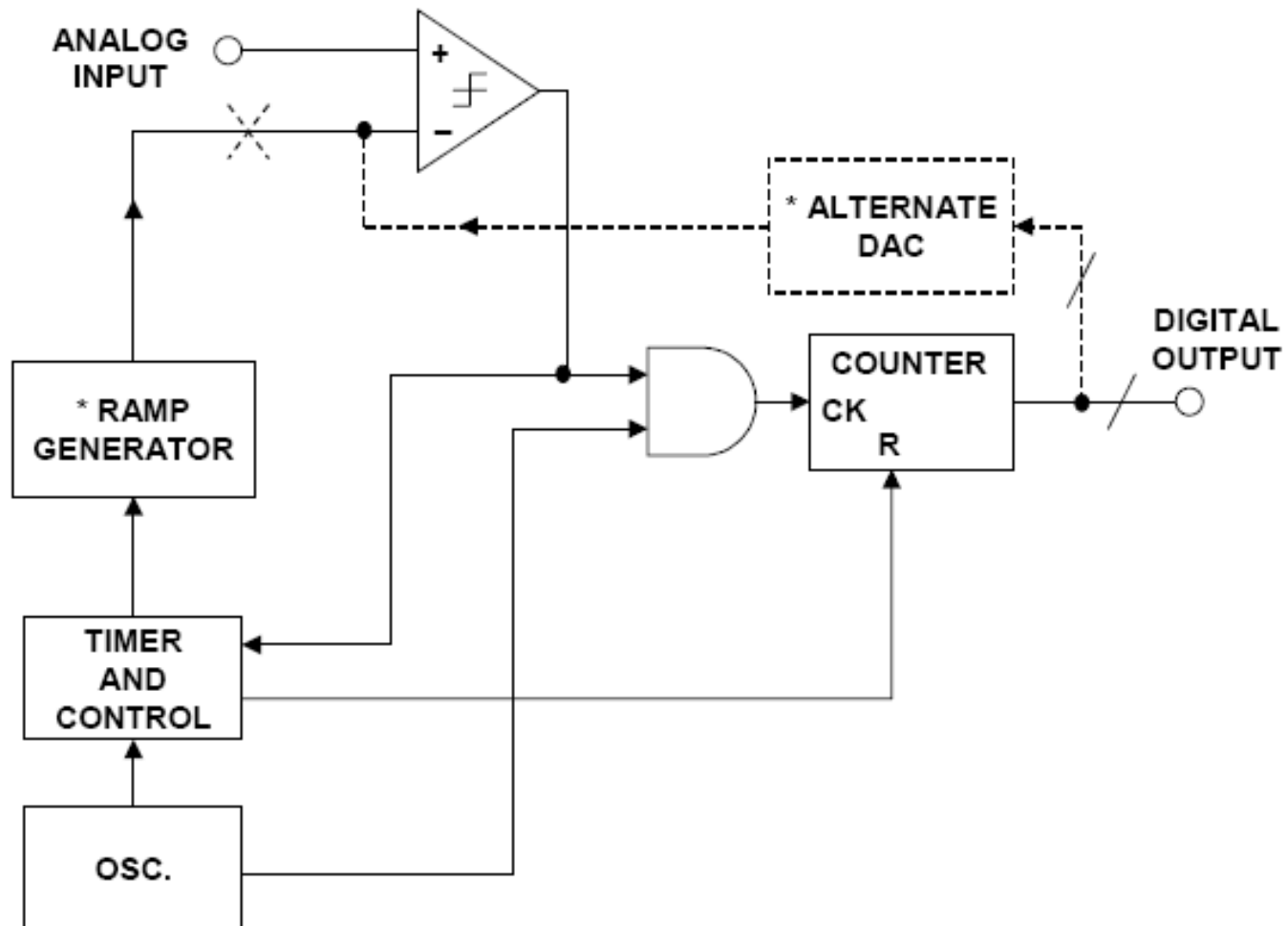


- Indirect measurement
  - Voltage->Time->Digital output
  - Instantaneous value
- Counter registers the oscillator ticks
- Sampling at the end of the conversion
- Amplitude dependent sampling
  - Should be eliminated: use charge run-down architecture

# Charge Run-Down ADC

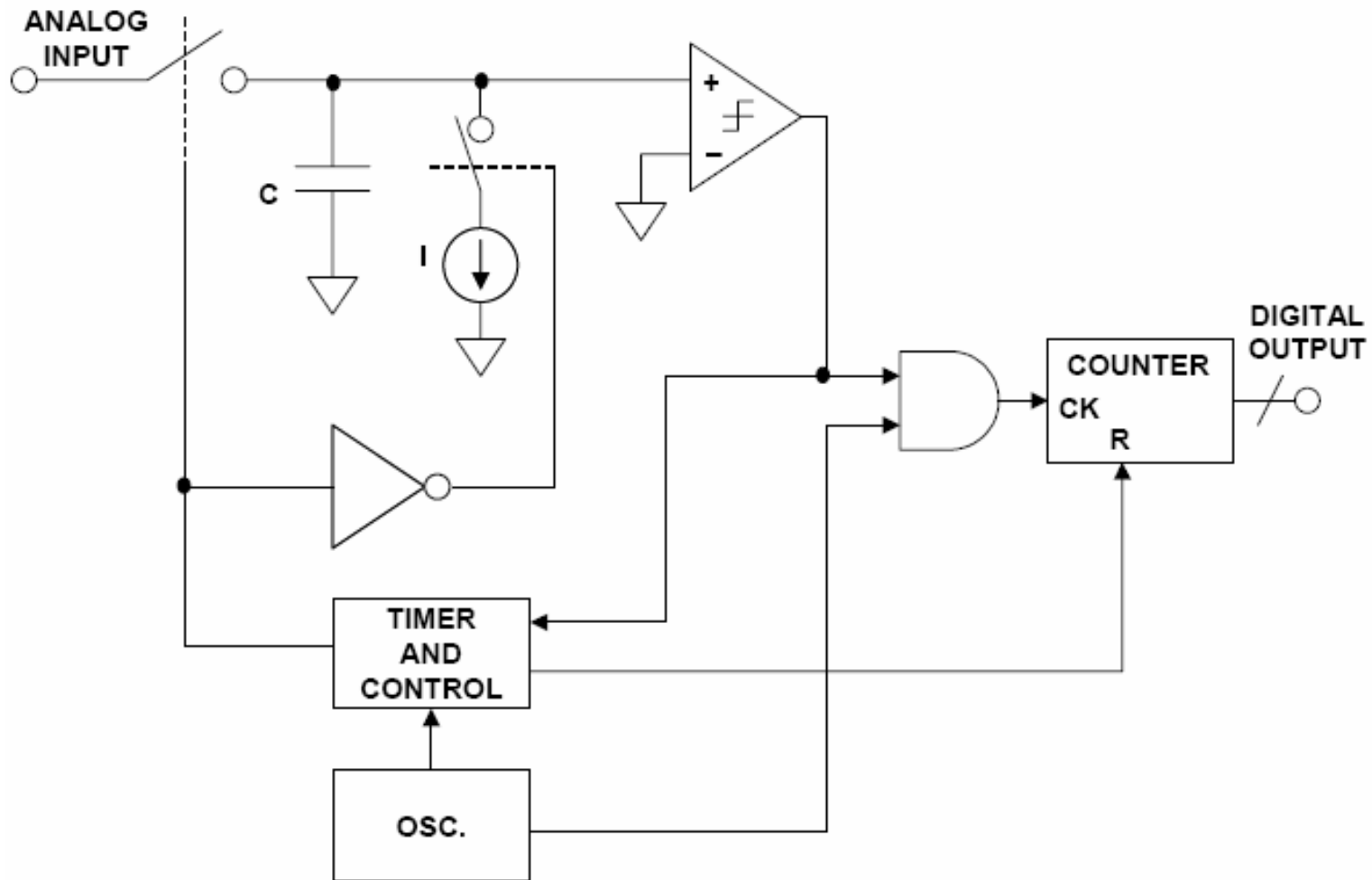


- Capacitor is charged up to the input voltage
- Counter measures the discharge time of capacitor caused by current source
- Accuracy is determined by:
  - Value of capacitance
  - Amplitude of current
  - Time base
- Sampling starts at power on

# Dual Slope ADC

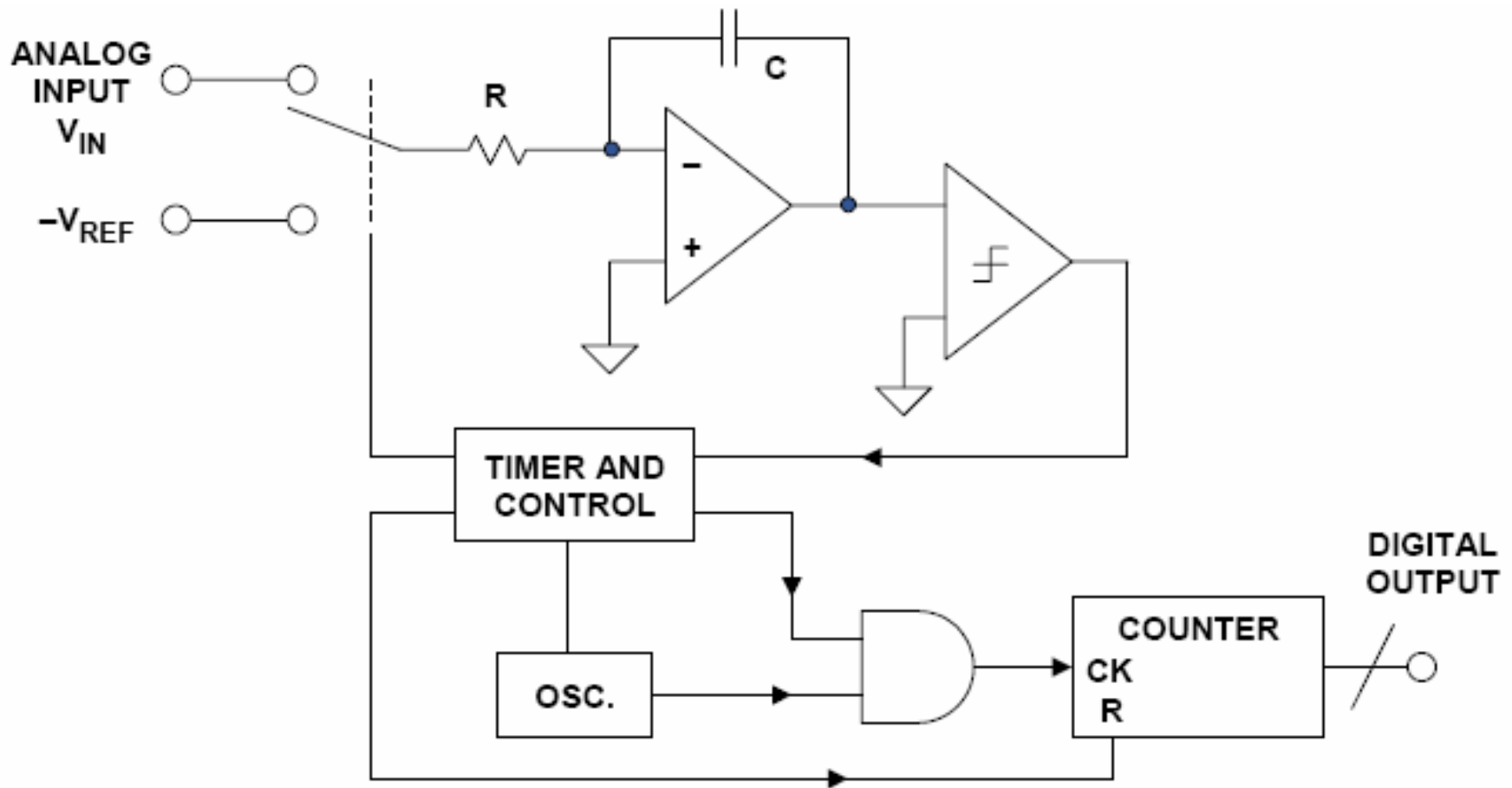

- Integrator output waveforms

 

$$\frac{V_{IN}}{RC} T = \frac{V_{REF}}{RC} t_x$$

$$t_x = \frac{V_{IN}}{V_{REF}} T$$

- Only a short time stability is needed for the clock generator
- Reference voltage dependent



# Voltage-to-Frequency ADC


- monotonic
- free of missing codes
- Integrates noise
- consume small power.




# Sigma-Delta ADC

- Resolutions up to 24-bits
- Excellent differential linearity
- Internal digital filter (can be linear phase)
- Long throughput delay time (output latency)
- Difficult to multiplex inputs due to digital filter settling time

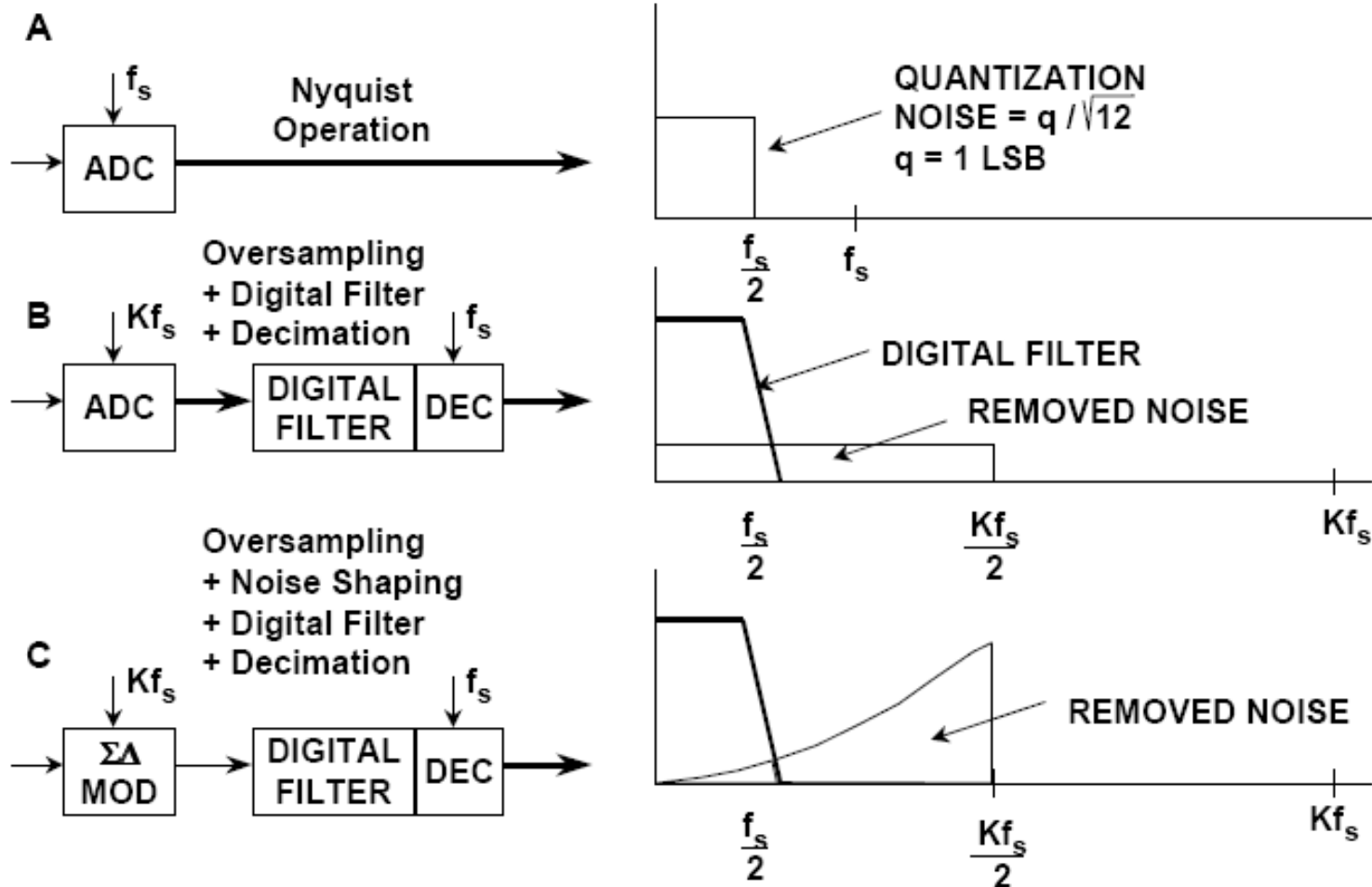
# • Comparison of noise reduction techniques



- First-order Sigma-Delta ADC

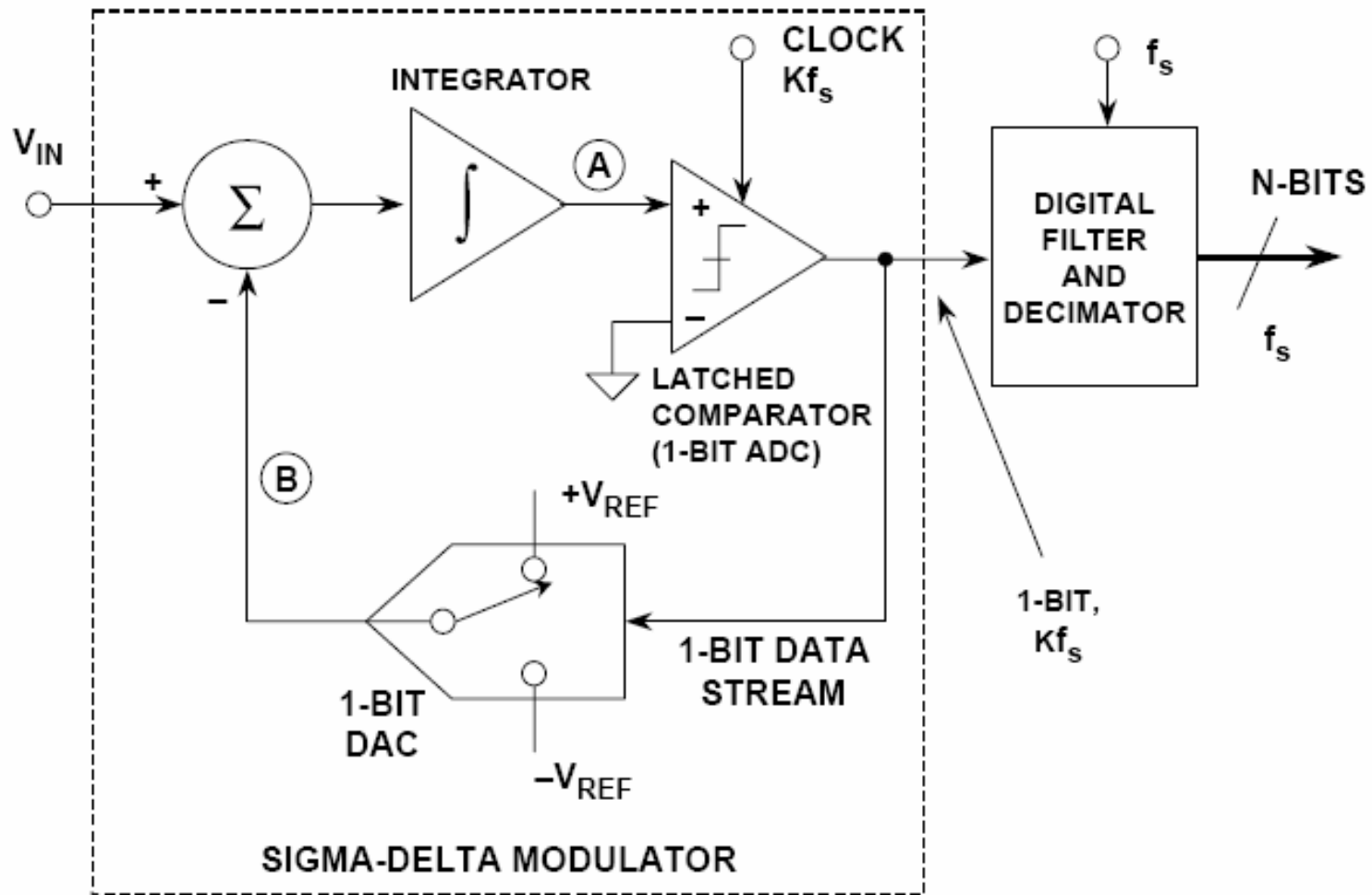

- Linearized model of Sigma-Delta ADC

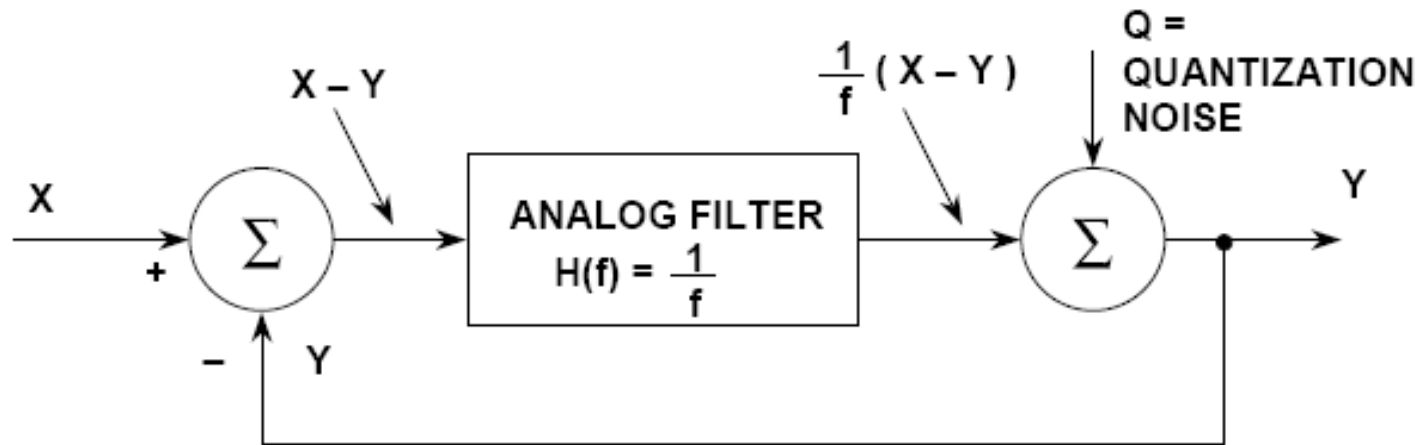

$$Y = \frac{1}{f} (X - Y) + Q$$

REARRANGING, SOLVING FOR Y:

$$Y = \frac{X}{f+1} + \frac{Qf}{f+1}$$

SIGNAL TERM


NOISE TERM

- Frequency domain behaviour


| Y          | X | Q |
|------------|---|---|
| Low freq.  | 1 | 0 |
| High freq. | 0 | 1 |

- Using higher order filter: better suppression  
longer settling  
stability issues

- Second-order Sigma-Delta ADC

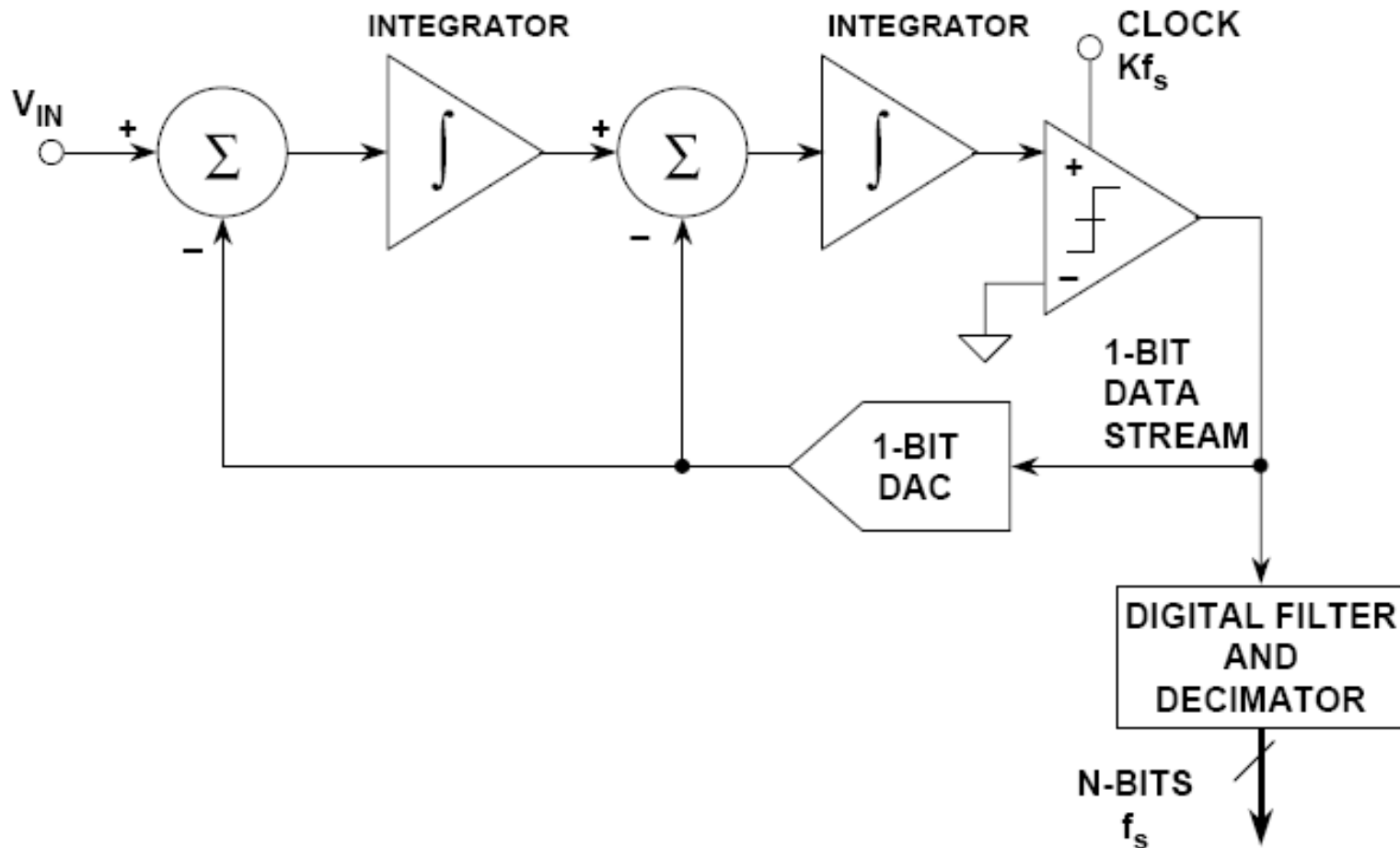


 - Noise reduction properties of Sigma-Delta ADCs





- Multi-bit Sigma-Delta ADCs

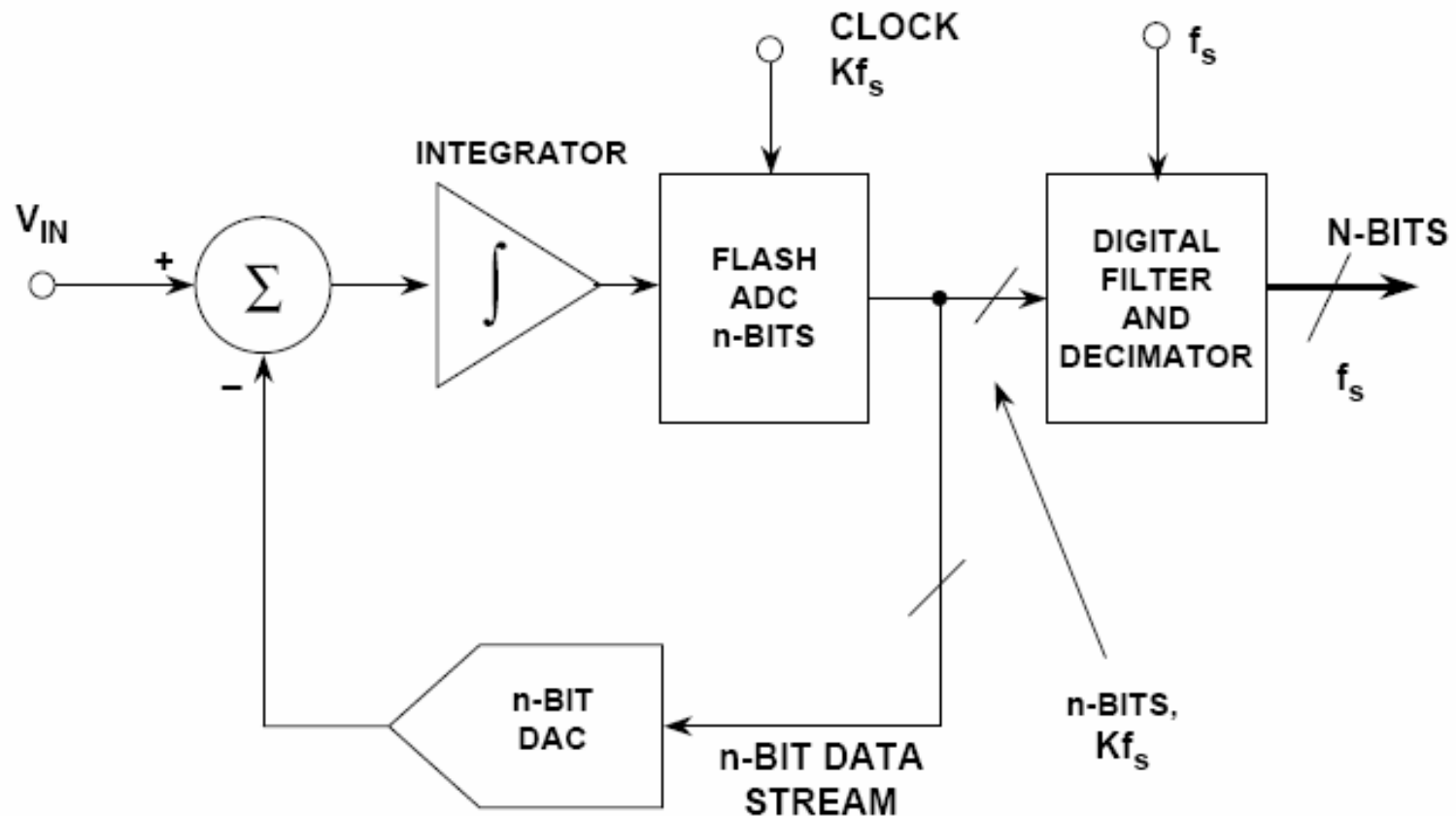

- Linearity problems
- Higher bit number can be achieved with the same oversampling ratio
- Application of Sigma-Delta ADCs
  - Mainly for audio (20-20kHz)
  - Typical bit number: 16-24 bits
  - Pros
    - Linear phase
    - Low cost (ideal for mass production)

– Cons:

- Low sampling frequency
- Cannot be multiplexed (one Sigma-Delta ADC per channel)

# Characterization of distortions in signal analysis

- Harmonic distortion (dBc)
  - Harmonics fall at frequencies  $|\pm K \cdot f_s \pm n \cdot f_a|$ 
    - $f_s$ : sampling frequency
    - $f_a$ : input signal frequency
    - $n$ : order of harmonic
    - $K$  is a natural number
  - Types: worst harmonic (largest value)

total harmonic distortion, THD=

$$\sqrt{\frac{\sum H_i^2}{N}} \cdot \frac{1}{A}$$

A: amplitude of input signal

H: amplitude of harmonic

N: number of harmonics

- Total harmonic distortion + noise (THD+N)

$$THD + N = \frac{\sqrt{\frac{\sum H_i^2}{N} + \frac{\sum n_i^2}{M}}}{A}$$

- n: noise+other disturbances excluding harmonics
- M: defines the noise bandwidth

- Signal-to-noise ratio, SNR

$$SNR = \frac{A}{\sqrt{\frac{\sum n_i^2}{M}}}$$


- Signal-to-noise and distortion ratio

$$\text{SINAD} = 1 / (\text{THD} + \text{N})$$


- Effective number of bits (in dB)

$$\text{ENOB} = (\text{SINAD} - 1.76) / 6.02$$

- Spurious-free dynamic range

 


- Intermodulation distortion

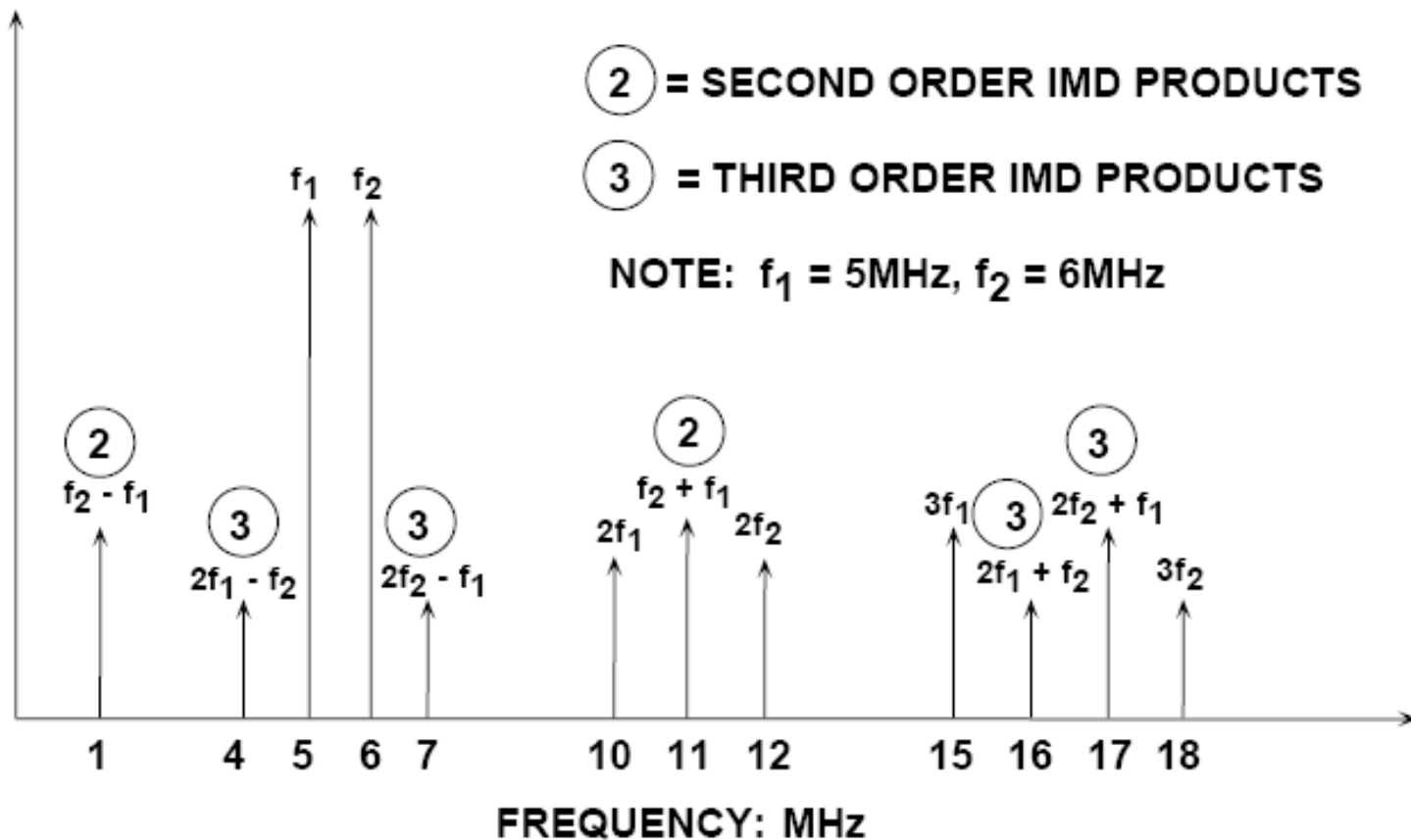



# Jitter

- Uncertainty of sampling time instant

 

# References

- Analog Devices: Basic Linear Design
- Analog Devices: ADCs for DSP Application