

Field Programmable Gate Array (FPGA)

Lecturer: Krébesz, Tamas

FPGA in general


- Reprogrammable Si chip
- Invented in 1985 by Ross Freeman (Xilinx inc.)
- Combines the advantages of ASIC and uC-based systems
- HW-timed -> fast operation and reliable
- Cheap even if the volume is low (in contrast to ASIC)

FPGA vs. uC-based systems

- Similar flexibility
- FPGA: execution speed is not limited by the number of processing cores
 - Parallel in nature
 - No competition for system resources
 - Processing tasks are assigned to dedicated chip sections
 - Autonomous operation of functions
 - Performance is not affected by multiple tasks



- How is it achieved?
 - Application logic is implemented in HW not by executing on top of OS in SW

Building blocks of FPGA

 


Xilinx Spartan 3E family architecture

  - FPGA is built up of a finite number of predefined resources
 - Configurable logic block (CLB)
(slices, logic cell)
 - Basic logic unit of FPGA
 - Made up of two basic components
 - Flip-flops (FF)
 - Look-up-tables (LUT)
 - FF: on every CLK edge FF latches 1 or 0 on its input and hold that value constant until next CLK edge-> binary shift register



– LUT:

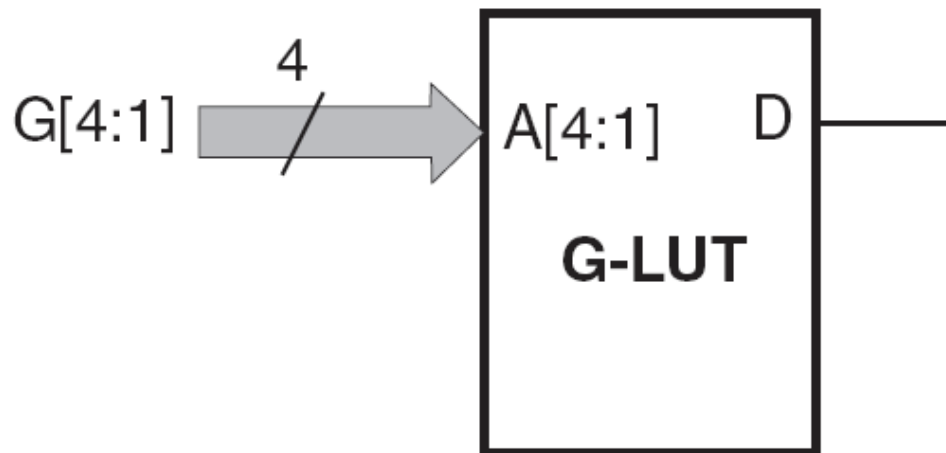- Provides mucs of the logic of CLB
- Small amount of RAMs
- Logic is implemented as truth tables within LUT memory
 - Truth table: predefined list of outputs for every combination of inputs



- Example for implementing logic function:
AND operation



INPUT		OUTPUT
A	B	A AND B
0	0	0
0	1	0
1	0	0
1	1	1

- Input/output blocks (IOBs)
 - Control the data flow between the I/O pins and the internal logic
- Digital CLK manager (DCM)
 - Distributing, multiplying, dividing CLK signal
 - Different CLK rate is possible for different FPGA sections
- Fixed-function logic block
 - Prebuilt processing block to save FPGA resources
 - Example: multiplier blocks
 - Dedicated multiplier associated with RAM

- Block RAM (BRAM)
 - Configurable, user-defind RAM
 - 16-36 kbyte
 - Used for
 - Data storage
 - Passing data between logic blocks running at different CLK rates


FPGA-based systems

- No driver system or code-based system (that uP and OS have)
- Communications to peripherals is difficult
- Hybrid architecture: uP is paired with FPGA and connected to I/O
- Implementation
 - System components and their interconnections (wiring) has to be defined by design SW

- In the past only low-level design solution existed
- Now high-level synthesis (HLS) design tools available
 - HW description languages (HDL)
 - Verilog, VHDL -> text based
- Even higher level design languages
 - Graphical-based (G-code) languages

(Note: coding in HDL is out of the scope of this subject)

 - The code is compiled and a bit file is generated to be downloaded on the FPGA
 - It defines the circuit itself (blocks and interconnections)




Reconfigurable interconnections

- Fusible link
 - Not reversible
 - Applying a high-voltage pulse disconnects the wires
- Antifuse link
 - Not reversible
 - Applying a high-voltage pulse connects the wires


- Flash transistor
 - Switching the transistor to on/off state controls the connection of wires
 - Reversible
 - Non-volatile (if power off, the state is preserved)
- SRAM-based
 - Most widely used
 - Reversible
 - Volatile (reprogramming is needed at every startup)

Resources of CLB

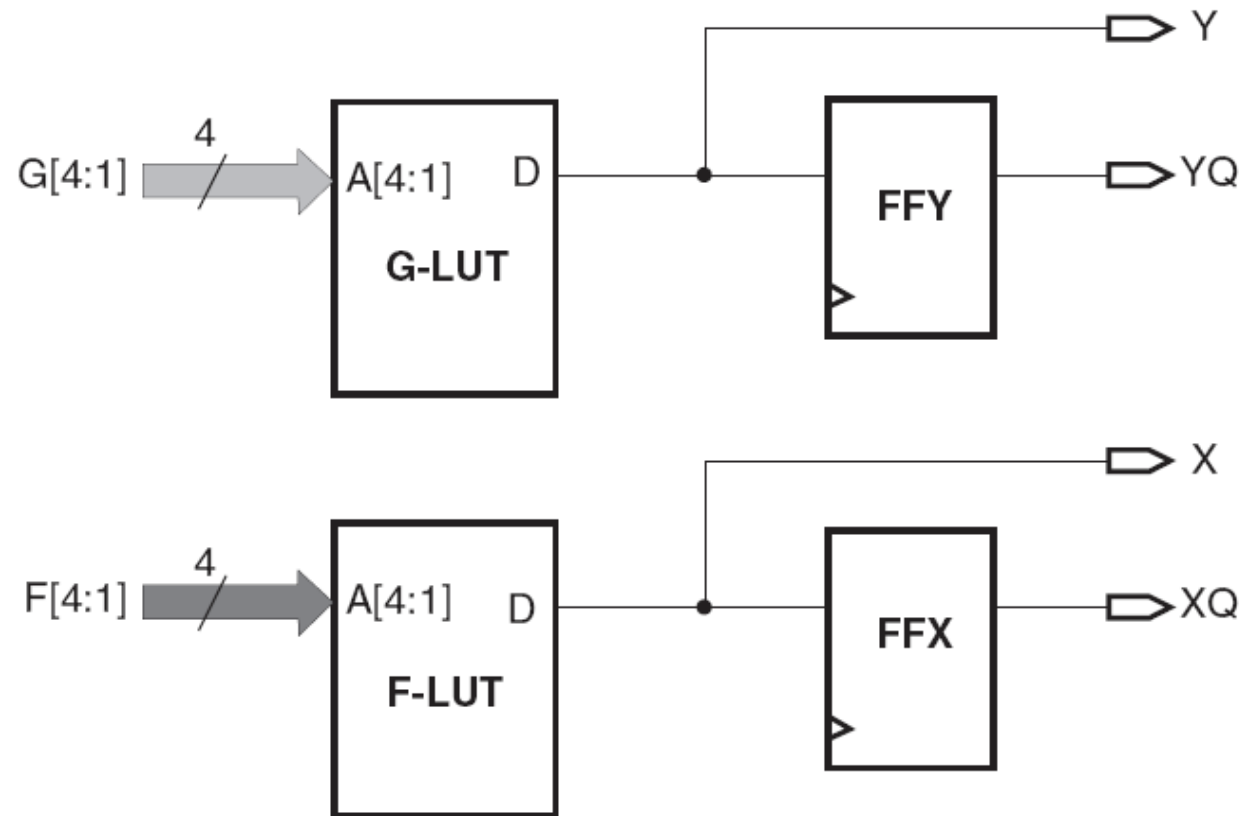
- Resource unit = logic cell = 1LUT+1FF
- In a slice:



 - Logic functions of many variables requires to many levels of logic cells -> slow
- Arithmetic operations requires carry-bit
 - Fast carry generation is a must
 - Example: full adder




Fast carry generation

 


- $\text{Sum} = A \text{ xor } B \text{ xor } C$
- Carry: propagation/generation
- $\text{Cout} = A * B + A * \text{Cin} + B * \text{Cin}$
 $(A \text{ xor } B) * (\text{Cin} \text{ or } A)$ selects either Cin or A

- Application of multiplexer (MUX) for logic


- MUX-based AND:

 

- MUX-based OR:

 


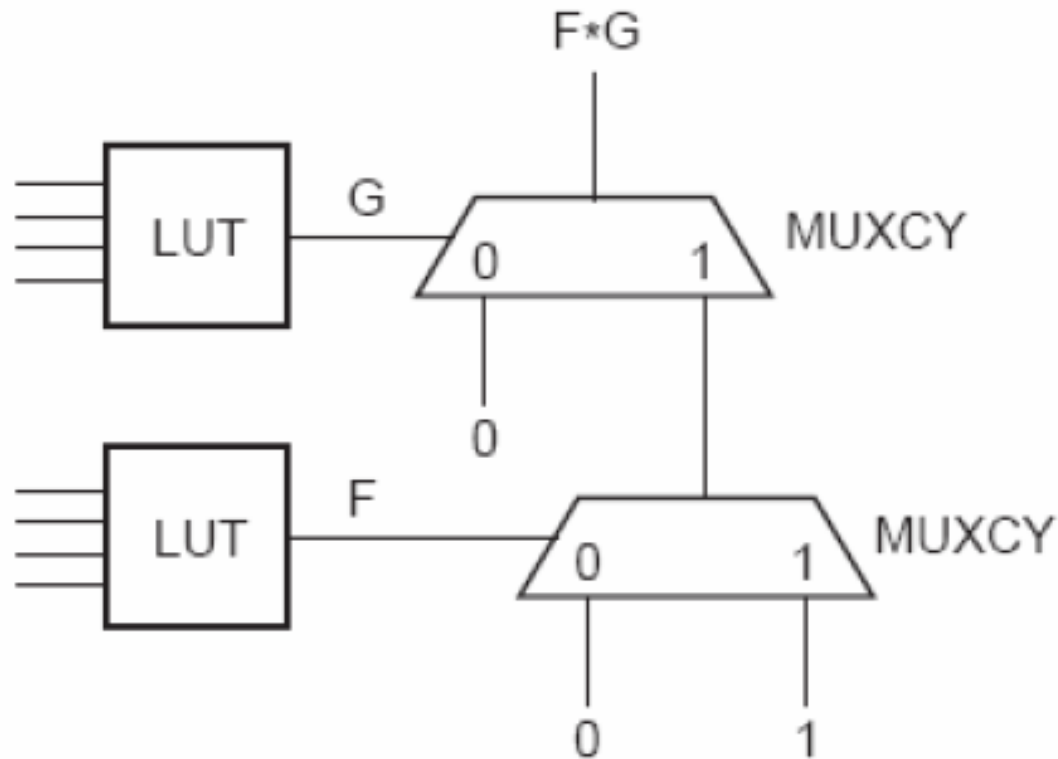- Combining LUT4s using MUX
 - „wider” logical functions





LUT RAM

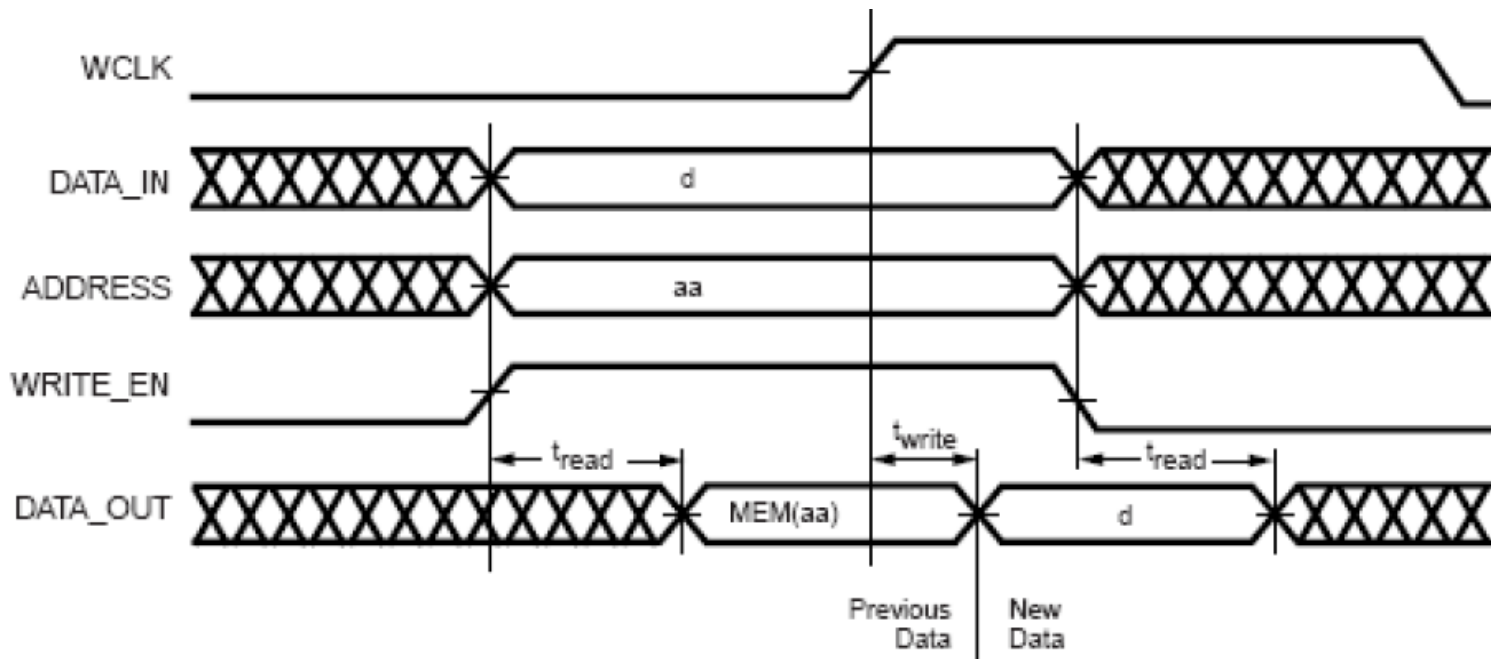
- Writing is synchronous
 - CLK edge -> writing starts
- Reading async -> independent of CLK



 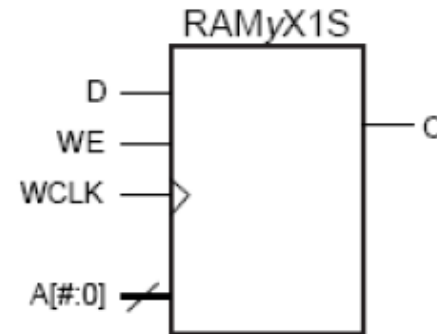
- Distributed RAM
 - Single port RAM:
read or write access
allowed one at a time
 - Dual port RAM:
read or write possible
at the (nearly) same
time



 - Realization: in one slice
 - one RAM16x1D or ...



- ...one RAM32x1S

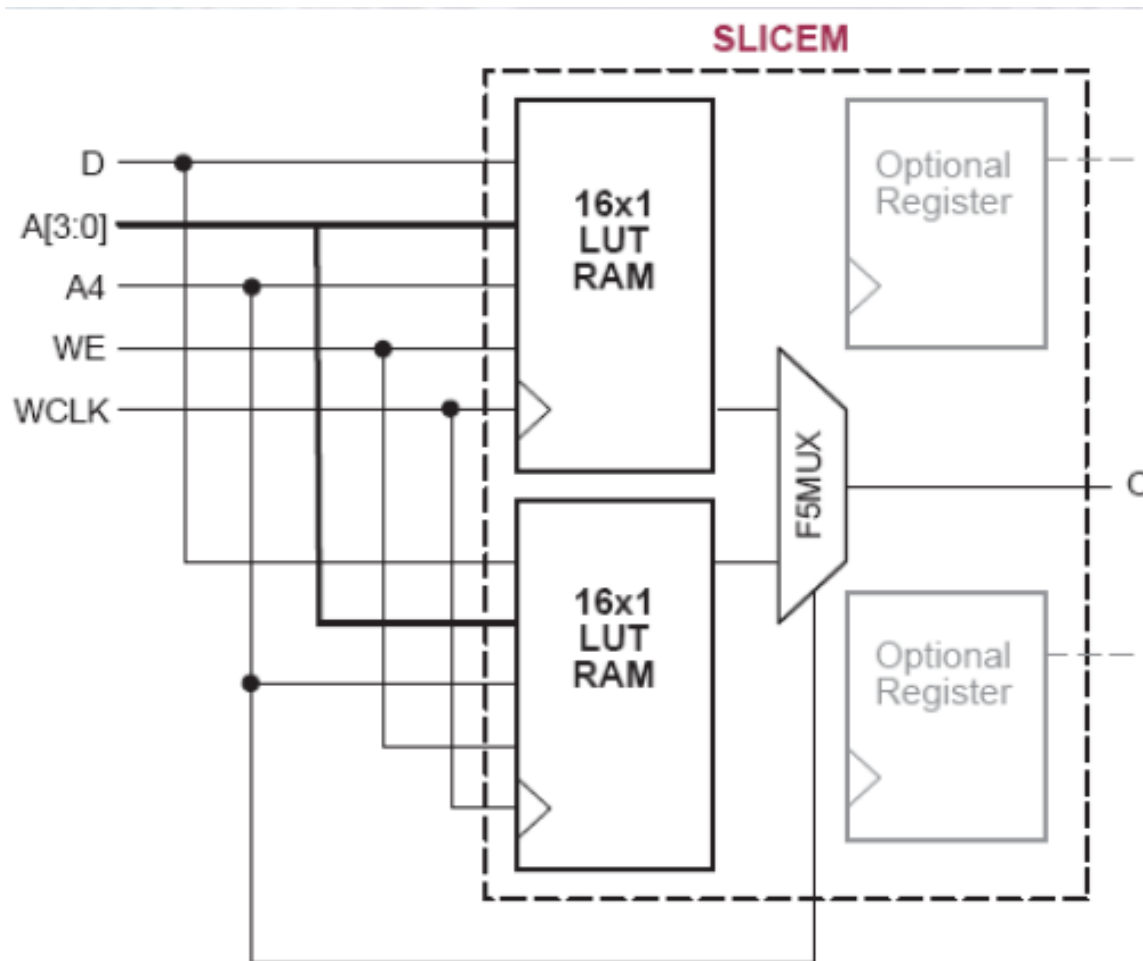

- Size of RAM (data width) can be increased
 - RAM32x8S -> 8 slices are used

Slice M:


Logic/ROM

Distributed RAM


Shift register

Slice L:

Logic/ROM only

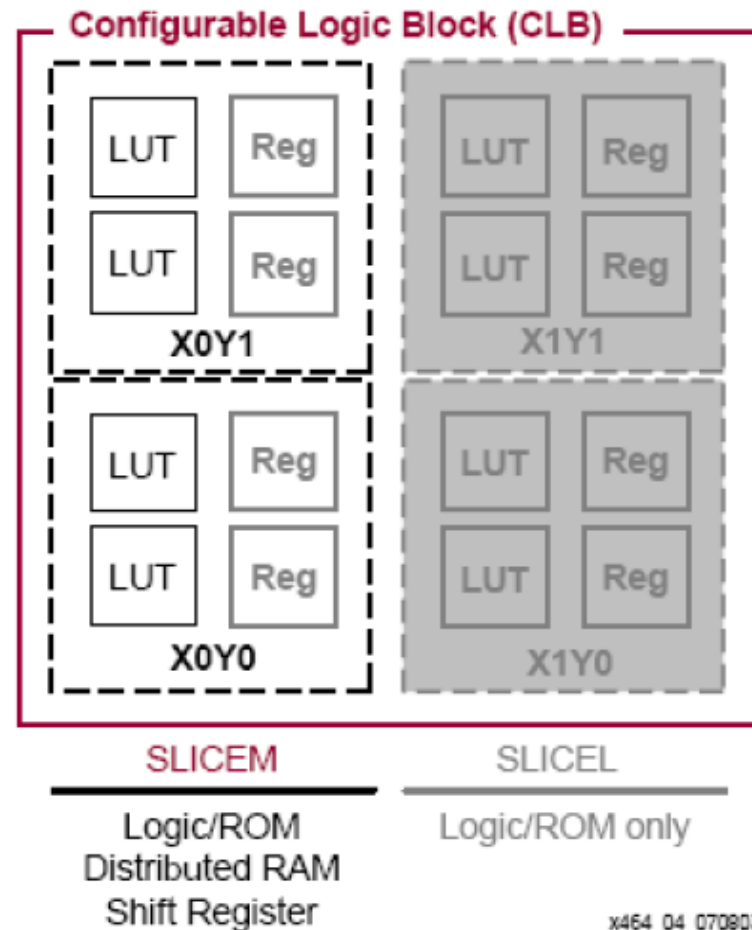


LUT shift register (SRL16)

 

- Flexible applications
- Serial delay of variable length (1-16)
- Can be cascaded to neighbouring CLBs

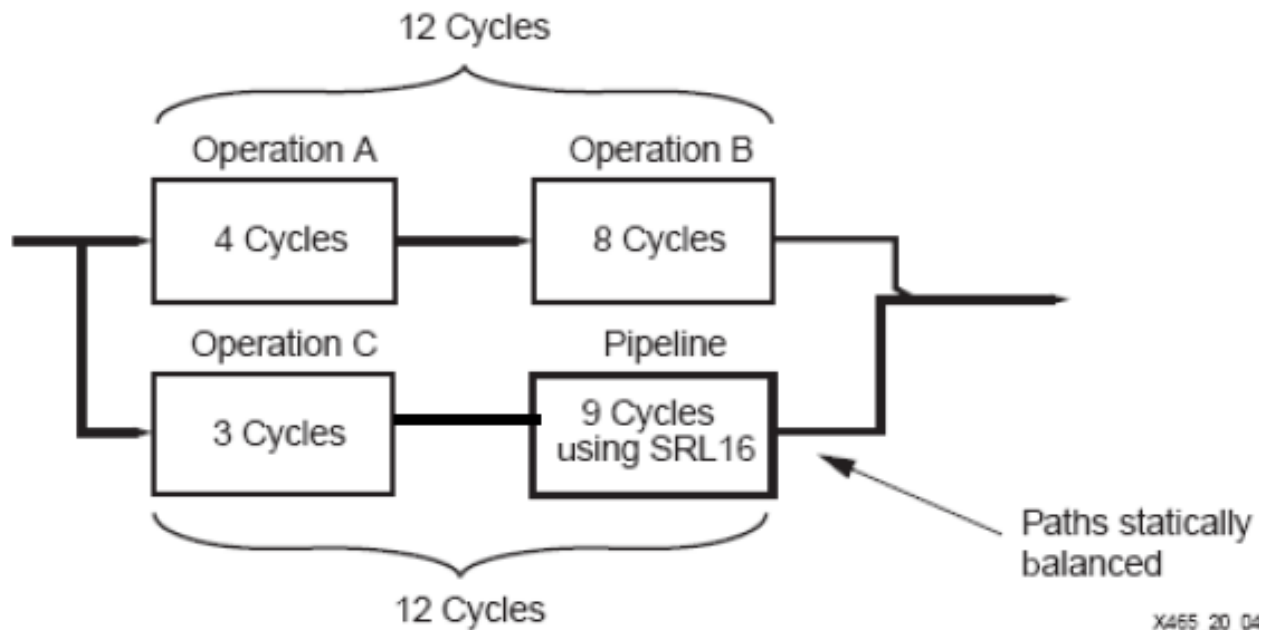
- Typical application of LUT SRL
 - Balancing delays caused by pipe-line
 - Data width determines the number of LUTs



- Small FIFO
 - Data in SRL
 - Auxiliary logic
 - Address counter
 - Status indicator
- Random number generator
- Code generator
- Counter


BRAM

- 2-4 kbyte dual port synchronous RAM
- 4-36 pieces
- Data width can be changed dynamically
- R/W options:

 

DS312-2_01_020705

- BRAM on the FPGA

 


UG332_04_12_011008

- BRAM is used for
 - data exchange between different CLK rate sections
 - as a logic circuit similar to a big LUT
 - storing tables (sin()); cos(); etc.)

Multiplier

- Full parallel 18x18-bit multiplier
- Matched to BRAM 18-bit configuration
- FIR filtering supported
- 2's complement -> signed operations
- 36-bit result
- Can be extended to 35x35-bit

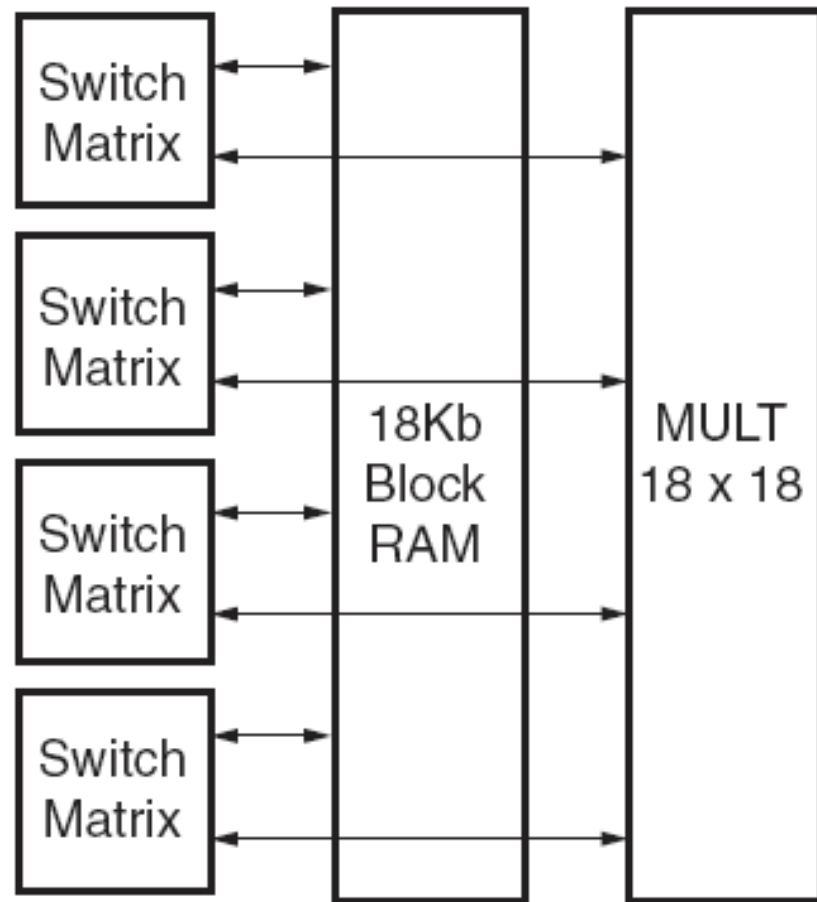- Block diagram of interconnects with multiplier



DS312_08_100110

I/O blocks

- Connection between FPGA and outside world
- Several I/O standard supported
 - Single ended: LVCMOS 1.2; 1.5; 1.8; 2.5;3.3V
 - Differential:
 - LVDS – low-voltage differential signalling
 - SSTL – stub series terminated logic
 - TMDS – transition minimized differential signaling

- Three state driver
- Registers
- Programmable delays (IODELAY)
- Transceiver

Clock source management

- Very important part of the design
- Synchronous operation is required
 - One CLK in one block/module
 - Slower scheduling implemented by CLK driven enable input
 - For the whole design different CLKs possible
 - Careful design between blocks using different CLKs

- Global CLK network
 - Die are divided into 4
 - Each $\frac{1}{4}$ has 8-8 global CLK network
 - Can be used independently vs. Globalized
 - » Matter of energy consumption
 - Driving only by global CLK buffer (BUFG)
 - Sources of CLK
 - External
 - CLK handle modul output
 - Any internal signal

- Features
 - Only minimal delay of CLK on the whole FPGA area
 - Cannot be used as logic signal
 - CLKs can be changed by MUXs
 - Can be used for
 - Synchronization
 - Frequency divider
 - 2x frequency multiplier
 - Phase shifter/splitter
 - PLL frequency synthesizer

References

- Xilinx Spartan-3E FPGA Family Data Sheet
- Xilinx online resources