

Digital design lab 4A


Digital design lab 4A

- Today you will learn about hierarchical design of digital circuits
- The design will be done on 2 levels:
 - First you will design the submodules
 - Then the top module will be designed, and the submodules will be instantiated
- The PC is good example for hierarchical digital systems: the submodules are the processor, memory, VGA, etc. Each submodule has a well defined functionality, they are independent subsystems with unique behavior.
- In this case the top module is the motherboard, which connects the submodules, and integrates the subsystems (submodules) in to one high-level system.

Digital design lab 4A

- The specification of the high level system of today's laboratory is the following: the circuit reads two hexadecimal numbers from the switches: one number from sw[3:0], and the other from sw[7:4].
- The two numbers (A and B), and their sum (A+B) will be shown on the 7-segment display of the system: one digit for A, one digit for B, and two digits for A+B (since the maximum value is $F + F = 1E$).
- To implement such system, we need the following components: multiplexer, decoder, hexadecimal to 7-segment converter.
- In addition, we need a circuit that continuously counts from 0 to 3. This is a sequential circuit, so it won't be studied in details right now.

- The design is the following:

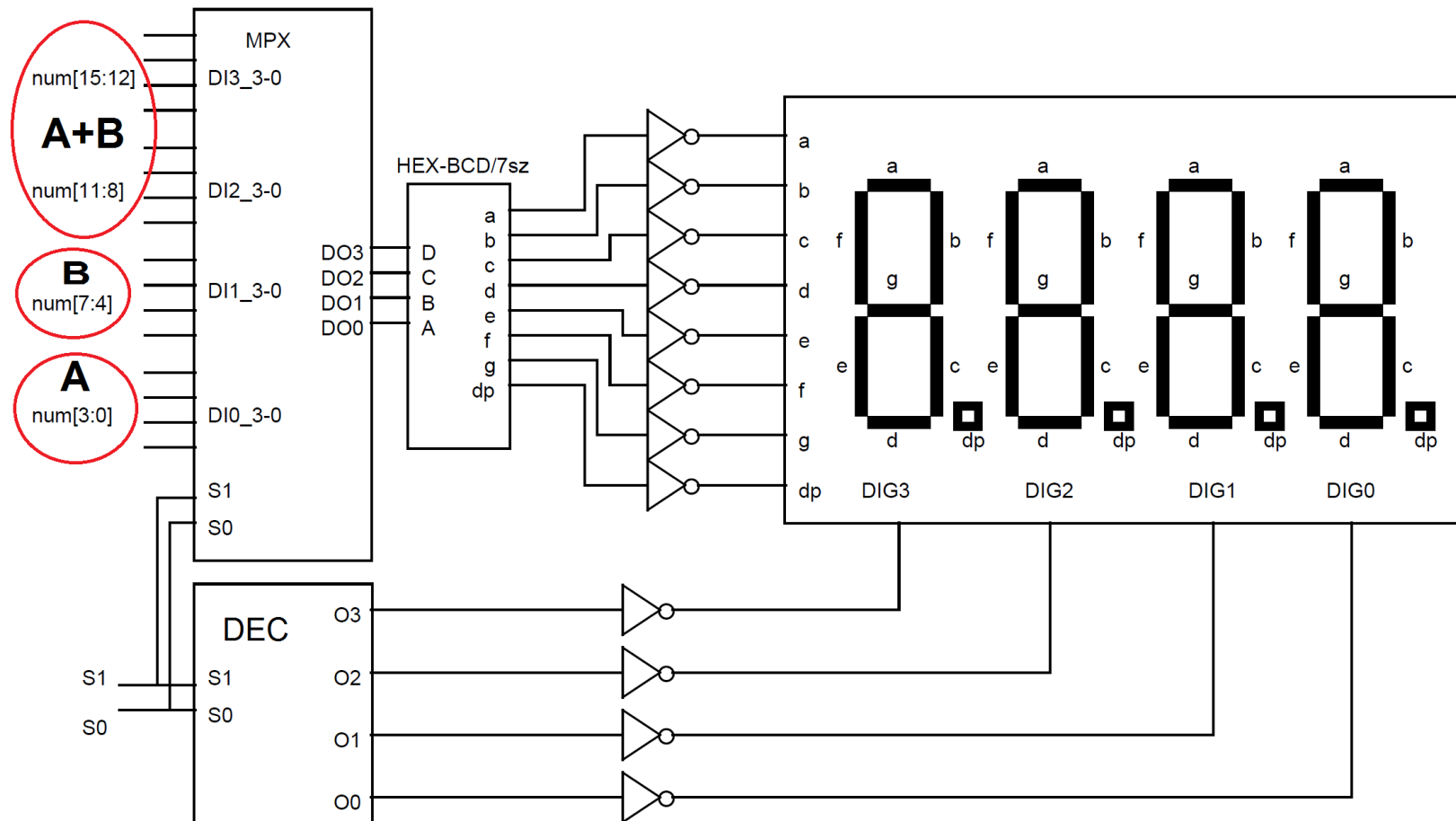

Digital design lab 4A

- Let's start with the 7-segment display (in the top right corner). It has two group of inputs:
 - Inputs a b c ... g and dp: these inputs control the LEDs, dp is for the decimal point LED, it will not be used today.
 - Inputs DIGn: Digit selector inputs, the LED control inputs are forwarded to the selected digit.
- These are **negative logic inputs**: 0 input means true and 1 means false.
- **Example**: if the b and c inputs are 0, the others are 1 on the LED control input, and DIG2=0, the others are 1 on the digit selector input, than a 1 will appear on the second digit from the left.
- **Note**: we will design the circuit assuming positive logic, and we will invert the signals in the last step (as it is shown in the figure)

Digital design lab 4A


- The S1-S0 signals belong to the counter that counts from 0 to 3 repeatedly: 00, 01, 10, 11, 00, 01, 10, 11, 00,
- We use the decoder to decode this signal: the corresponding output of the decoder is set to 1 to select a digit.
- At the same time S1-S0 is the input of the multiplexor too: based on the value of S1S0, the multiplexor forward one of its 4 4-bit input.
- This value is converted to a 7-segment number, and the result of the conversion appears on the LED control inputs of the 7-segment display.
- Let's start the implementation.

Digital design lab 4A

- Launch the ISE design suite



- Create a new project

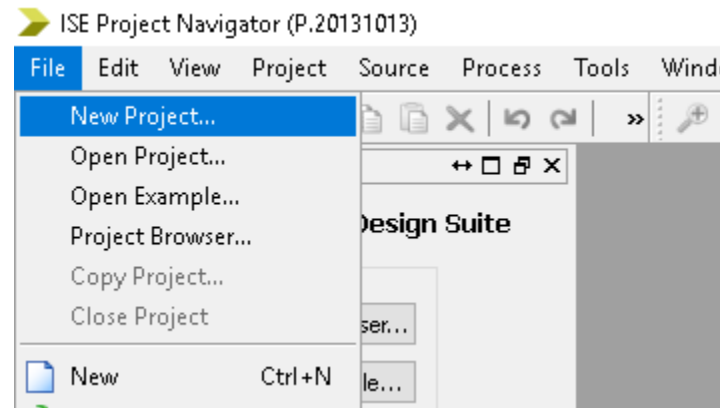

Digital design lab 4A

- Name: Digital_design_lab_4A
- Work on the D: drive
- Press Next

New Project Wizard

← Create New Project
Specify project location and type.

Enter a name, locations, and comment for the project

Name: Digital_design_lab_4A

Location: D:\Digital_design_lab_4A ...

Working Directory: D:\Digital_design_lab_4A ...

Description:

Select the type of top-level source for the project

Top-level source type:
HDL

More Info Next > Cancel

Digital design lab 4A

- Verify the settings:
 - Spartan3E
 - XC3S250E
 - TQ144
 - -4
- Press Next, than Finish

New Project Wizard

← Project Settings
Specify device and project properties.


Select the device and design flow for the project

Property Name	Value
Evaluation Development Board	None Specified
Product Category	All
Family	Spartan3E
Device	XC3S250E
Package	TQ144
Speed	-4
Top-Level Source Type	HDL
Synthesis Tool	XST (VHDL/Verilog)
Simulator	ISim (VHDL/Verilog)
Preferred Language	Verilog
Property Specification in Project File	Store all values
Manual Compile Order	<input type="checkbox"/>
VHDL Source Analysis Standard	VHDL-93
Enable Message Filtering	<input type="checkbox"/>

More Info < Back **Next >** Cancel


Digital design lab 4A

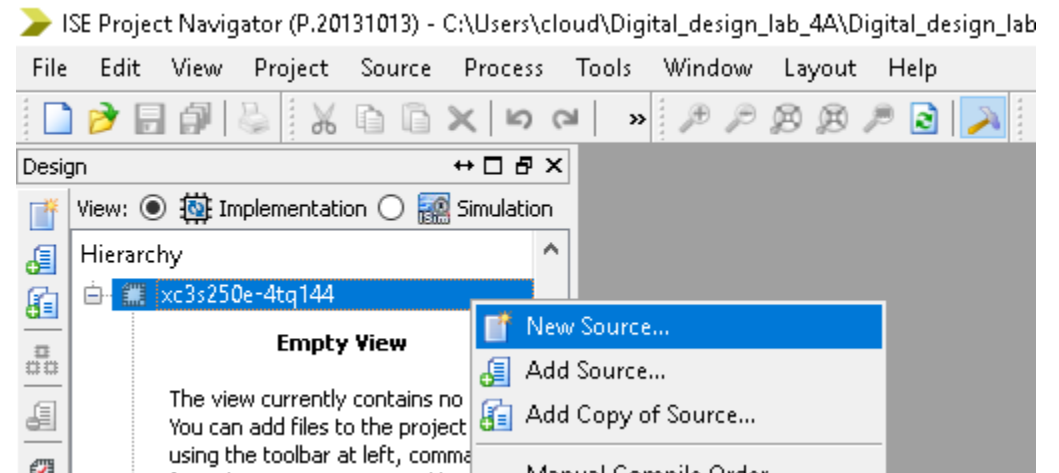- Right click on the label
- Select New source...



Digital design lab 4A

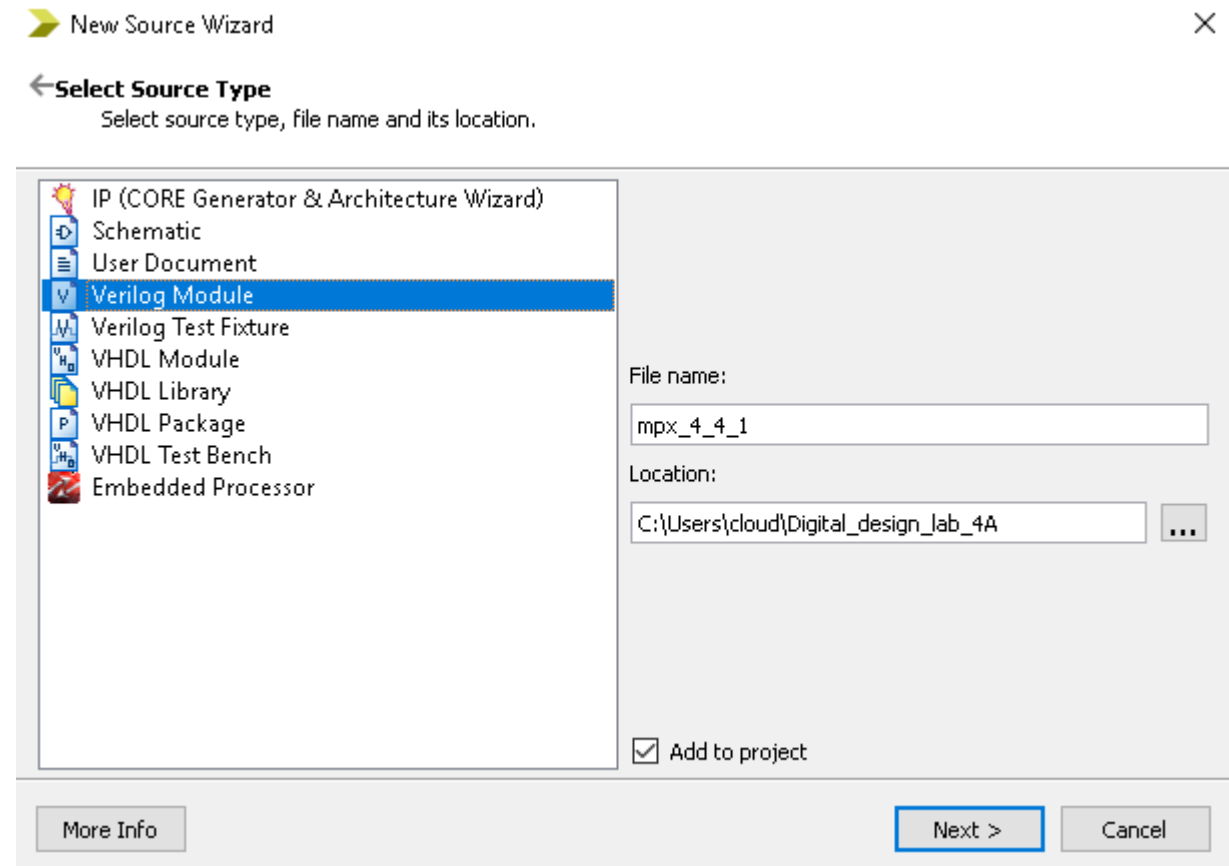- Select Verilog module
- Name: mpx_4_4_1
- This will be a 4x4x1 multiplexor:
It has 4 4-bit input
- Make sure “Add to project” is checked
- Press Next



Digital design lab 4A

- Do **NOT** add the signals here, We will add them manually later
- Press Next, then Finish

New Source Wizard ✕


← Define Module
Specify ports for module.

Module name

Port Name	Direction	Bus	MSB	LSB
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		

More Info < Back **Next >** Cancel


Digital design lab 4A

- Add the following source code:
- Note: we use “output reg” instead of “output” in the module declaration
- This is needed to be able to use the always block
- As we have seen on the practice, this is a simpler and more overviewable way to describe the circuit’s behavior.
- Use the “<=“ operator for register assignments (instead of “=“)
- Save all changes 

```
21 module mpx_4_4_1(  
22     input [1:0] s,  
23     input [15:0] num,  
24     output reg [3:0] out  
25 );  
26  
27 always @ (*)  
28     case (s)  
29         2'b00: out <= num[3:0];  
30         2'b01: out <= num[7:4];  
31         2'b10: out <= num[11:8];  
32         2'b11: out <= num[15:12];  
33         default: out <= num[3:0];  
34     endcase  
35  
36 endmodule  
37
```


Digital design lab 4A

- Add another new source file

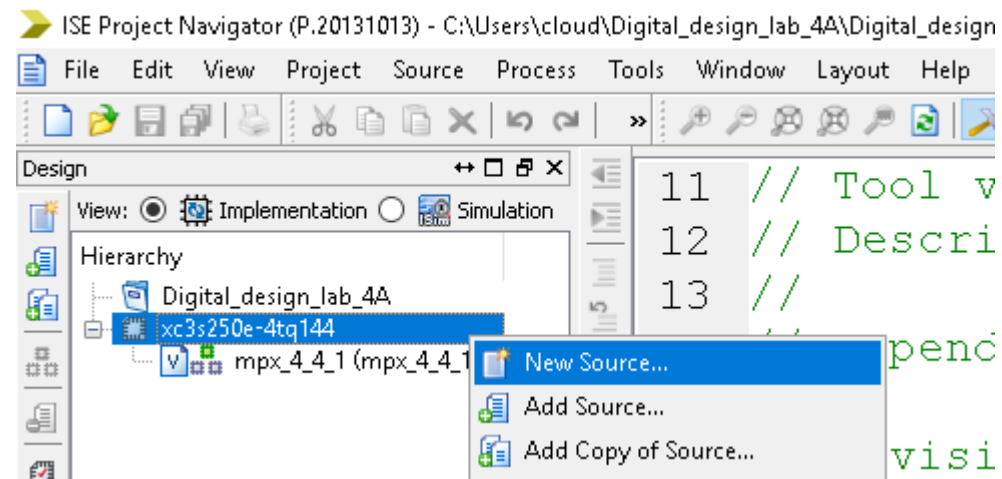

Digital design lab 4A

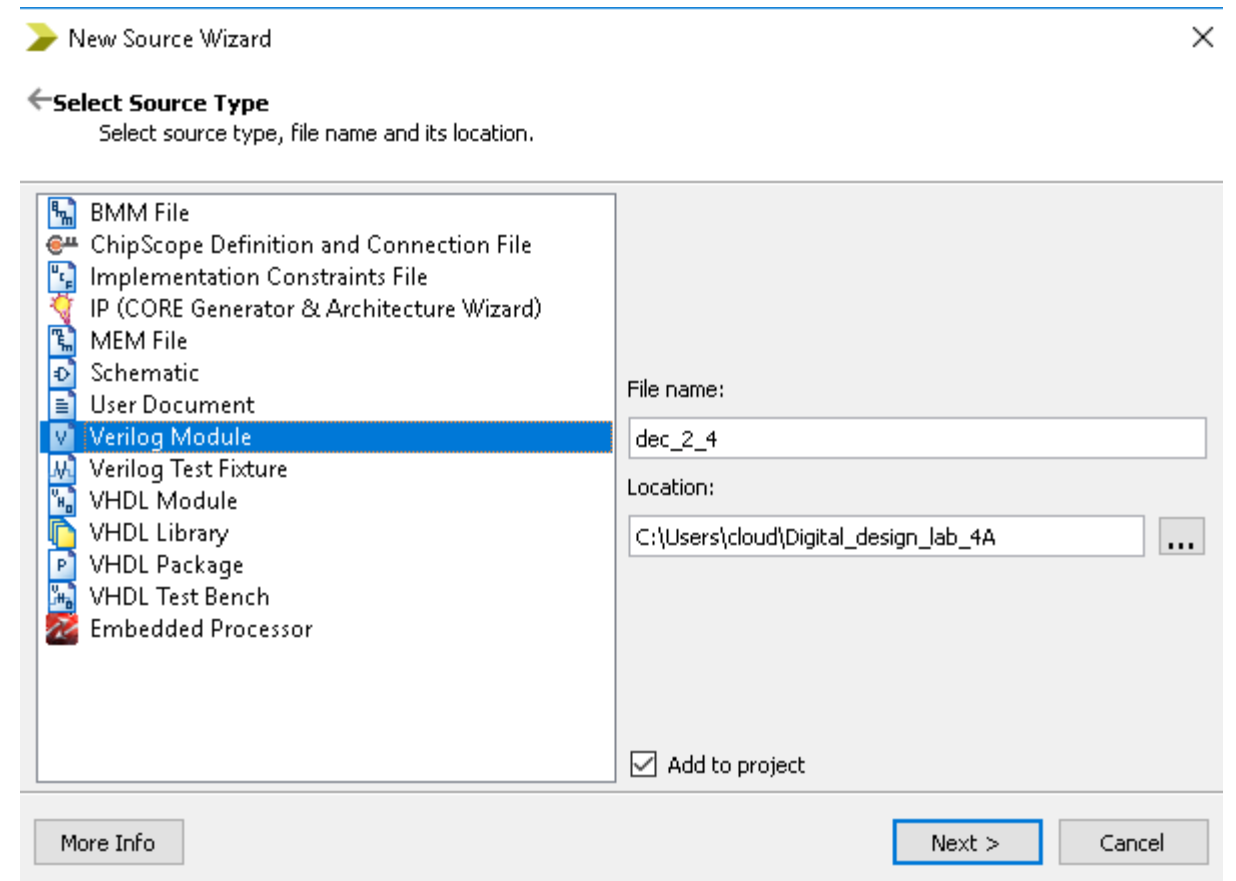- Verilog module
- Name: dec_2_4
- This will be the decoder
- Make sure “Add to project” is checked
- Press Next



Digital design lab 4A

- Leave the table blank
- Press Next, then Finish


New Source Wizard ✕

← Define Module
Specify ports for module.

Module name

Port Name	Direction	Bus	MSB	LSB
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		


Digital design lab 4A

- Add the following source code:
- Mind the reg keyword after output in the header
- Save all changes 

```
21 module dec_2_4(  
22     input  [1:0] s,  
23     output reg [3:0] dig  
24 );  
25  
26 always @ (*)  
27     case (s)  
28         2'b00: dig <= 4'b0001;  
29         2'b01: dig <= 4'b0010;  
30         2'b10: dig <= 4'b0100;  
31         2'b11: dig <= 4'b1000;  
32         default: dig <= 4'b0001;  
33     endcase  
34 endmodule
```


Digital design lab 4A

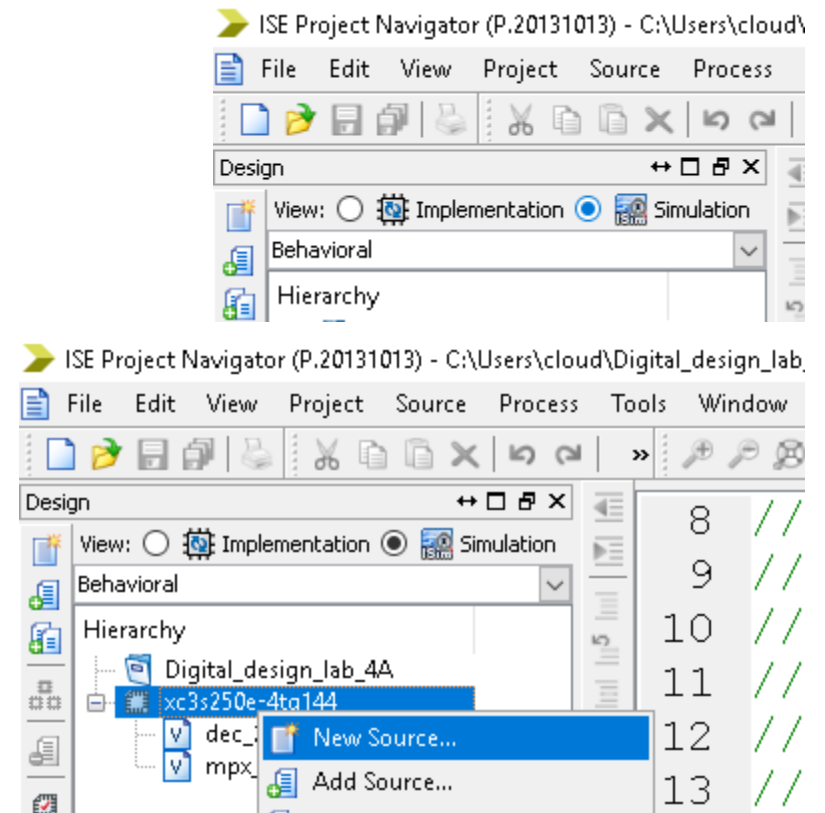- Now we will test the decoder and the multiplexor
- First switch to Simulation mode
- Then right click on the label, and select New Source




Digital design lab 4A

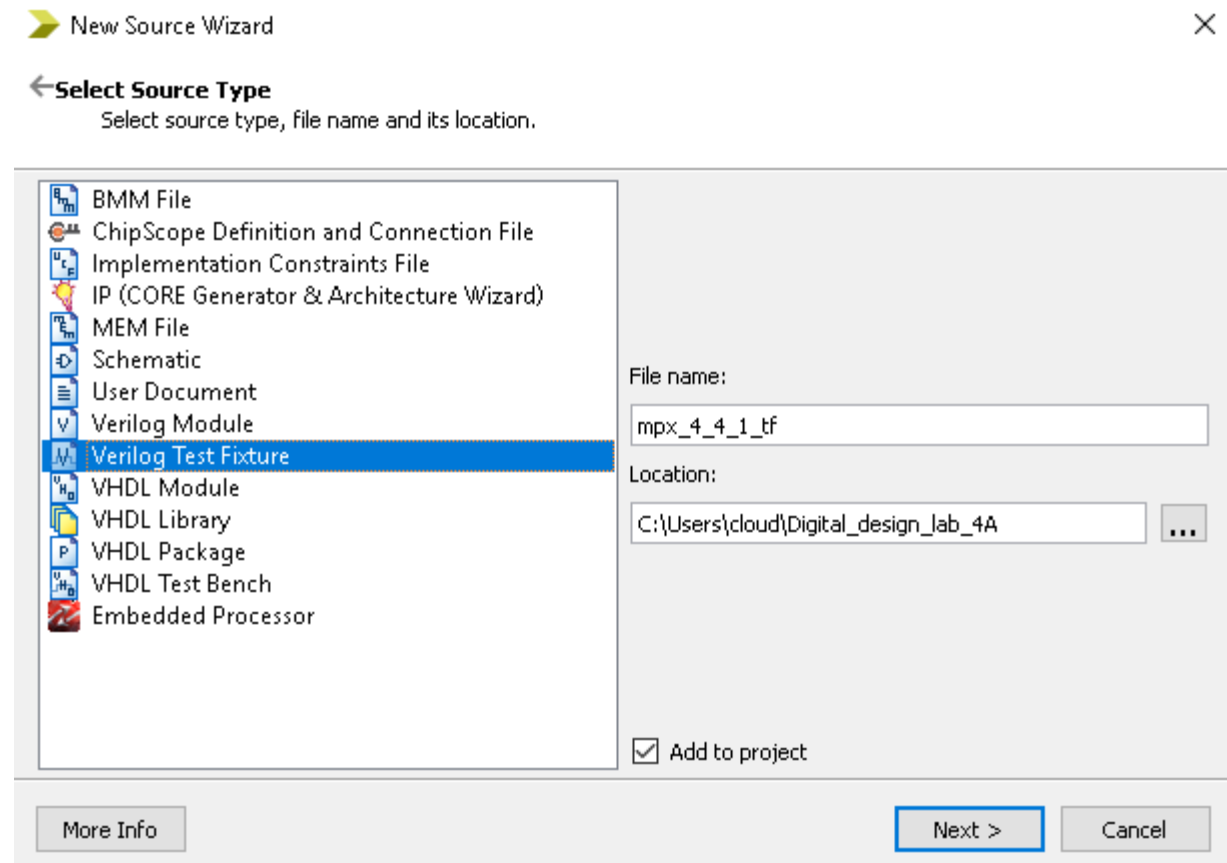- Select Verilog Test Fixture
- Name: mpx_4_4_1_tf
- Press Next



Digital design lab 4A

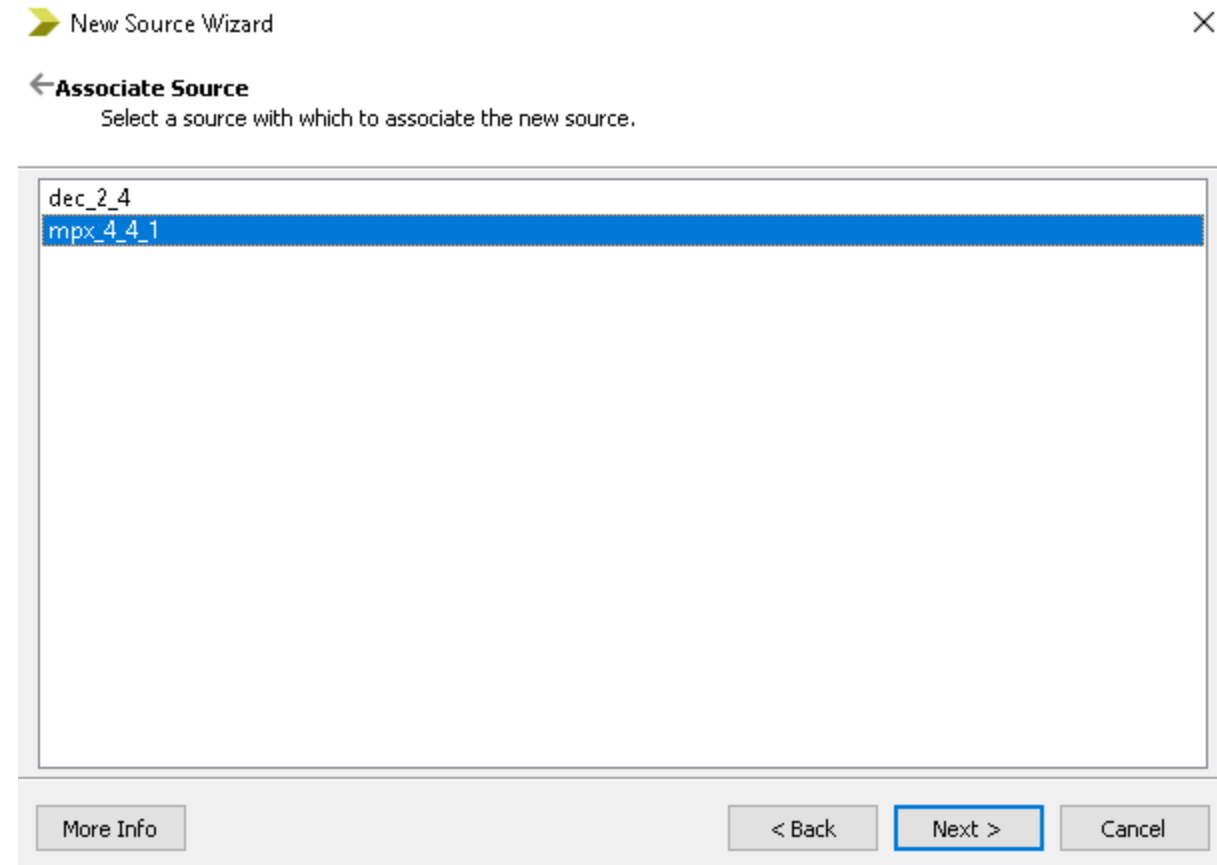- Select the mpx_4_4_1 circuit here
- Press Next, then Finish




Digital design lab 4A

- Add the following code after the `initial begin` part
- Save all changes 


```
41 initial begin
42     // Initialize Inputs
43     s = 0;
44     num = 0;
45
46     // Wait 100 ns for global reset to finish
47     #100;
48
49     // Add stimulus here
50     #100; s=2'b00; num=16'h048C;
51     #100; s=2'b01;
52     #100; s=2'b10;
53     #100; s=2'b11;
54
55 end
```

Digital design lab 4A

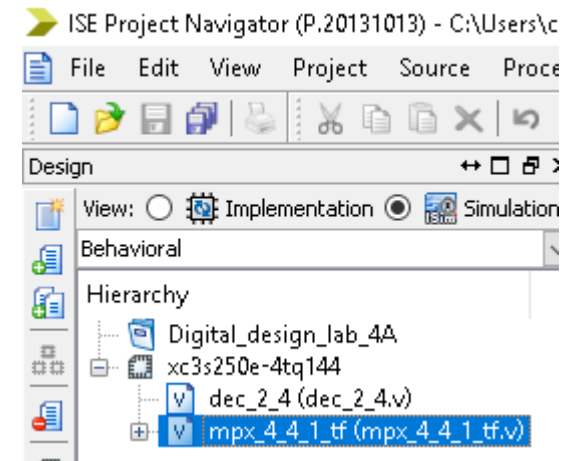- Left click on the mpx_4_4_1_tf module in the top left corner of the ISE





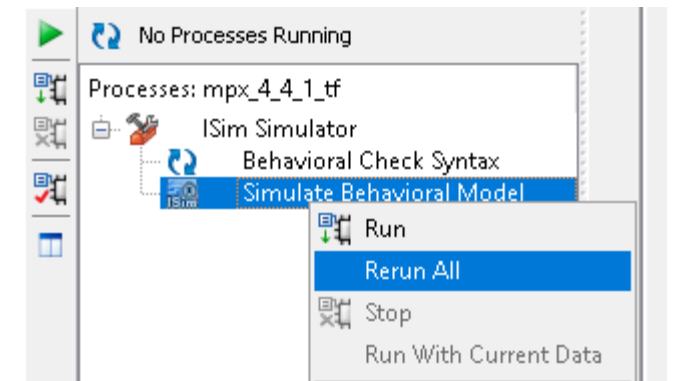- Then right click on “Simulate Behavioral Model”, and select “Rerun All”




Digital design lab 4A

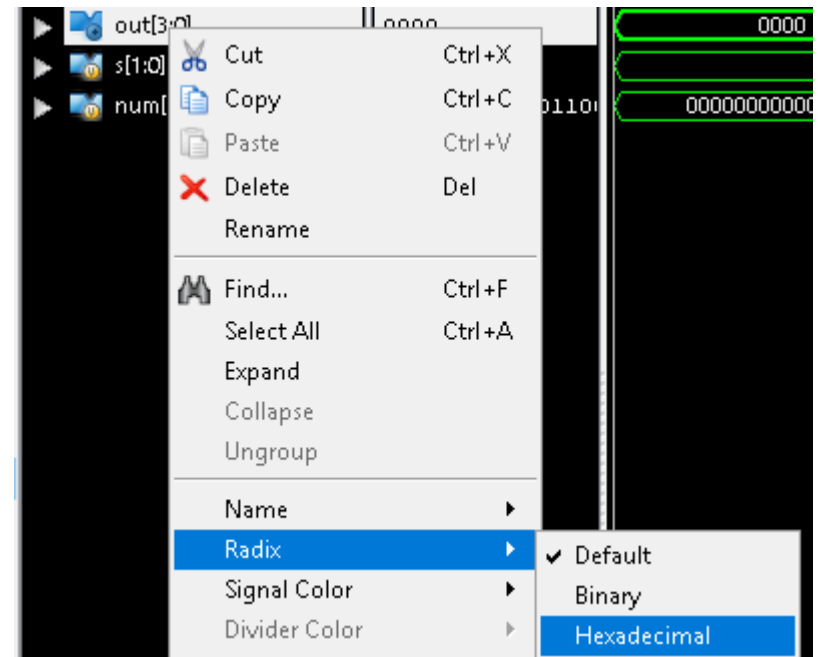 - A window pops up with the simulation results. Press the “Zoom to Full View” button
- Right click on the out[3:0] signal, and select Radix->Hexadecimal
- Do the same for the s[1:0] and num[15:0] signals
- Check the simulation output



Digital design lab 4A

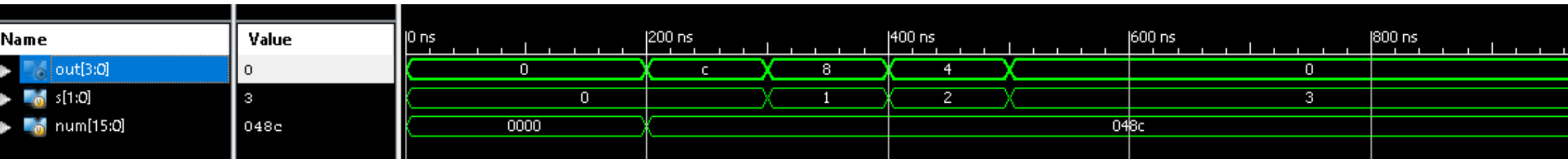
- Does the correct hexadecimal value appear on the output for each value of s[1:0]?
- Help: num = 0000010010001100 = 048C



- For example, for s=1 the output of the multiplexor is 8. Is that right?
- What is the output for s=0, s=2 and s=3?
- Close the simulator


Digital design lab 4A

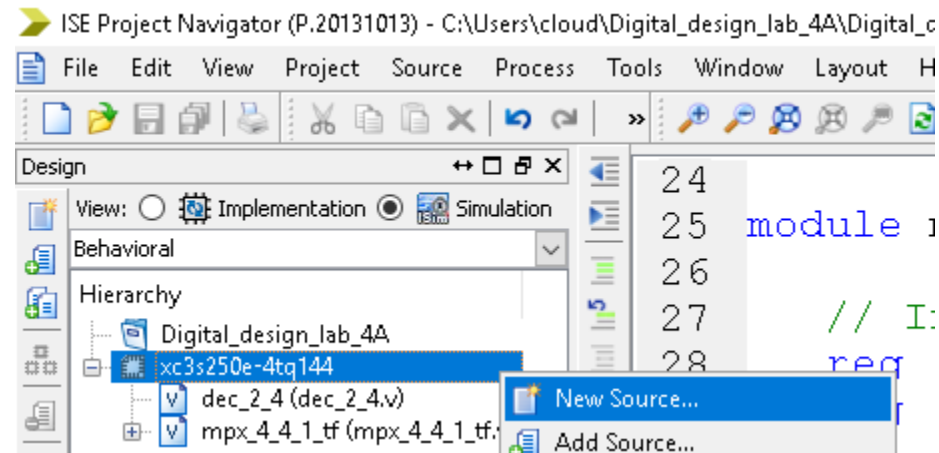- Now you will test the decoder. Right click on the label, and select New source...




Digital design lab 4A

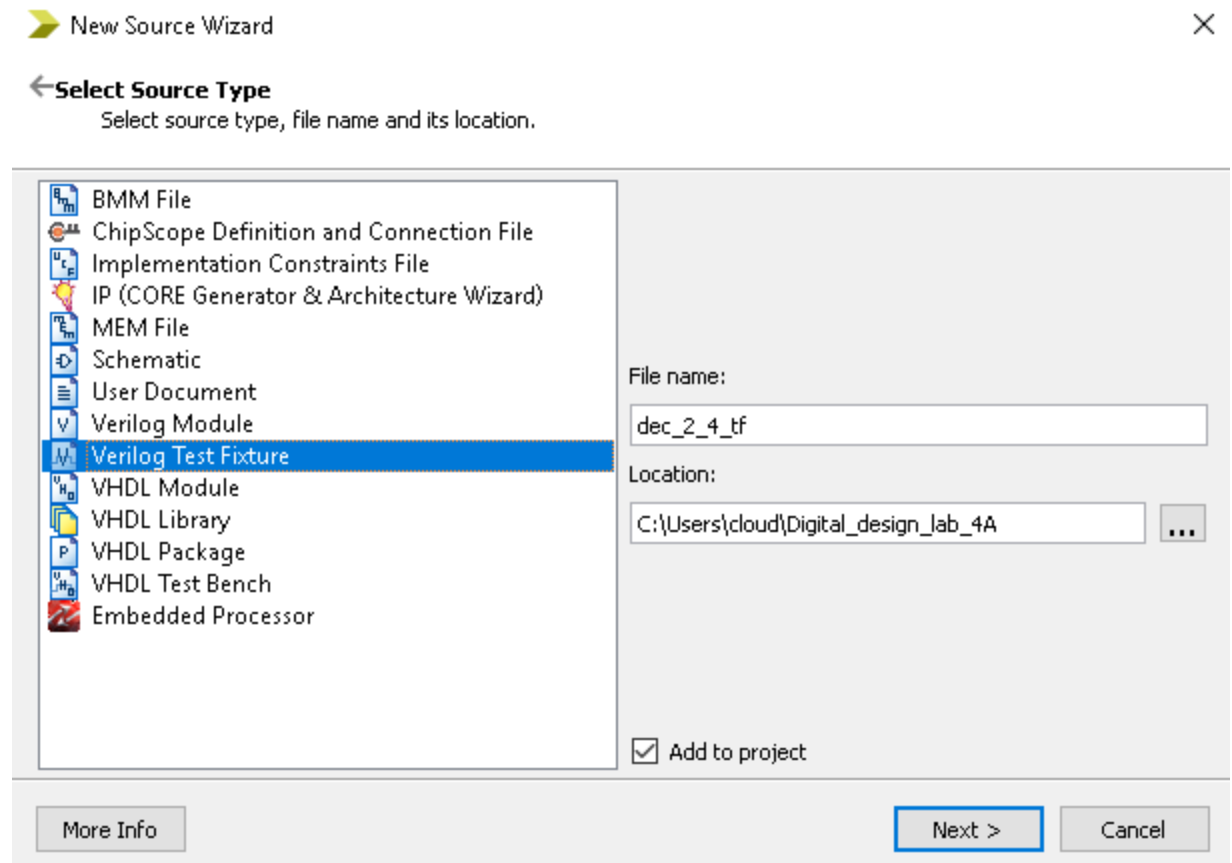- Name: dec_2_4_tf
- Don't modify the location
- Check "Add to project"
- Press Next




Digital design lab 4A

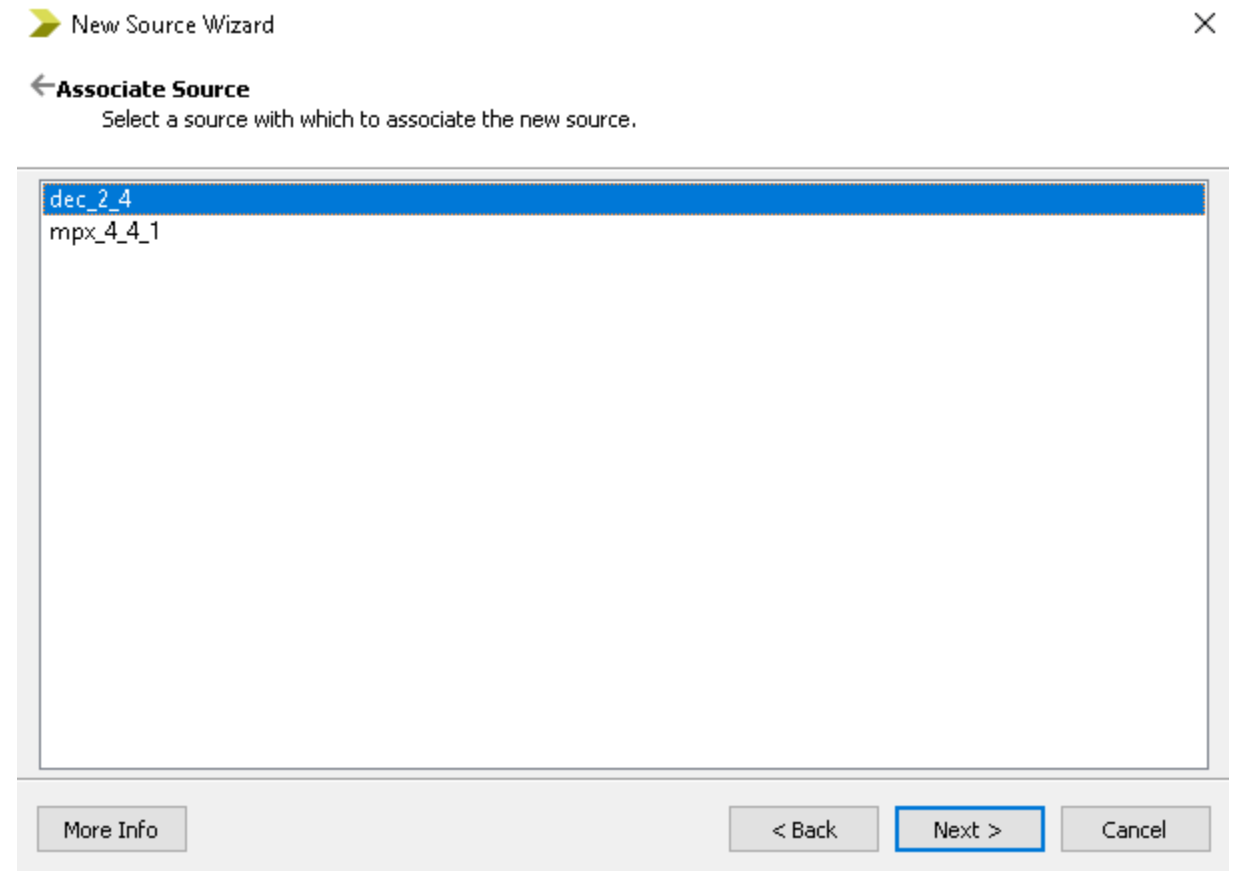- Select the dec_2_4 module
- Press Next, then Finish





Digital design lab 4A

- We will test the module using a for loop
- Add the `integer i;` line before the `initial begin` part
- Don't forget to save your changes 

```
38 integer i;
39 initial begin
40     // Initialize Inputs
41     s = 0;
42
43     // Wait 100 ns for global reset to finish
44     #100;
45
46     // Add stimulus here
47     for (i=0; i<4; i=i+1)
48     begin
49         #25; s=i;
50     end
51 end
```


Digital design lab 4A

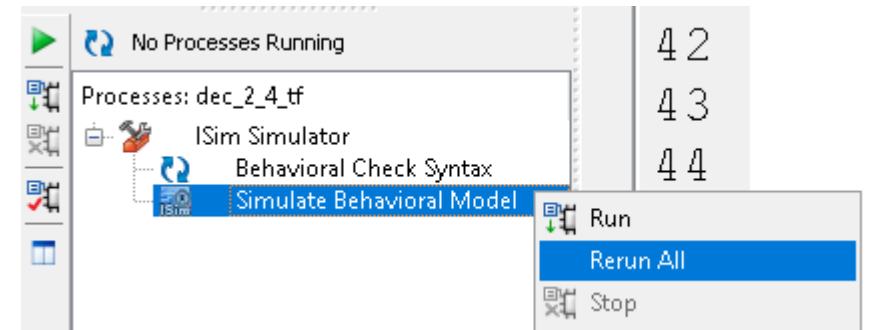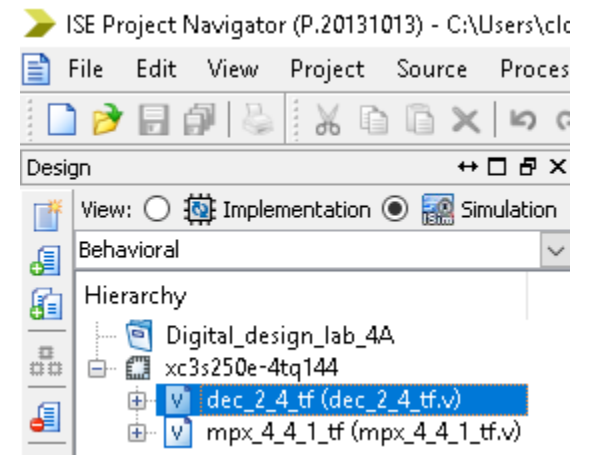- Left click on the dec_2_4_tf module in the top left corner
- Then right click on “Simulate Behavioral Model”, and select “Rerun All”




Digital design lab 4A

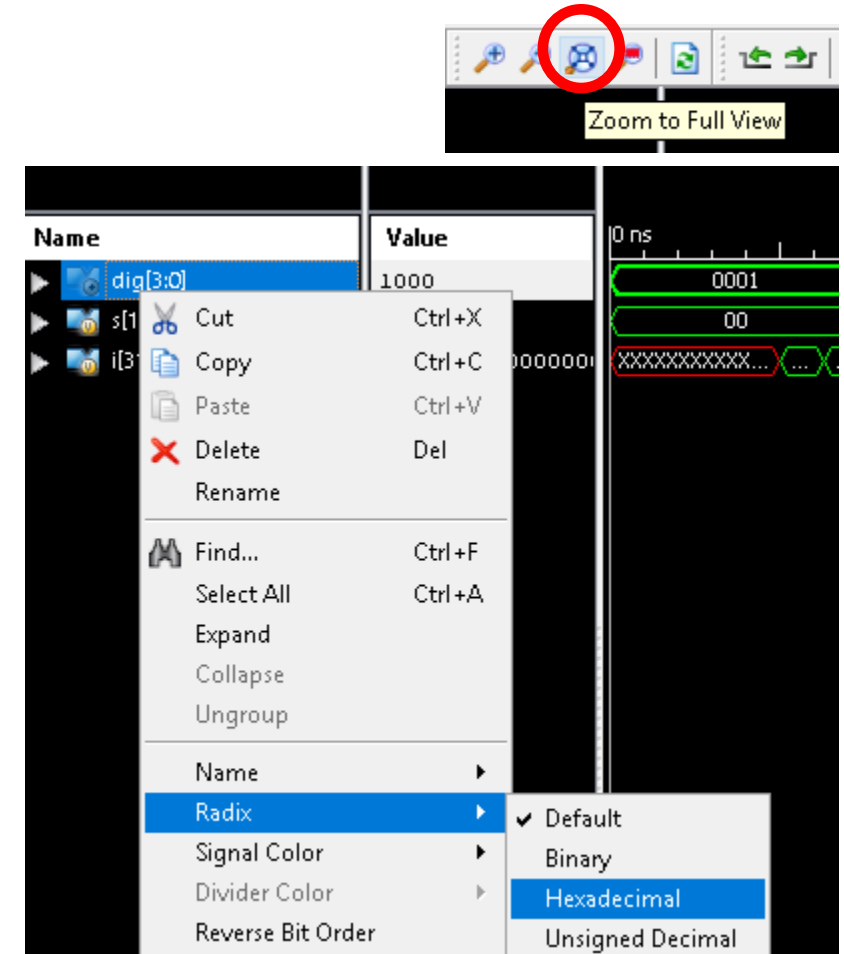- Press the “Zoom to Full View” button
- Switch to hexadecimal number representation for the dig[3:0] and s[1:0] signals.



Digital design lab 4A



- Check the simulation results:

 

- The output is the following: $s=00 \rightarrow \text{dig}=0001$, $s=01 \rightarrow \text{dig}=0010$, $s=10 \rightarrow \text{dig}=0100$, $s=11 \rightarrow \text{dig}=1000$. Is that correct?
- Close the simulator


Digital design lab 4A

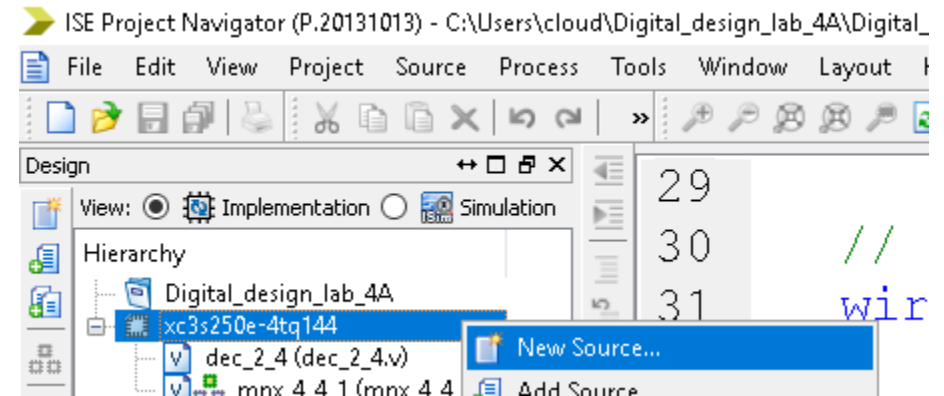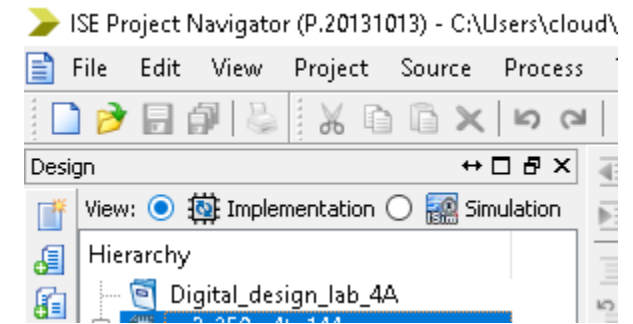- Switch back to implementation mode
- Right click on the label, and select New Source...



Digital design lab 4A

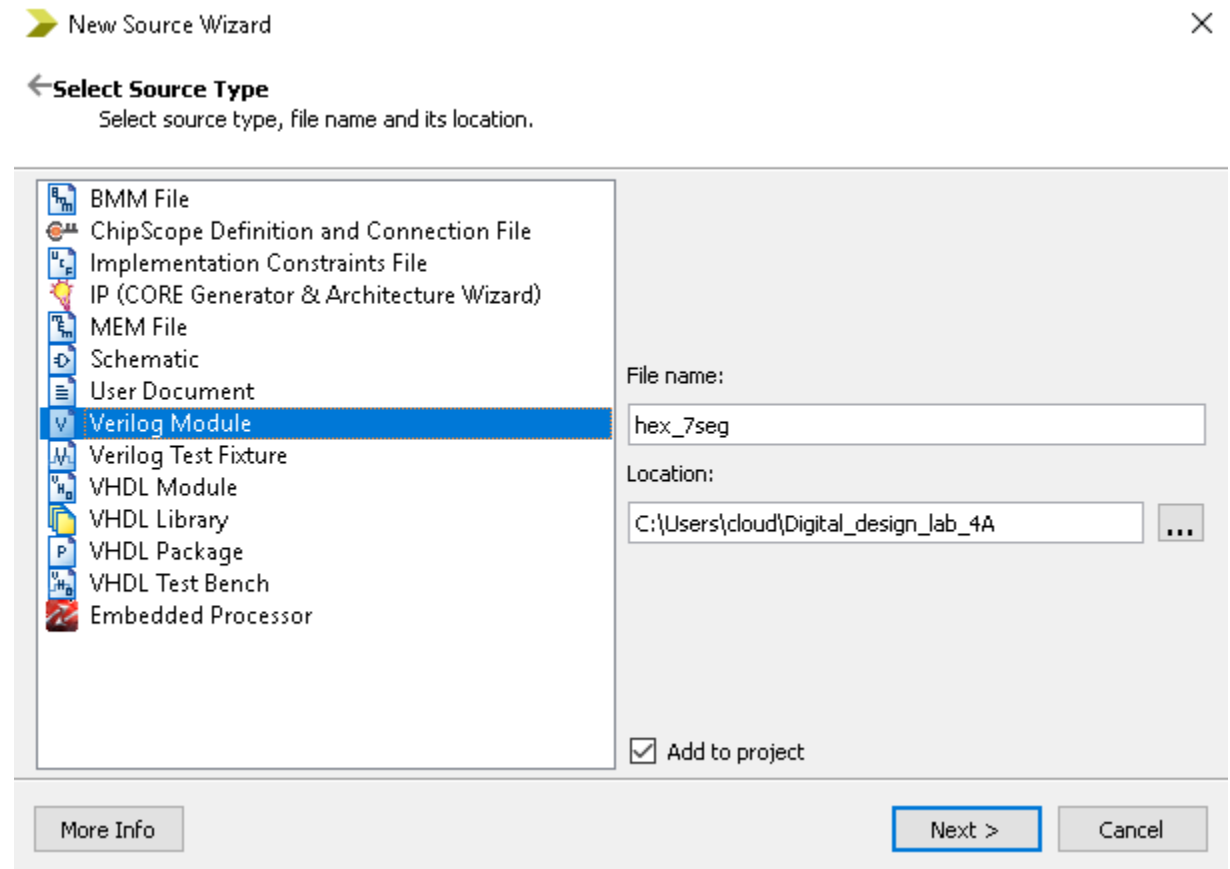- Name: hex7_seg
- Don't modify the location
- Check "Add to project"
- Press Next



Digital design lab 4A

- Leave the table blank
- Press Next, then Finish

New Source Wizard ✕

← **Define Module**
Specify ports for module.

Module name

Port Name	Direction	Bus	MSB	LSB
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		

Digital design lab 4A

- Add the following code
- Mind the reg keyword

```
21 module hex_7seg(  
22     input [3:0] hex,  
23     output reg [7:0] seg  
24 );  
25  
26  
27 endmodule  
28
```

- Copy and paste the code from the next slide above `endmodule`
- This will be the implementation of the hexadecimal to 7-segment converter, the output is defined for every possible input in the body of a case statement
- Think about it: otherwise we would have to design a 4-input combinational circuit for every LED, minimize the Boolean functions, and implement each

```
always @ (*)
```

```
    case (hex)
```

```
        4'b0000 : seg <= 7'b0111111; // 0
```

```
        4'b0001 : seg <= 7'b0000110; // 1
```

```
        4'b0010 : seg <= 7'b1011011; // 2
```

```
        4'b0011 : seg <= 7'b1001111; // 3
```

```
        4'b0100 : seg <= 7'b1100110; // 4
```

```
        4'b0101 : seg <= 7'b1101101; // 5
```

```
        4'b0110 : seg <= 7'b1111101; // 6
```

```
        4'b0111 : seg <= 7'b0000111; // 7
```

```
        4'b1000 : seg <= 7'b1111111; // 8
```

```
        4'b1001 : seg <= 7'b1101111; // 9
```

```
        4'b1010 : seg <= 7'b1110111; // A
```

```
        4'b1011 : seg <= 7'b1111100; // b
```

```
        4'b1100 : seg <= 7'b0111001; // C
```

```
        4'b1101 : seg <= 7'b1011110; // d
```

```
        4'b1110 : seg <= 7'b1111001; // E
```

```
        4'b1111 : seg <= 7'b1110001; // F
```

```
        default : seg <= 7'b0000000; // 0
```


```
    endcase
```

Digital design lab 4A


- Save all changes



- Add another source to the project

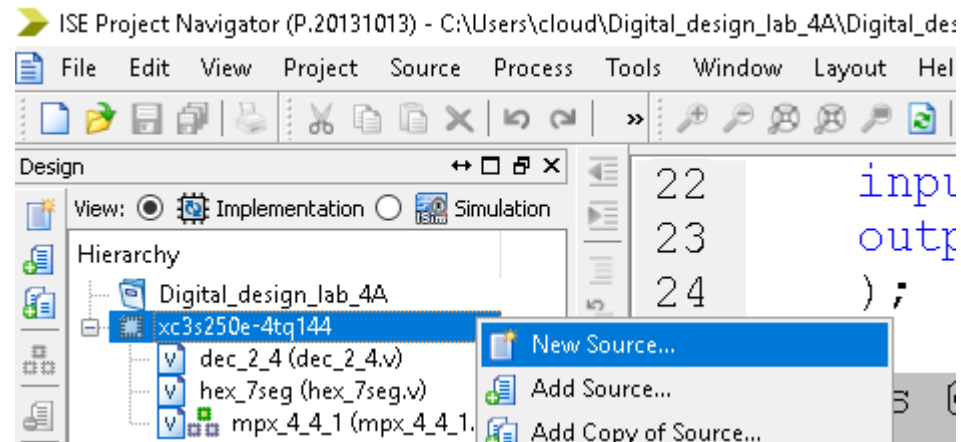

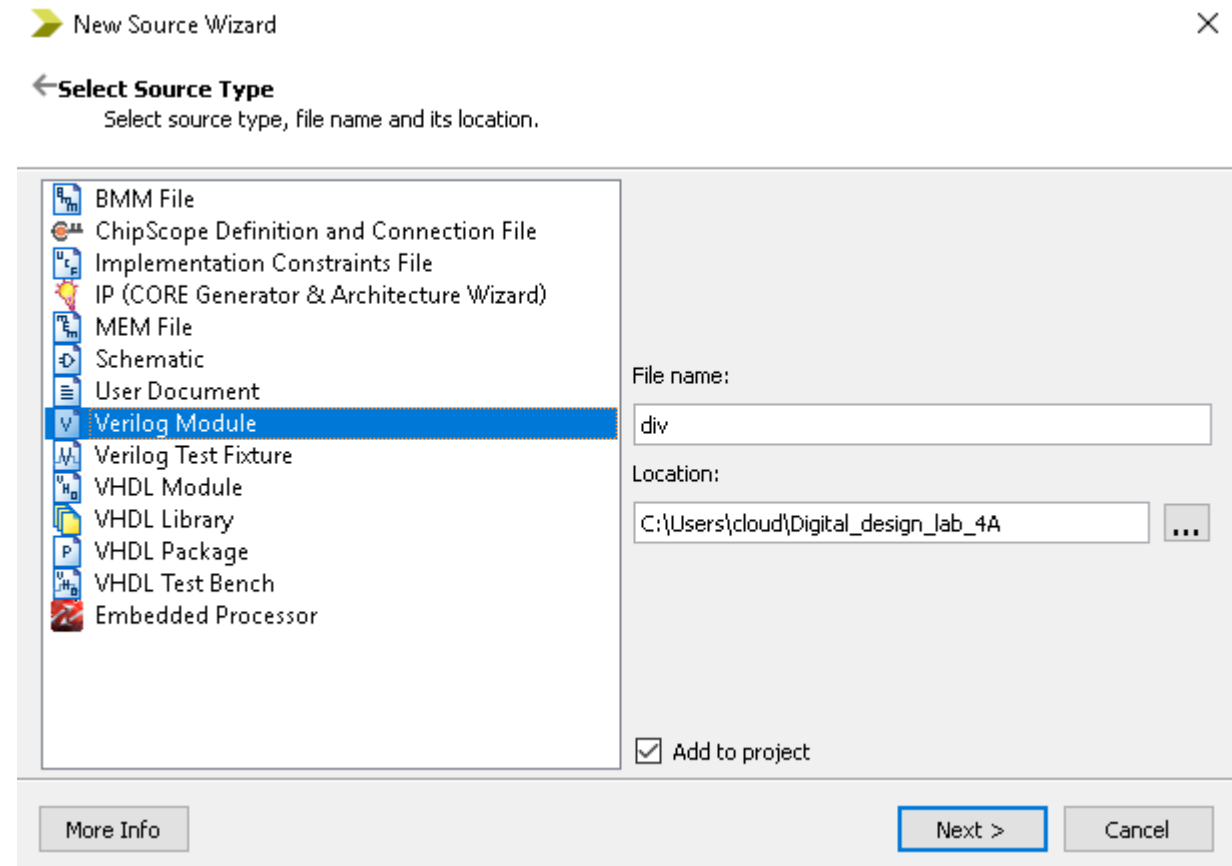- This is the “div” clock divider, a sequential circuit that counts from 0 to 3
- Right now we do not go into the details, since you have not heard about sequential circuits
- Name: div
- Don’t modify location
- Check “Add to project”
- Press Next



Digital design lab 4A

- Leave the table blank
- Press Next, then Finish

New Source Wizard ×

← Define Module
Specify ports for module.

Module name

Port Name	Direction	Bus	MSB	LSB
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		

Digital design lab 4A


- Add the following source code

```
21 module div(  
22     input clk,  
23     output reg [1:0] s  
24 );  
25  
26     always @ (posedge clk)  
27     begin  
28         s <= s + 1;  
29     end  
30 endmodule
```

- Save your changes 


Digital design lab 4A

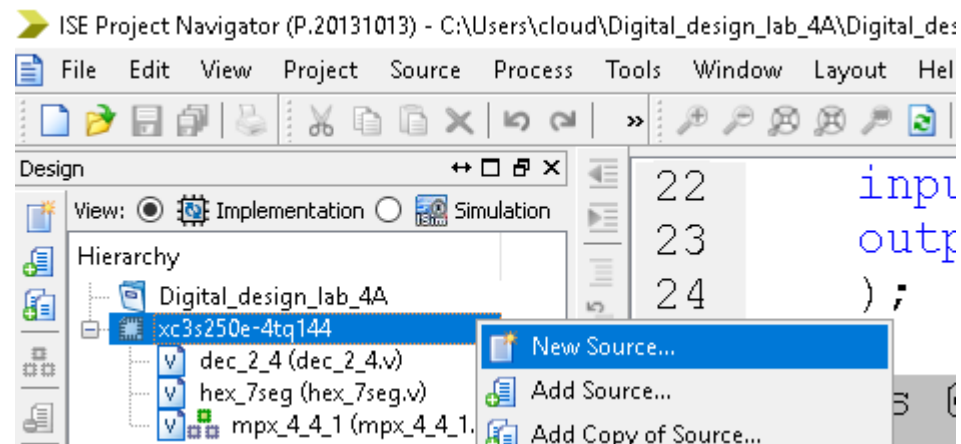- Now you can implement the top module, that connects all submodules together



Digital design lab 4A

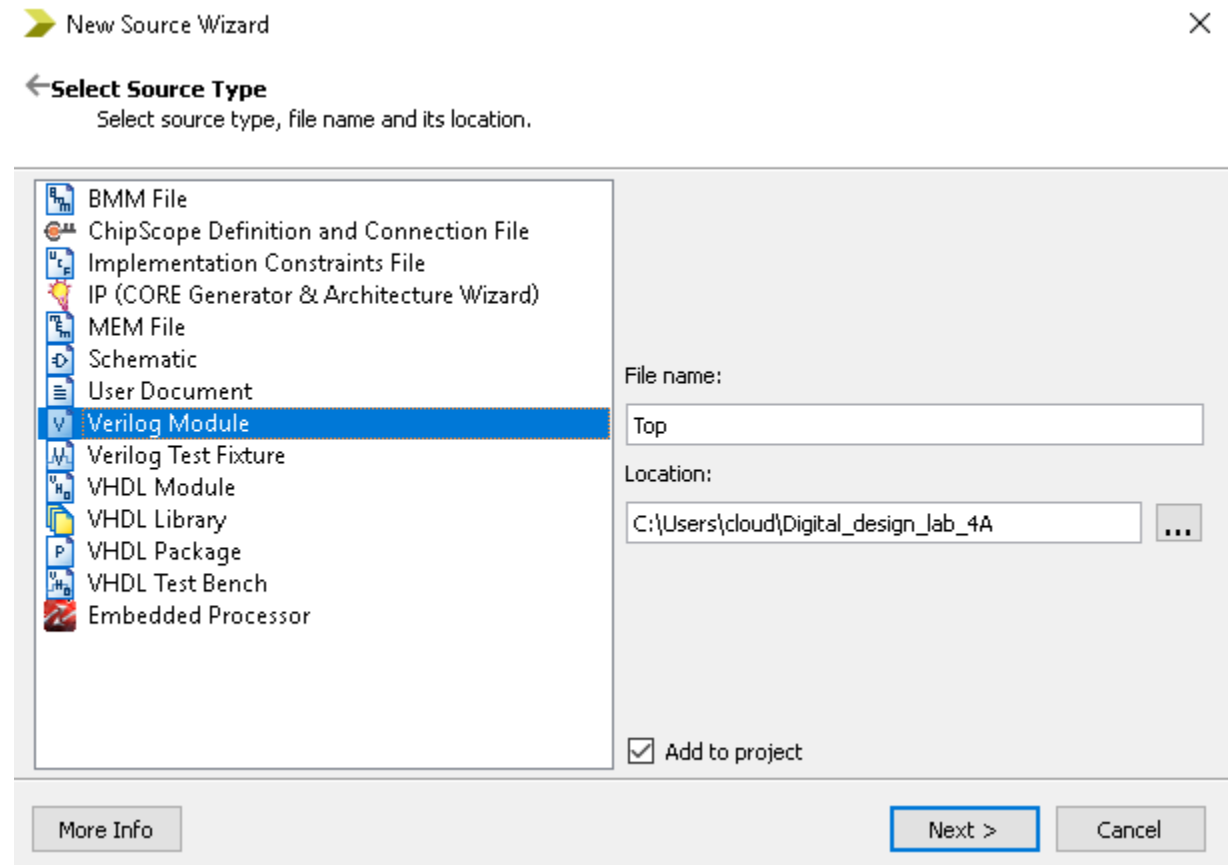- Name: Top
- Don't modify location
- Check "Add to project"
- Press Next



Digital design lab 4A

- Table: blank
- Next + Finish

New Source Wizard

← Define Module
Specify ports for module.

Module name: Top

Port Name	Direction	Bus	MSB	LSB
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		

More Info < Back **Next >** Cancel

Digital design lab 4A

- First add the declaration of the module:
- The “_n” tag after seg and dig means that these are negative logic signals:

```
21 module Top(  
22     input [7:0] sw,  
23     output [7:0] seg_n,  
24     output [3:0] dig_n,  
25     input clk  
26 );  
27  
28  
29 endmodule
```

Digital design lab 4A

- Then add the following wires:
 - a, b (for sw[3:0] and sw[7:4])
 - s (for the output of the div module)
 - dig (digit selector for the display)
 - seg (LED control input for the display)
 - num (multiplexor input)
 - out (multiplexor output)

```
21 module Top(  
22     input  [7:0] sw,  
23     output [7:0] seg_n,  
24     output [3:0] dig_n,  
25     input  clk  
26 );  
27  
28     wire [3:0] a;  
29     wire [3:0] b;  
30     wire [1:0] s;  
31     wire [3:0] dig;  
32     wire [3:0] out;  
33     wire [15:0] num;  
34     wire [7:0] seg;  
35  
36  
37 endmodule
```

Digital design lab 4A

- Add the following assignments:
- Note that a+b will be connected to the lower 8 inputs of the multiplexor
- Since dig_n and seg_n are negative logic signals, we invert the values of dig and seg before the assignment.
- Note: dig and seg are 4 and 8 bits long.
You can apply the ~ operator on N-bit wide wires, it will invert all bits
- For example, if x=1001, then ~x=0110.

```
34     wire [7:0] seg;
35
36     assign a = sw[7:4];
37     assign b = sw[3:0];
38     assign num[15:12] = a;
39     assign num[11:8] = b;
40     assign num[7:0] = a + b;
41     assign dig_n = ~dig;
42     assign seg_n = ~seg;
43
44     endmodule
```

Digital design lab 4A

- The last step is the instantiation of the submodules: we need to define which wires of the Top module do we connect to the inputs and outputs of a given submodule.
- We also have to give a name for the instantiated submodule, since we can have multiple modules of the same type.
- Imagine you have a mod module with in input and out output. You want to connect the x wire to the input of the module, and y to the output. The syntax of the instantiation is:
`mod mod1 (.input(x), .output(y));`
- Now mod1 is the name of the current instance

Digital design lab 4A


- Instantiate your submodules in the following way:

```
42     assign seg_n = ~seg;
43
44     div DIV(.clk(clk), .s(s));
45     dec_2_4 DEC(.s(s), .dig(dig));
46     mpx_4_4_1 MPX(.s(s), .num(num), .out(out));
47     hex_7seg H7S(.hex(out), .seg(seg));
48
49     endmodule
```

- Save all changes 

Digital design lab 4A

 
- After the instantiation, you will see that all submodules are organized under the Top module:



- The ISE indents the submodules under Top to show that they are on a lower hierarchical level


Digital design lab 4A

- Now we will implement and download the module to the FPGA board. A file has been prepared for this purpose, you can download it using the following link: [download](#)
- If the browser opens the file instead of displaying the download dialog window: right click, and select “Save as...”
- Download the file, and save it to the **current working directory** of your project (D:\Digital_design_lab_4A).
- If you are not sure, you can check it in the title bar of the ISE (top of the ISE window)

 


Digital design lab 4A

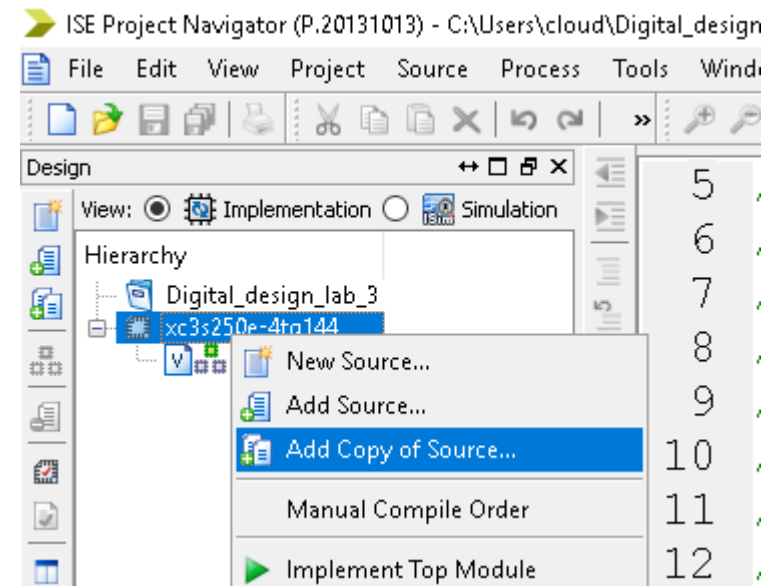- Go back to the ISE, right click on the „xc3s250e-4tq144” label and select „Add copy of source”




Digital design lab 4A

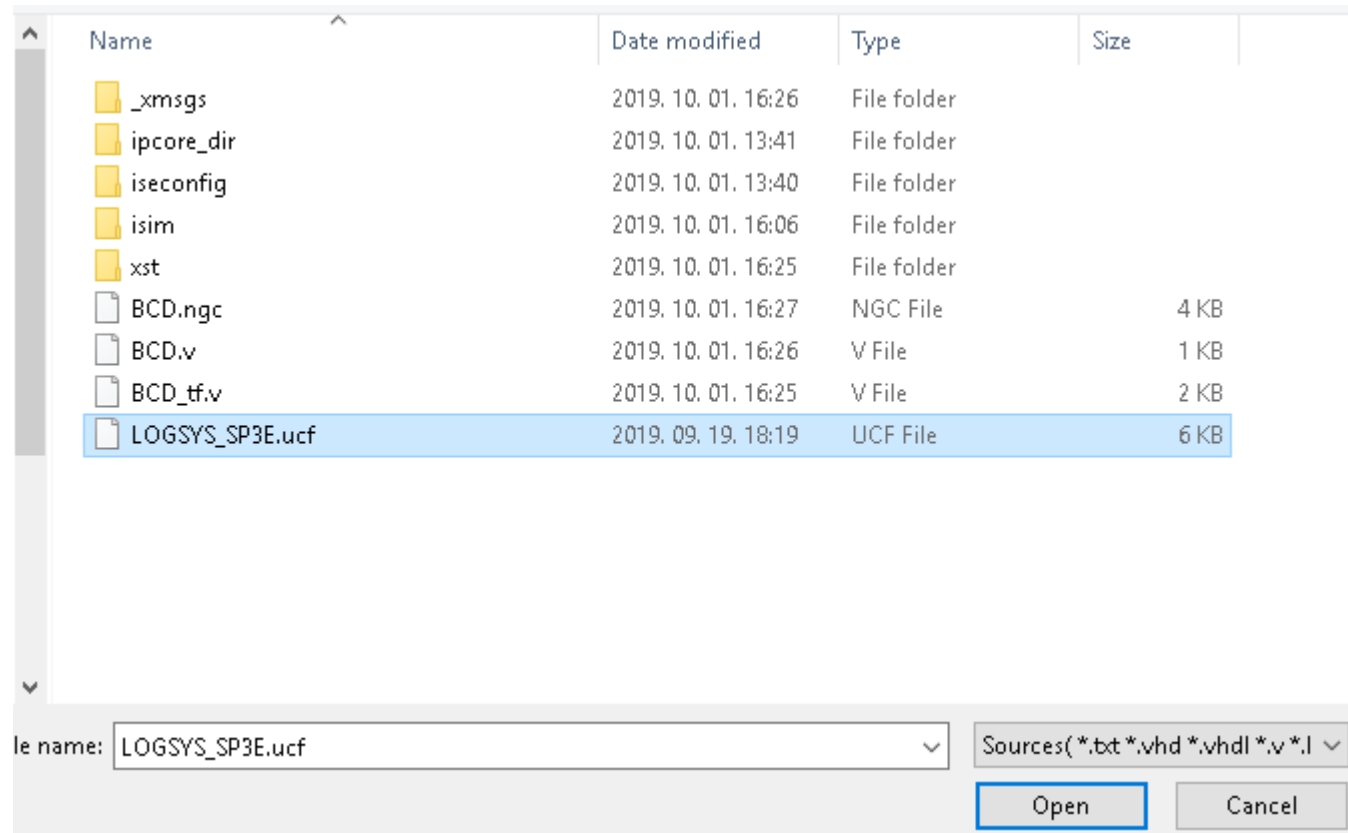- Browse the file you have downloaded, select it and press Open:



Digital design lab 4A

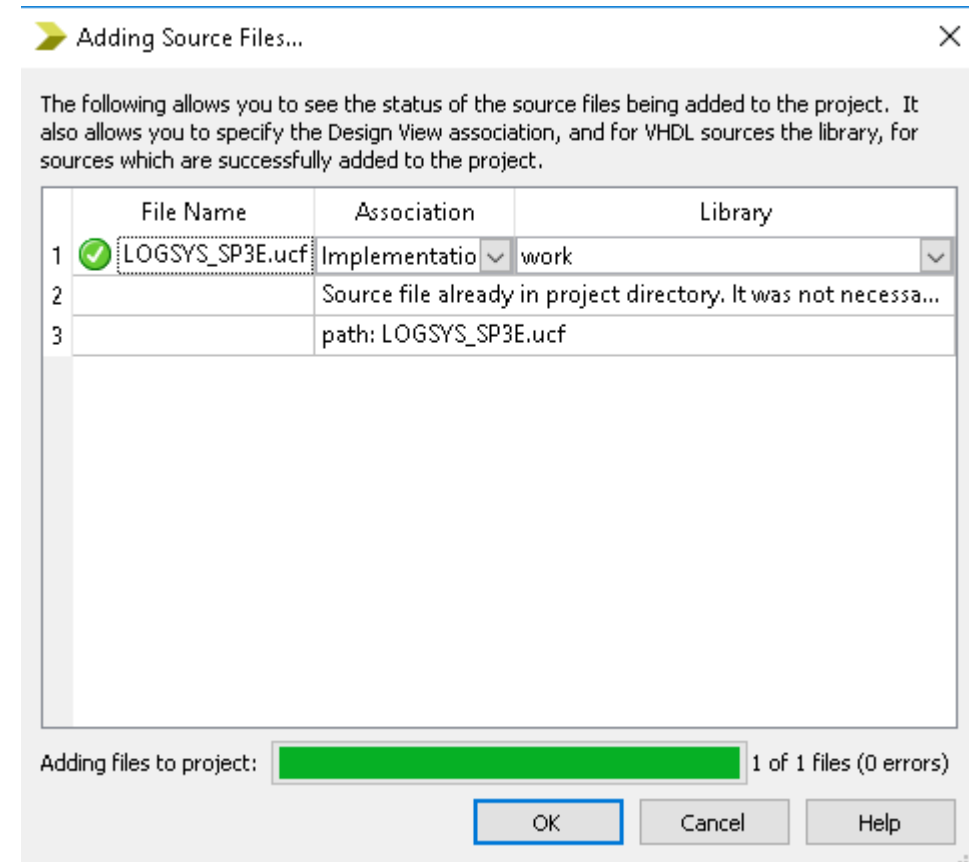
- The following window appears:
- Press OK
- If you have difficulties, ask for assistance



Digital design lab 4A

- Now open the previously added file. Uncomment the clk signal first: select the line, right click and select Uncomment-> Line(s)


```
10 # LOGSYS Fejlesztőkábel GUI vezérlő és kc
11 #NET "mosi"      LOC = "P120";
12 #NET "miso"     LOC = "P143";
13 #NET "clk"      LOC = "P129" | PULLDOWN;
14 #NET "rst"     LOC = "P129" | PULLDOWN;
15
16 # 4 darab aktív gomb, balról :
17 #NET "bt<3>"
18 #NET "bt<2>"
19 #NET "bt<1>"
20 #NET "bt<0>"
```

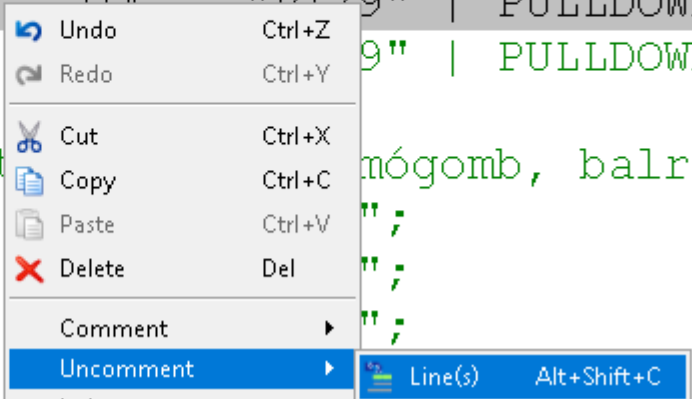

Digital design lab 4A

- Then uncomment the sw signals:

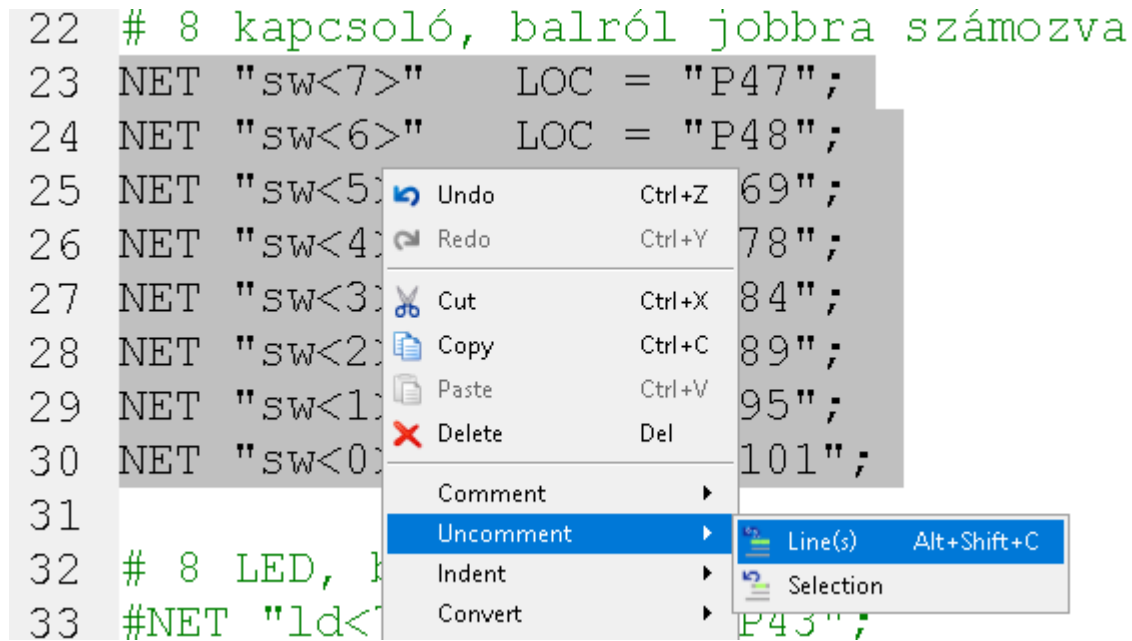
```
22 # 8 kapcsoló, balról jobbra számozva
23 NET "sw<7>" LOC = "P47";
24 NET "sw<6>" LOC = "P48";
25 NET "sw<5>" LOC = "P69";
26 NET "sw<4>" LOC = "P78";
27 NET "sw<3>" LOC = "P84";
28 NET "sw<2>" LOC = "P89";
29 NET "sw<1>" LOC = "P95";
30 NET "sw<0>" LOC = "P101";
31
32 # 8 LED, balról jobbra számozva
33 #NET "ld<7>" LOC = "P43";
```



Digital design lab 4A

- Finally, uncomment the dig_n signals
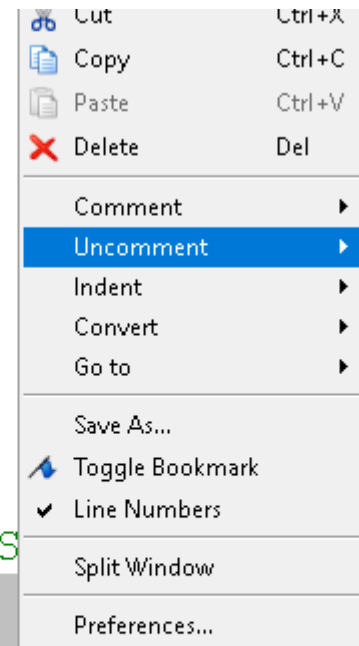
```
# 4 digités kijelző aktív ALACS
#NET "dig_n<3>" LOC = "P22";
#NET "dig_n<2>" LOC = "P26";
#NET "dig_n<1>" LOC = "P35";
#NET "dig_n<0>" LOC = "P40";
```





7 <- tizedes]

rálóasztó jelei,


Digital design lab 4A

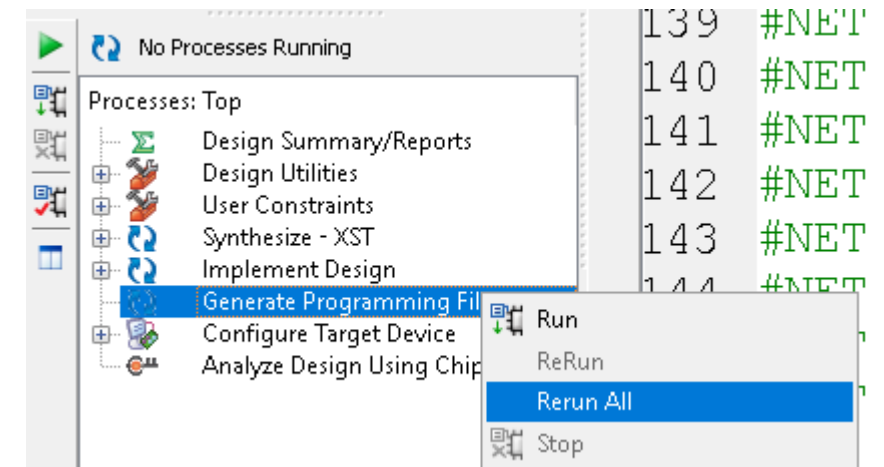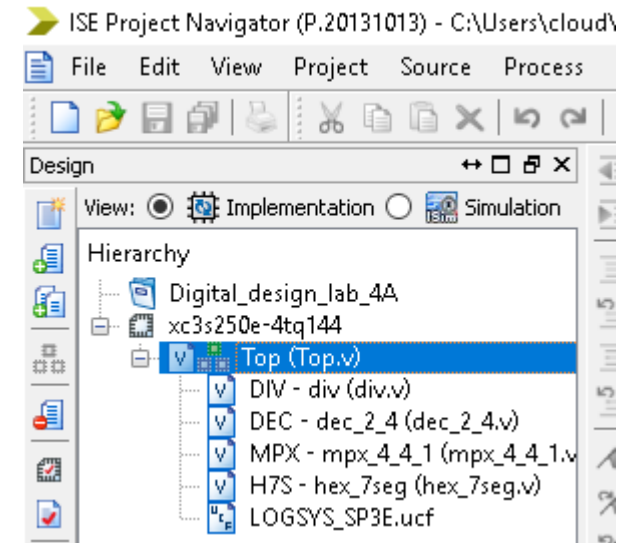- Now you can generate the programming file
- First, left click on the Top module in the top left corner
- Then right click on “Generate Programming File”, and select “Rerun All”



Digital design lab 4A

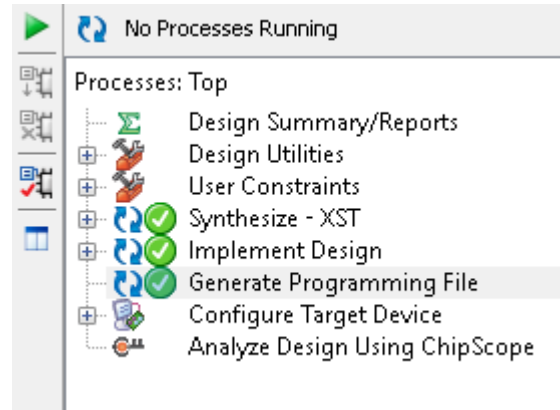- After the generation, you should see this.



- If you see errors or warnings, ask for assistance.

Digital design lab 4A

- If the program file was generated successfully, you can connect the FPGA board to the PC
- Mind the orientation of the JTAG connector!




Digital design lab 4A

- Launch the Logsys GUI application




 - Press the +5V button to turn the board on




Digital design lab 4A

 
- On the right side of the screen, select JTAG download:



- Press the „Query JTAG chain” button

 


 - Then press „Configure the Selected Device”




Digital design lab 4A

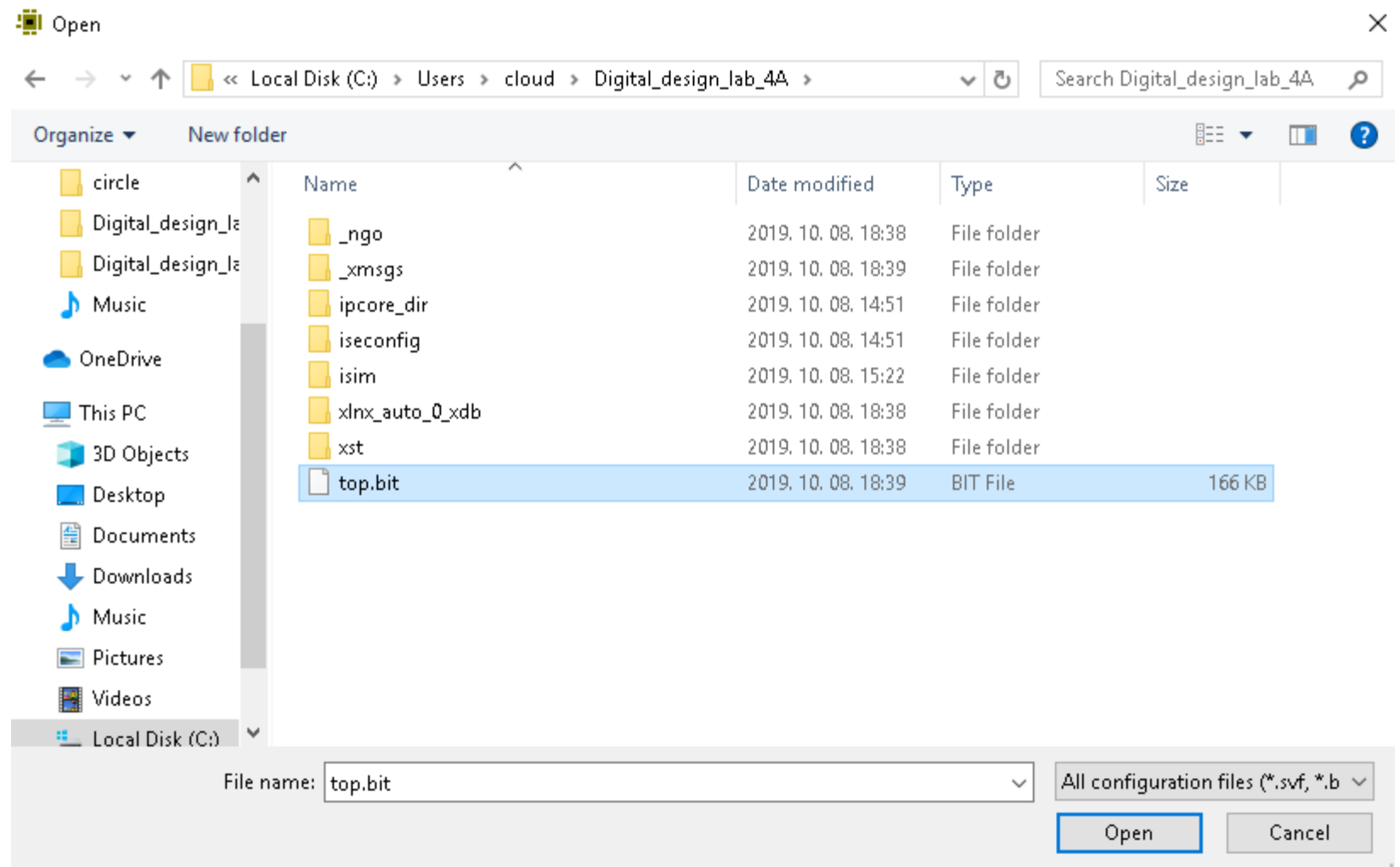- Browse the generated file in your working directory
- Press Open



Digital design lab 4A

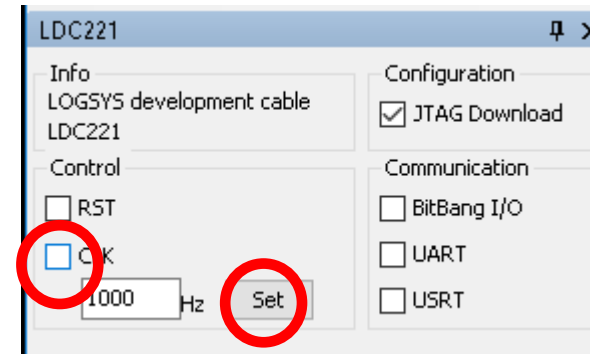- The circuit requires to add a system clock input for the circuit
- First set the value of the clock frequency to 1000
- Press the Set button
- Click into the CLK checkbox
- Note: on Windows 10 the tick might not appear, but it should be fine



Digital design lab 4A

- Now try to set different inputs on the switches. Can you see the correct values and their sum on the 7-segment display?
- If you want to see the circuit in “slow motion”, first set the frequency to 1-2 Hz, press then press the Set button.
- Now you can see the circuit selecting the individual digits one by one.
- This can't be seen when the clock frequency is high, due to the dynamics of the human eye.