 


# Digital design laboratory 7

# Counters

- Today we are going to implement a 16 bit counter using four 4-bit counters
- The output of the counters will be displayed on the 7 segment led display
- The counter can be enabled using the buttons of the FPGA
- The value set on the switches can be loaded into the first two counters (lower 8 bit).

# Counters



# Counters

- Launch Xilinx ISE Design Suite
- File->New Porject...
- Name: DigLab7
- Location: D:\DigLab7
- Press Next twice
- Press Finish

**New Project Wizard**

**Create New Project**  
Specify project location and type.

Enter a name, locations, and comment for the project

Name: DigLab7

Location: D:\DigLab7

Working Directory: D:\DigLab7

Description:


Select the type of top-level source for the project

Top-level source type:  
HDL

More Info      Next >      Cancel

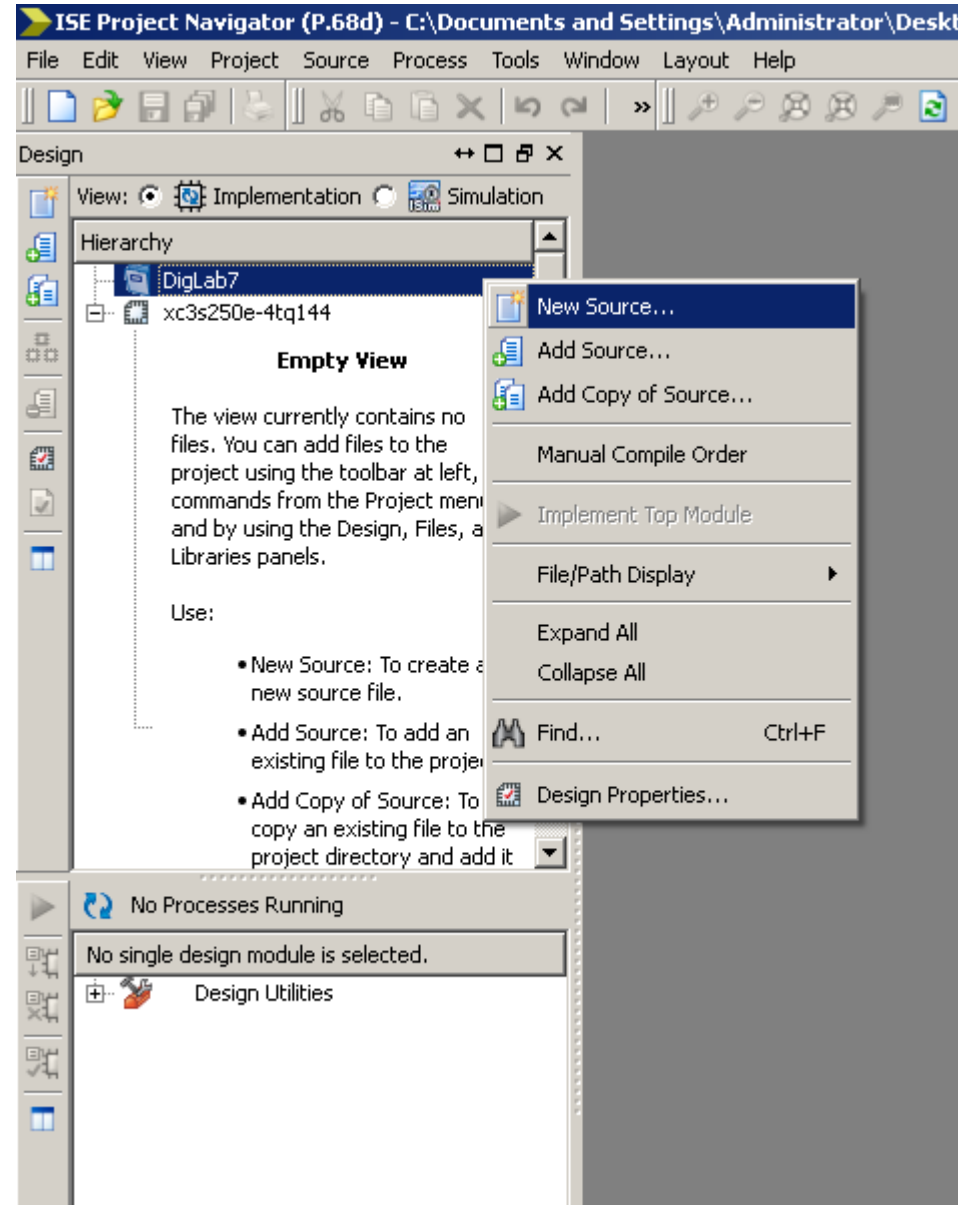
# Counters

- Add the Topmodule
- Right click on the project
- Select New Source...



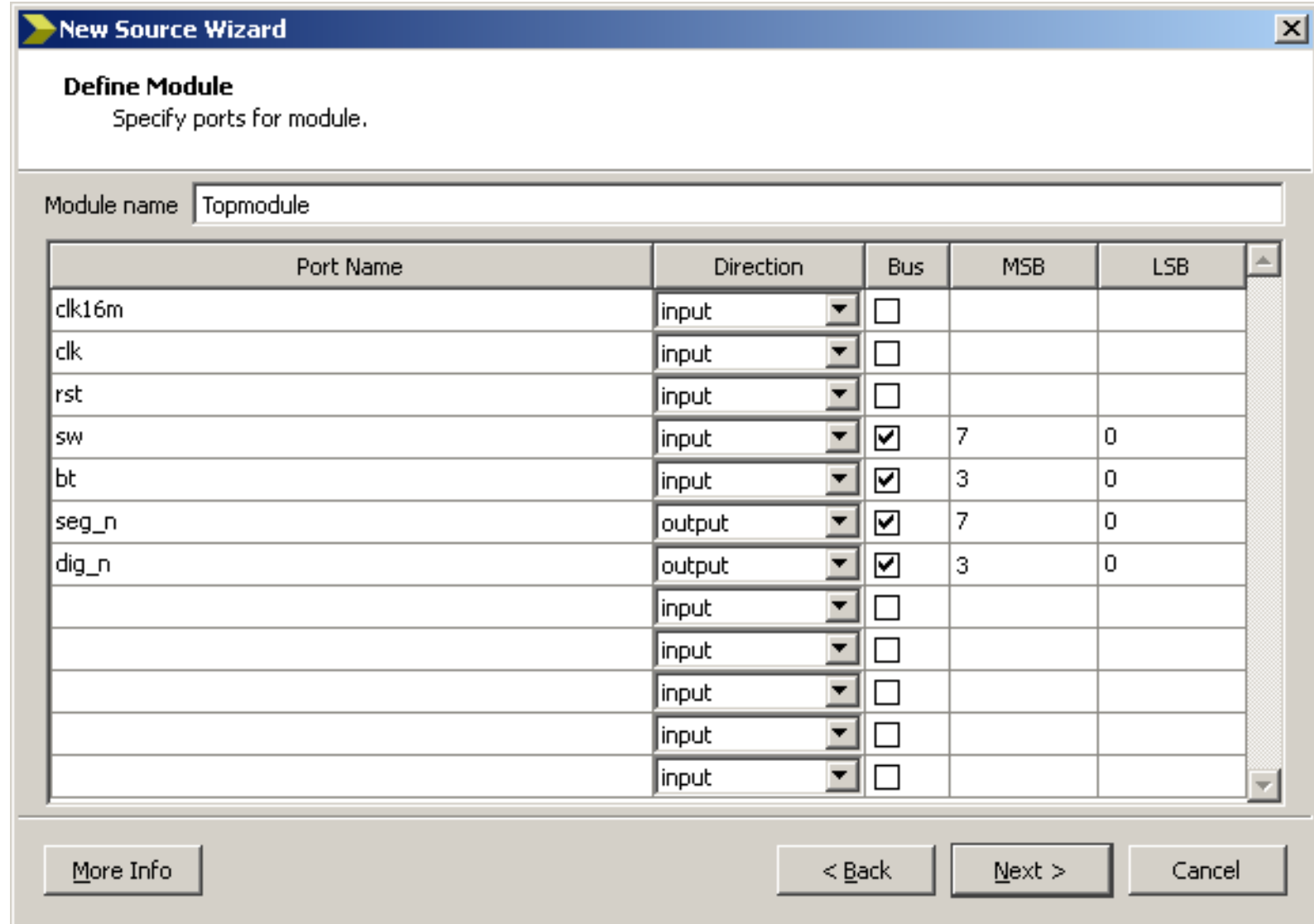
# Counters

- Select Verilog Module
- Name: Topmodule
- Press next
- Inputs:  
clk16m, clk, rst,  
sw [7:0], bt[3:0]
- Outputs:  
seg\_n [7:0],  
dig\_n [3:0]
- Press Next, then Finish


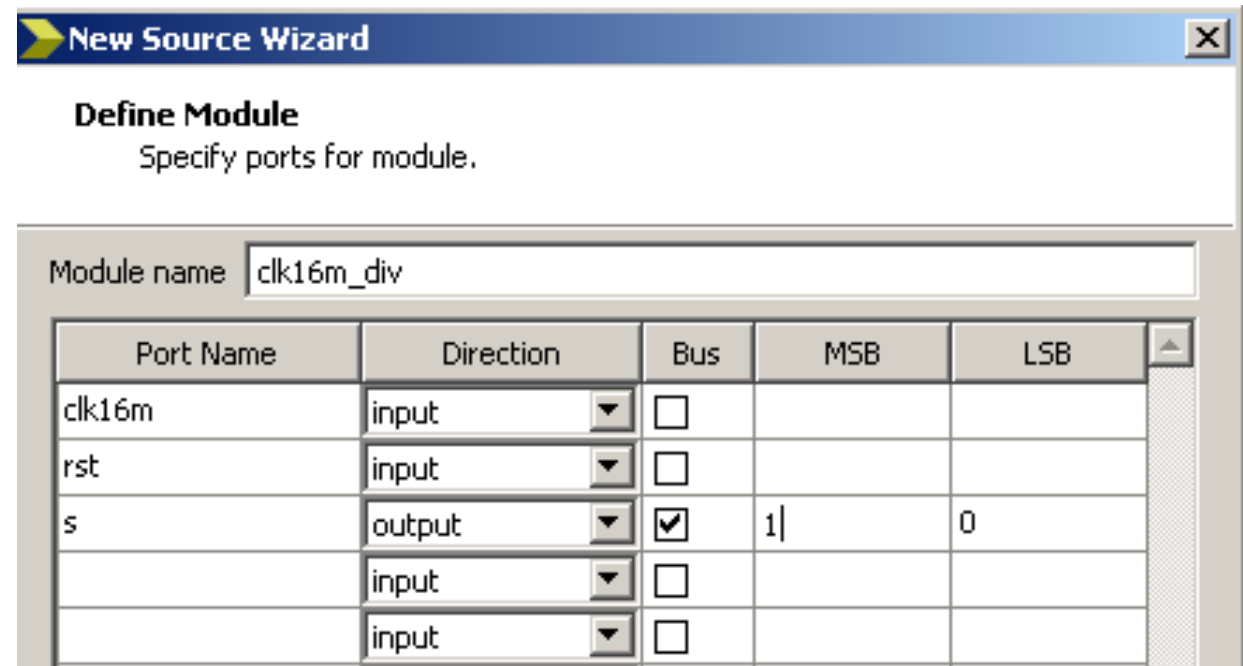
# Counters

- To use the 7 segment display, we need a 4x1 multiplexer and a decoder. First we need a select signal to control these circuits.
- The refresh rate of the LEDs will be 1 kHz
- The 16 MHz clk16m signal will be used
- Add a new module to the project
- Name: clk16m\_div
- Input: clk16m, rst
- Output: s [1:0]



# Counters

- Define the s output as a register
- Add the following source code to clk16\_div

```
21 module clk16m_div(  
22     input clk16m,  
23     input rst,  
24     output reg [1:0] s  
25 );  
26  
27 reg [15:0] count_reg;  
28 wire count_16000;  
29  
30 assign count_16000 = (count_reg == 16'd15999);  
31  
32 always @ (posedge clk16m)  
33 if (rst)  
34     begin  
35         count_reg <= 16'd0;  
36         s <= 2'd0;  
37     end  
38 else if (count_16000)  
39     begin  
40         count_reg <= 16'd0;  
41         s <= s + 2'd1;  
42     end  
43 else count_reg <= count_reg + 1;
```






# Counters

- Multiplexer implementation:

```
21 module MUX4x1(  
22     input [15:0] data_in,  
23     input [1:0] sel,  
24     output reg [3:0] data_out  
25 );  
26  
27 always @ (*)  
28 case (sel)  
29     2'b00: data_out <= data_in[3:0];  
30     2'b01: data_out <= data_in[7:4];  
31     2'b10: data_out <= data_in[11:8];  
32     2'b11: data_out <= data_in[15:12];  
33 endcase  
34  
35  
36 endmodule
```
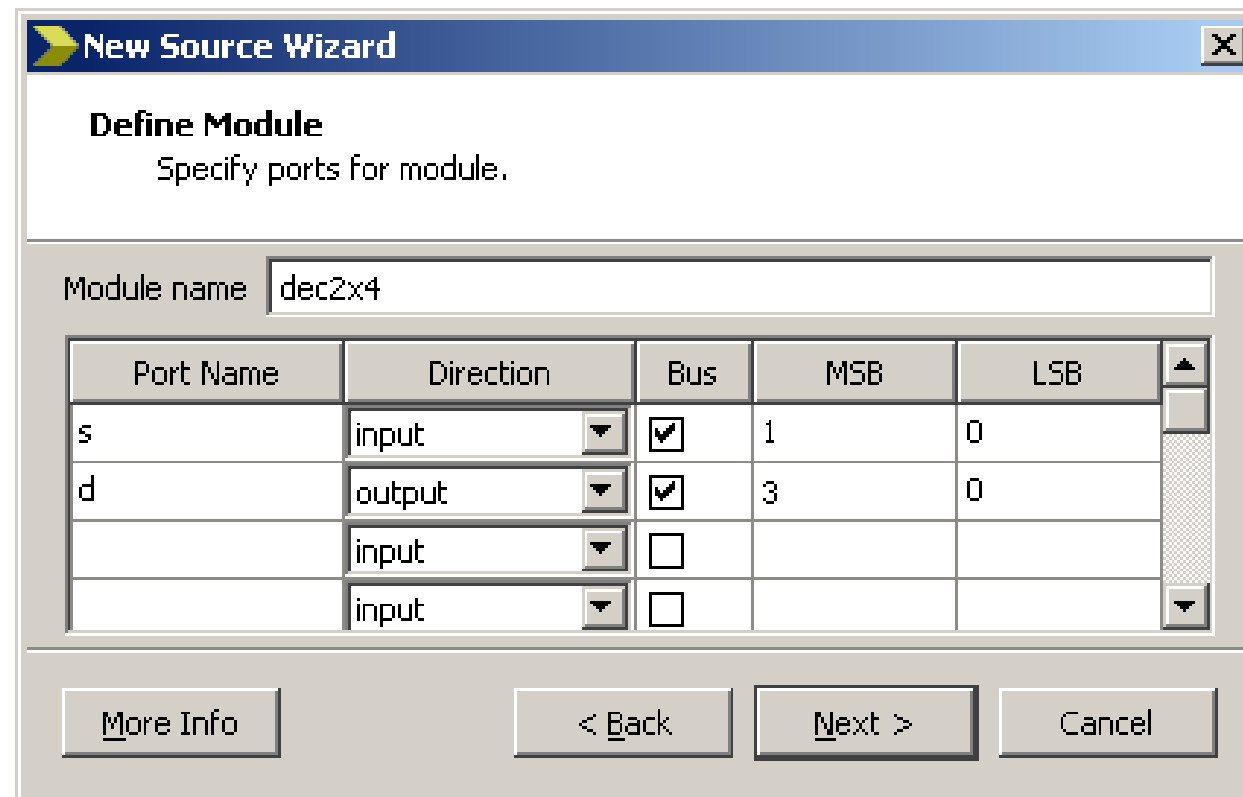
# Counters

- Now add the decoder module
- New source -> Verilog module
- Name: dec2x4




# Counters

- Decoder implementation:

```
21 module dec2x4(  
22     input [1:0] s,  
23     output reg [3:0] d  
24 );  
25  
26     always @ (*)  
27     case (s)  
28         2'b00: d <= 4'b0001;  
29         2'b01: d <= 4'b0010;  
30         2'b10: d <= 4'b0100;  
31         2'b11: d <= 4'b1000;  
32     endcase  
33  
34 endmodule  
35
```
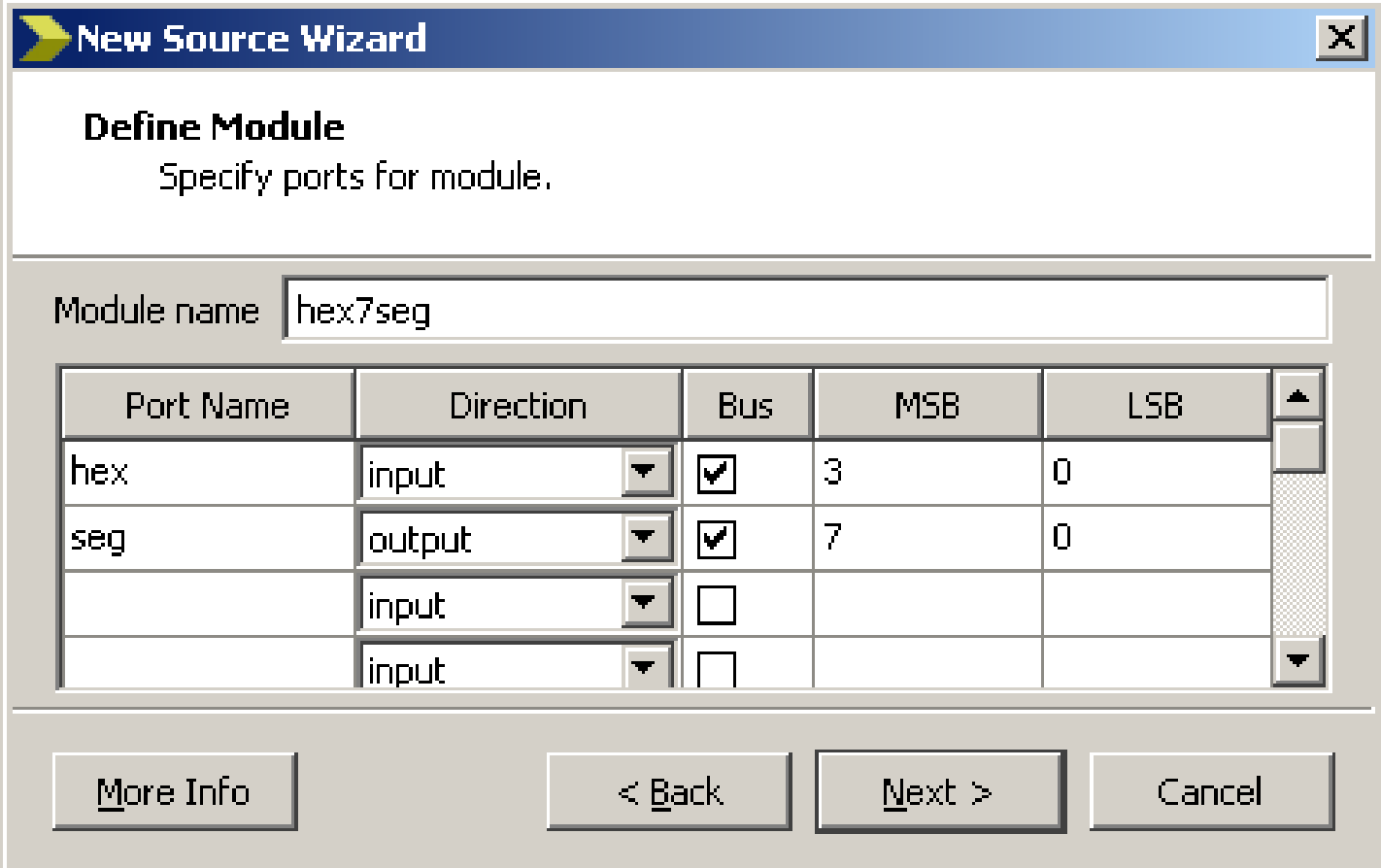
# Counters

- We need a converter for the 7-segment display
- Add new source
- Name: Hex7Seg
- Input: hex [3:0]
- Output seg [7:0]



**New Source Wizard**

**Define Module**  
Specify ports for module.

Module name:

Port Name	Direction	Bus	MSB	LSB
hex	input	<input checked="" type="checkbox"/>	3	0
seg	output	<input checked="" type="checkbox"/>	7	0
	input	<input type="checkbox"/>		
	input	<input type="checkbox"/>		

# Counters

- Add the reg keyword to the seg output
- Copy&Paste the code from the next slide

```
always @ (*)
```

```
    case (hex)
```

```
        4'b0000 : seg <= 8'b00111111; // 0
```

```
        4'b0001 : seg <= 8'b00000110; // 1
```

```
        4'b0010 : seg <= 8'b01011011; // 2
```

```
        4'b0011 : seg <= 8'b01001111; // 3
```

```
        4'b0100 : seg <= 8'b01100110; // 4
```

```
        4'b0101 : seg <= 8'b01101101; // 5
```

```
        4'b0110 : seg <= 8'b01111101; // 6
```

```
        4'b0111 : seg <= 8'b00000111; // 7
```

```
        4'b1000 : seg <= 8'b01111111; // 8
```

```
        4'b1001 : seg <= 8'b01101111; // 9
```

```
        4'b1010 : seg <= 8'b01110111; // A
```

```
        4'b1011 : seg <= 8'b01111100; // b
```

```
        4'b1100 : seg <= 8'b00111001; // C
```

```
        4'b1101 : seg <= 8'b01011110; // d
```

```
        4'b1110 : seg <= 8'b01111001; // E
```


```
        4'b1111 : seg <= 8'b01110001; // F
```

```
        default : seg <= 8'b00000000; // 0
```

```
    endcase
```
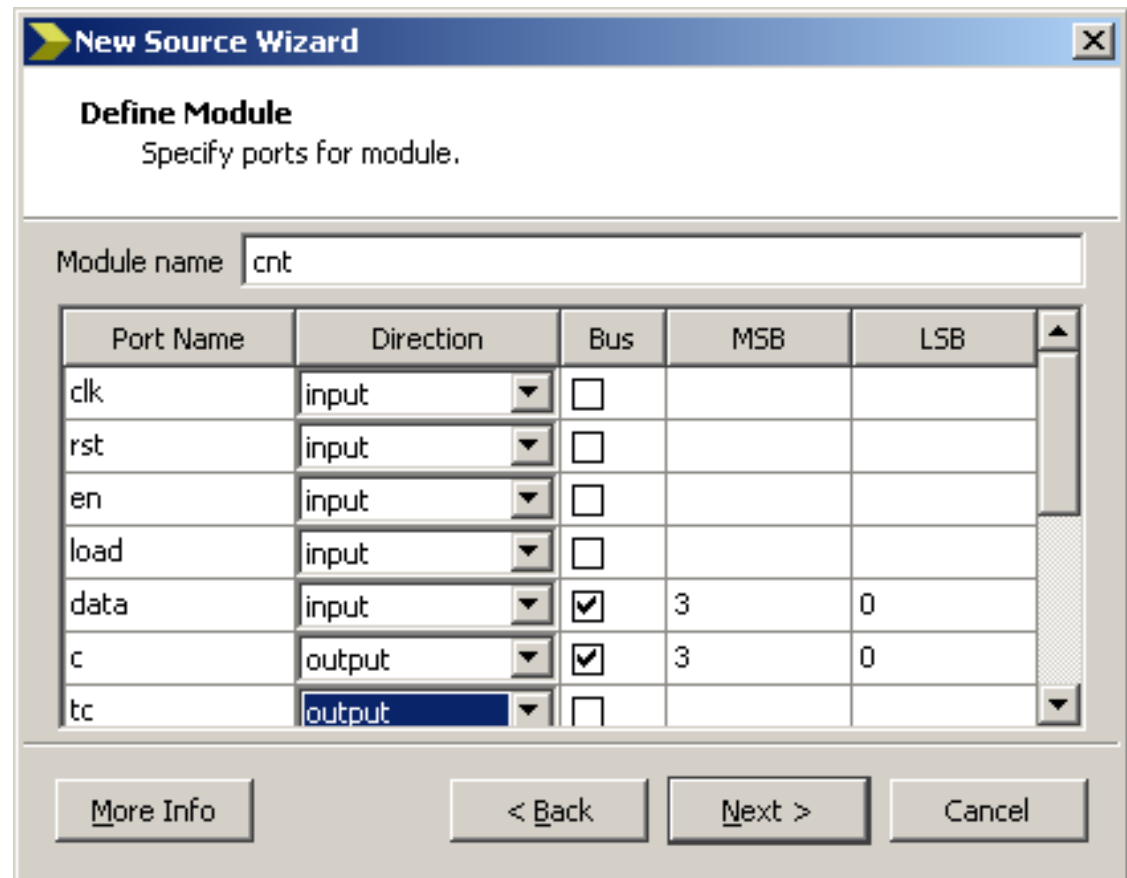
# Counters

- Now lets implement a four-bit counter circuit
- New source -> Verilog Module
- Name cnt
- Inputs:  
clk, rst, load, en, data [3:0]
- Outputs:  
c [3:0], tc





# Counters

- Add the reg keyword to the c output

- Source:

```
21 module cnt(  
22     input clk,  
23     input rst,  
24     input en,  
25     input load,  
26     input [3:0] data,  
27     output reg [3:0] c,  
28     output tc  
29 );  
30  
31  
32     assign tc = (c == 4'b1111);  
33  
34     always @ (posedge clk)  
35     if (rst) c <= 4'd0;  
36     else if (load)  
37         c <= data;  
38     else if (en)  
39         c <= c + 4'd1;  
40  
41 endmodule
```

# Counters

- Now go back to the Topmodule file
- The next task is the instantiation of the previous modules
- We start with the clk16m\_div module
- Add the following lines to the Topmodule:

```
27     output [7:0] seg_n,  
28     output [3:0] dig_n  
29 );  
30  
31     wire [1:0] sel;  
32  
33     clk16m div d(.clk16m(clk16m), .rst(rst), .s(sel));  
34  
35
```

# Counters

- Now add the multiplexer circuit:

```
wire [1:0] sel;
```

```
wire [15:0] mux_in;
```

```
wire [3:0] mux_out;
```

```
clk16m_div d(.clk16m(clk16m), .rst(rst), .s(sel));
```

```
MUX4x1 m(.data_in(mux_in), .sel(sel), .data_out(mux_out));
```

# Counters

- Next we instantiate the decoder and the hex7seg converter:

```
wire [1:0] sel;  
wire [15:0] mux_in;  
wire [3:0] mux_out;  
wire [7:0] seg;  
wire [3:0] dig;
```

```
assign dig_n = ~dig;  
assign seg_n = ~seg;
```

```
clk16m_div d(.clk16m(clk16m), .rst(rst), .s(sel));  
MUX4x1 m(.data_in(mux_in), .sel(sel), .data_out(mux_out));  
dec2x4 dec(.s(sel), .d(dig));  
hex7seg h(.hex(mux_out), .seg(seg));
```

# Counters

- Finally, implement the 4 counters:

```
wire [3:0] dig;  
wire en, load;  
wire [2:0] tc;  
assign en = bt[0]|bt[1];  
assign load = bt[2]|bt[3];
```

```
assign dig_n = ~dig;  
assign seg_n = ~seg;
```

```
clk16m_div d(.clk16m(clk16m), .rst(rst), .s(sel));  
MUX4x1 m(.data_in(mux_in), .sel(sel), .data_out(mux_out));  
dec2x4 dec(.s(sel), .d(dig));  
hex7seg h(.hex(mux_out), .seg(seg));
```

```
cnt c0(.clk(clk), .rst(rst), .en(en), .load(load), .data(sw[3:0]), .c(mux_in[3:0]), .tc(tc[0]));  
cnt c1(.clk(clk), .rst(rst), .en(tc[0]), .load(load), .data(sw[7:4]), .c(mux_in[7:4]), .tc(tc[1]));  
cnt c2(.clk(clk), .rst(rst), .en(tc[1]&tc[0]), .load(load), .data(4'd0), .c(mux_in[11:8]), .tc(tc[2]));  
cnt c3(.clk(clk), .rst(rst), .en(tc[2]&tc[1]&tc[0]), .load(load), .data(4'd0), .c(mux_in[15:12]), .tc());
```

# Counters

- Now you have to add the .ucf file
- Download it: [link](#)
- Unzip the file to the project directory
- Add it to the project with add source or add copy of source
- Uncomment the following lines:  
clk16m, clk, rst, bt (all), sw (all), seg\_n (all), dig\_n (all)
- Now generate the programming file
- After downloading, add CLK and test the counter

# Counters

- Try to add some functionality on your own:
  1. Modify the counter and the Topmodule:
    - bt[0]: enable and count up, bt[1]: enable and count down,
    - bt[2]: load value from switches into c0 and c1 counters
    - bt[3] load value from switches into c2 and c3 counters